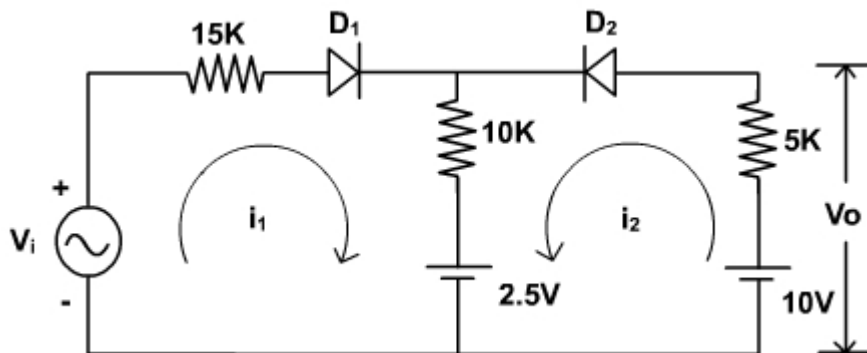



PH-218 Analog & Digital Electronics

Assignment-1 (Due date: 10th Jan 2011)


1. Draw the transfer characteristic of the circuit shown in fig.



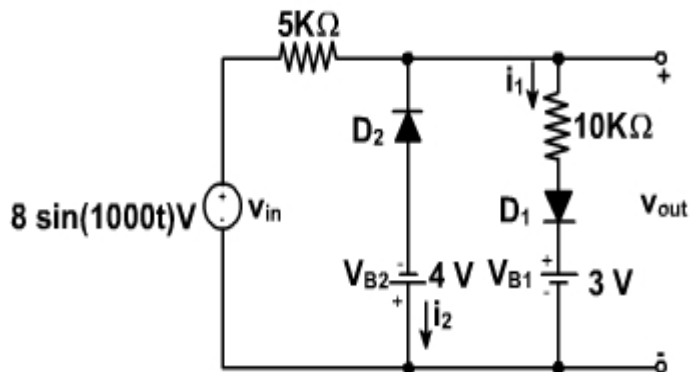2. Find the output voltage V_{out} of the clipper circuit of figure given below assuming that the diodes are (a) Ideal and (b) $V_{on} = 0.7 V$. For both cases, assume R_F is zero.



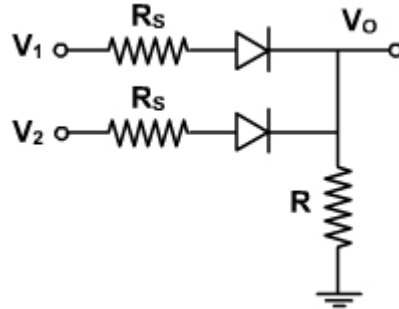3. Calculate the output voltage for (a) $V_1 = V_2 = 0$ (b) $V_1 = 0, V_2 = 5$ and vice versa (c) $V_1 = V_2 = 5$. Which logic gate is represented by this circuit?



Given: $R_s = 1\text{kohm}$ and $R = 10\text{kohm}$

4. Assuming a barrier potential of 0.7V and a reverse saturation current of 5nA at an ambient temperature of 25°C , what is the barrier potential and reverse saturation current of Si diode when the junction temperature is 100°C ?
5. Sedra & Smith Edition 5: problem 3.112
6. Sedra & Smith Edition 5: problem 3.99
7. Sedra & Smith Edition 5: problem 3.77 and 3.78