

Analog & Digital Electronics

Course No: PH-218

BJT

Lec-6: I-V characteristics and Ebers-Moll Model

Course Instructors:



❖ **Dr. A. P. VAJPEYI**




Department of Physics,
Indian Institute of Technology Guwahati, India

I-V Characteristics of BJT under common base configuration

Common Base configuration

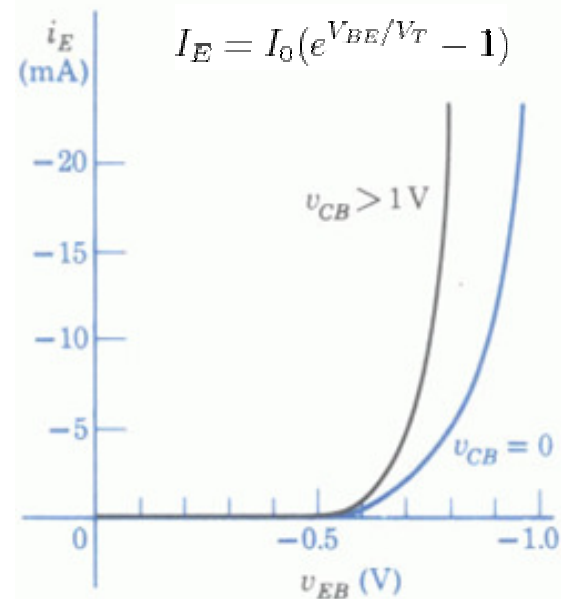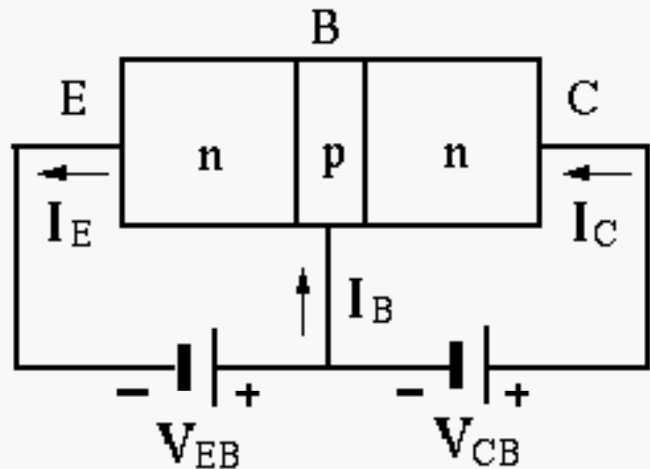

Input characteristics

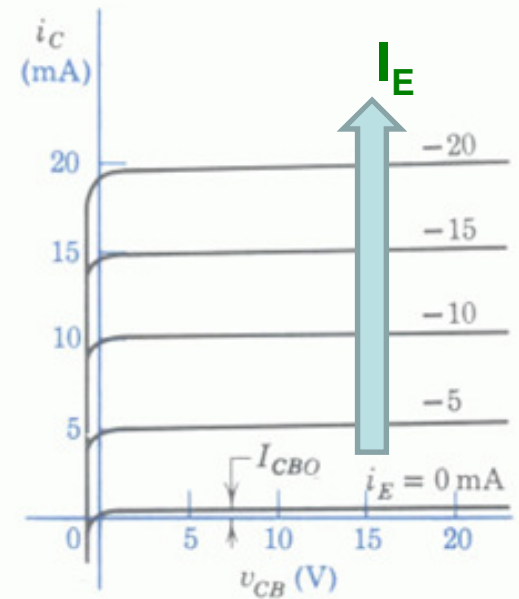


Output characteristics


- Input characteristics are like a normal forward biased diode.
- As the CB junction is reverse biased, the current I_C is independent of collector voltage and depends only upon the emitter current I_E . The collector current is almost constant and work as a current source.
- When $I_E=0$, $I_C=I_{CB0}$ is the leakage current caused by the minority carriers crossing the pn-junction.

$$I_C = \alpha I_E + I_{CB0}$$

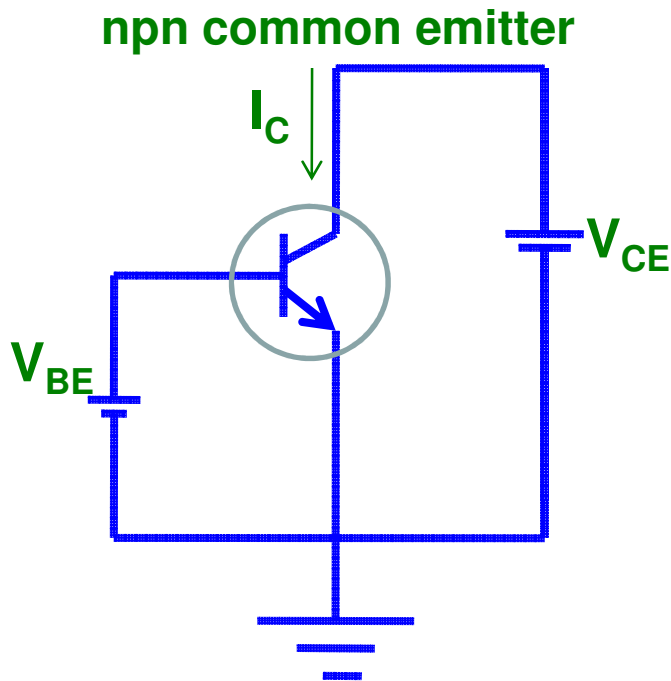
I-V Characteristics of BJT common emitter configuration



Input characteristics

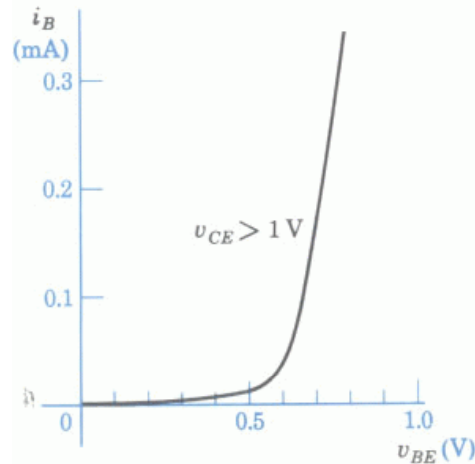

Output characteristics

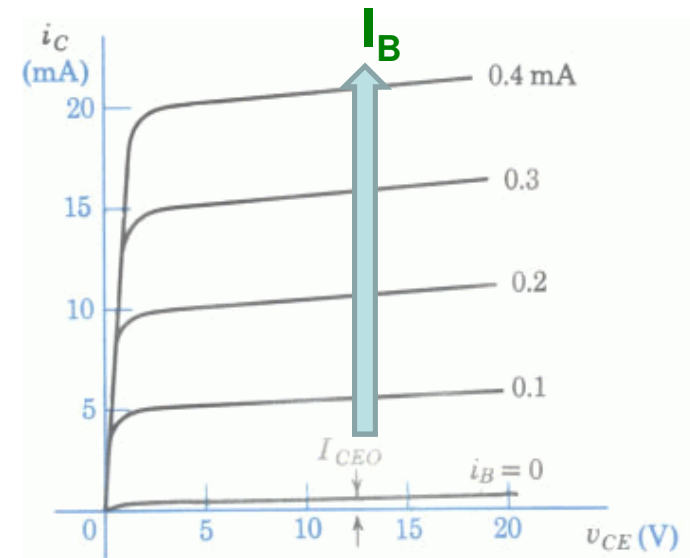

- Input characteristics are like a normal forward biased diode.
- As the CE junction is reverse biased, the current I_C is independent of collector voltage and depends only upon the base current I_B .
- In real diode, the collector current slightly increases with increase in collector emitter voltage (Early effect).
- At low value of V_{CE} , the CBJ becomes forward-biased and the transistor enters the saturation region.


Early Effect (Base width modulation)

Observed by James Early

$$I_C = I_s e^{\left(\frac{eV_{BE}}{kT}\right)} \left[1 + \frac{V_{CE}}{V_A} \right]$$

$$I_C = I_s e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right)$$

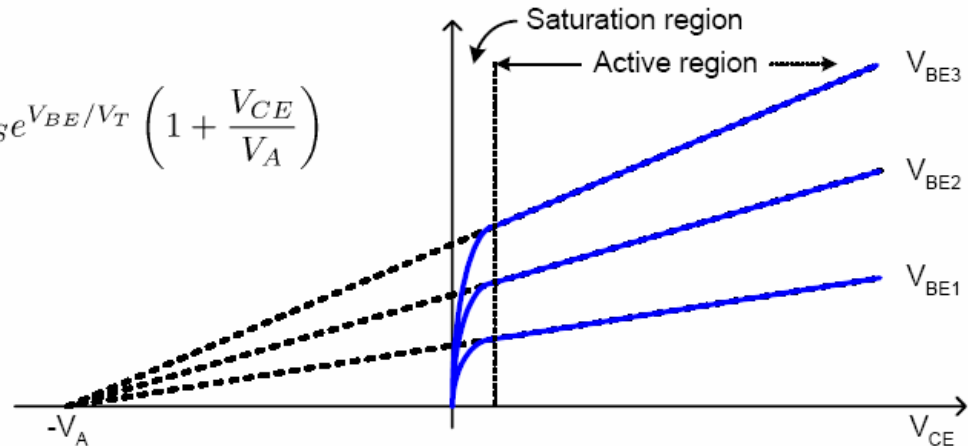
V_A is called the Early voltage and ranges from about 50 V to 100 V.



Early effect can be modeled as

$$I_C = I'_c + \frac{V_{CE}}{r_o} \quad \text{where} \quad I'_c = I_s \exp\left(\frac{eV_{BE}}{kT}\right)$$

$$r_o \equiv \left[\frac{\partial i_C}{\partial v_{CE}} \Big|_{v_{BE}=\text{constant}} \right]^{-1} \quad r_o = \frac{V_A}{I'_c}$$


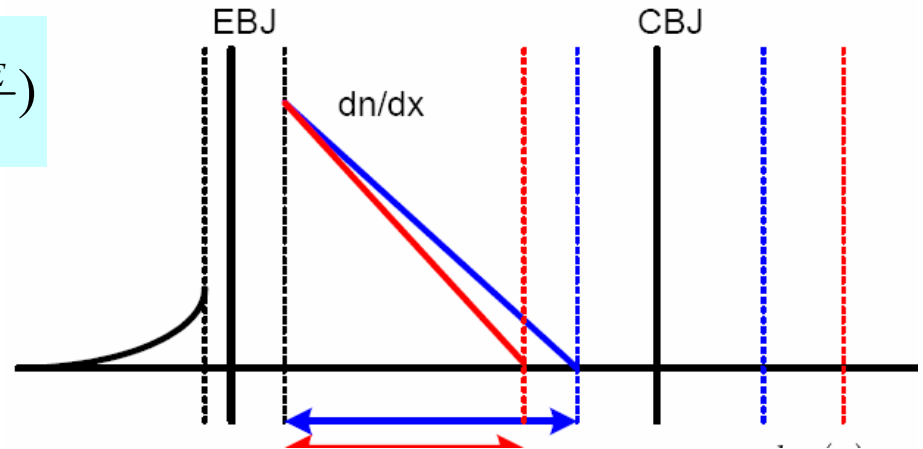


- When V_{CB} increases:
 - ❖ depletion region of CBJ widens
 - ❖ so the effective base width decreases (base-width modulation)

$$V_{CB} > V_{CB}$$



Base punch through

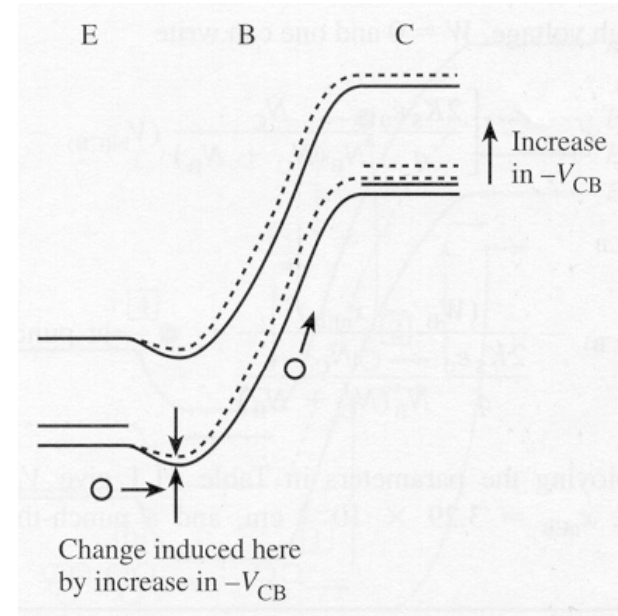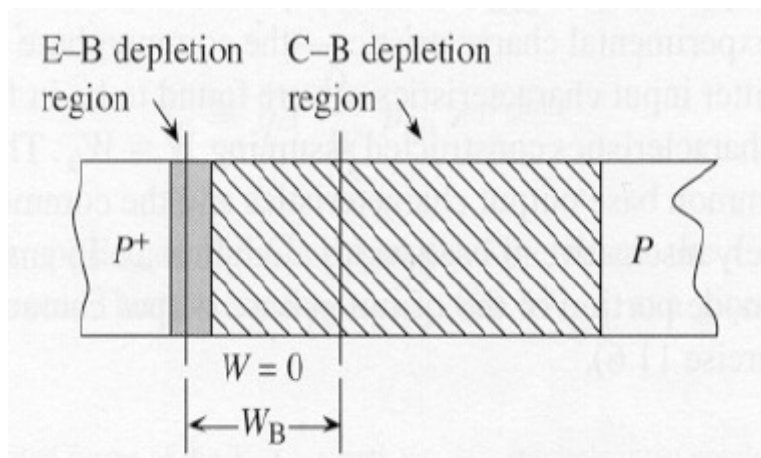➤ if reverse bias voltage of C-B junction is keep on increasing, a situation arises where E-B and C-B space charge regions touch each other, and the width of the quasi-neutral base region becomes zero, Known as base punch through.



- Any increase in V_{CB} beyond the punch-through point lowers the E-B potential barrier and allows a large injection of carriers from the emitter directly into the collector.
- If punch-through occurs, the maximum voltage (V_{CB0} or V_{CE0}) that can be applied to a BJT is limited.

DC Load Line Analysis

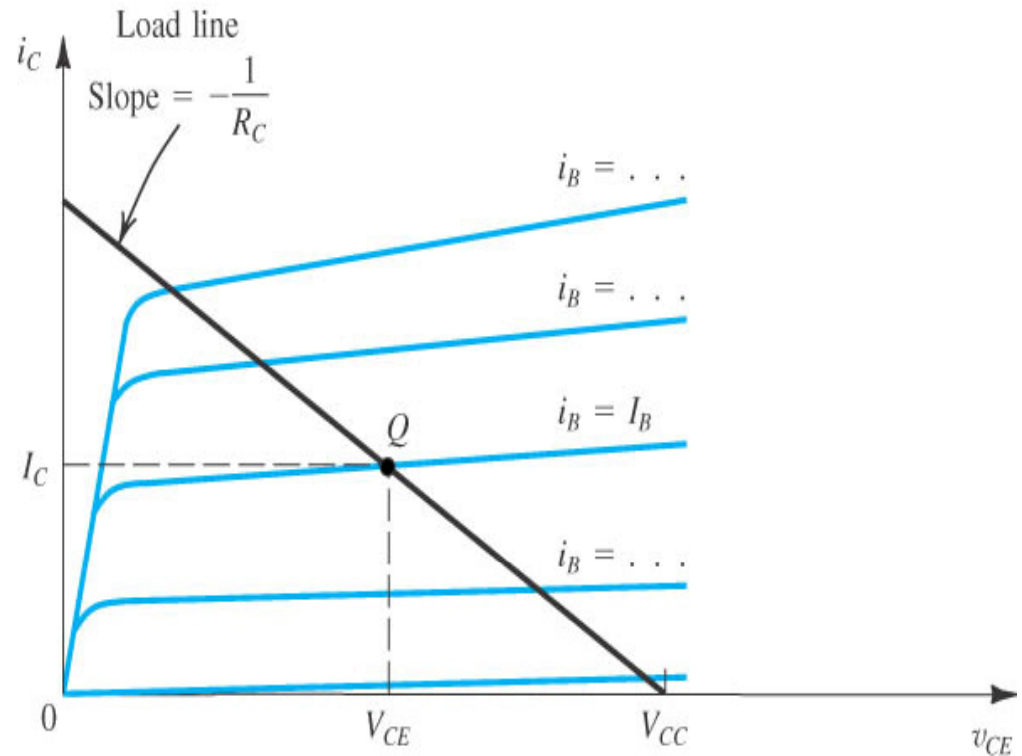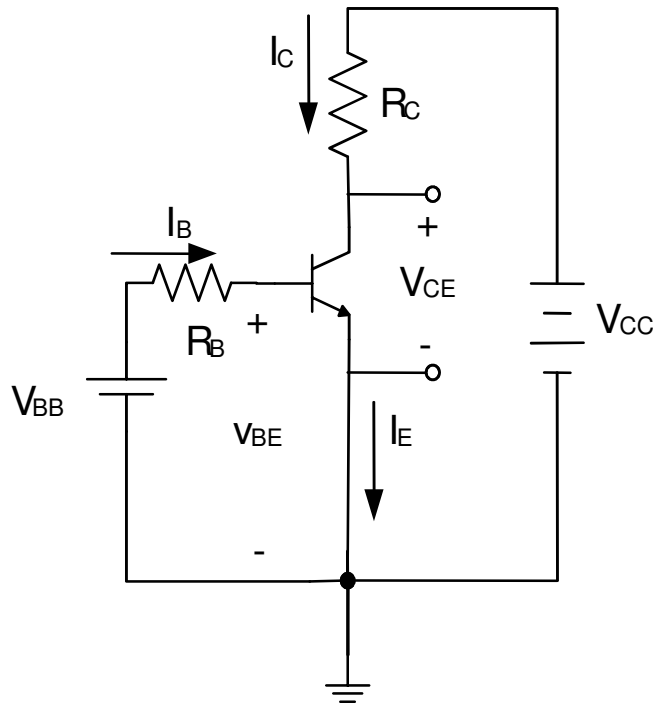

Application of KVL in output (CE)circuit:


$V_{CE} = V_{CC} - I_C R_C$; is called Load line equation.

When $I_C = 0$, $V_{CE} = V_{CC}$; When $V_{CE} = 0$, $I_C = V_{CC}/R_C$

➤ **The operating point Q (V_{CEQ} , I_{CEQ}) is determined by finding the intersection point of load line and BJT output characteristics for a particular value of base current.**

Ebers-Moll Model (Large-Signal Model)

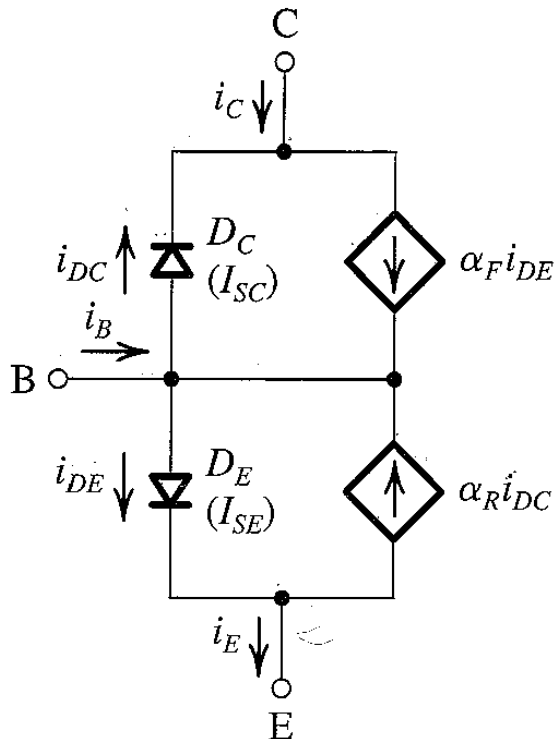- The Ebers-Moll (EM) model is a large-signal model for BJT. It relates the transistor d.c terminal currents to voltages.
- EM model is low frequency (static) model based on the fact that BJT is composed of two pn junctions – EB and CB junction.
- Therefore terminal currents of BJT can be expressed as a superposition of the currents due to the two pn junctions.




D_E : E-B junction diode
 D_C : C-B junction diode

$$I_{DE} = I_{SE} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad I_{DC} = I_{SC} \left(e^{\frac{V_{BC}}{V_T}} - 1 \right)$$

$$I_{DE} = \frac{I_C}{\alpha} = \frac{I_S}{\alpha} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) = I_{SE} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

Ebers-Moll Model (Large-Signal Model)

Reverse Active Mode

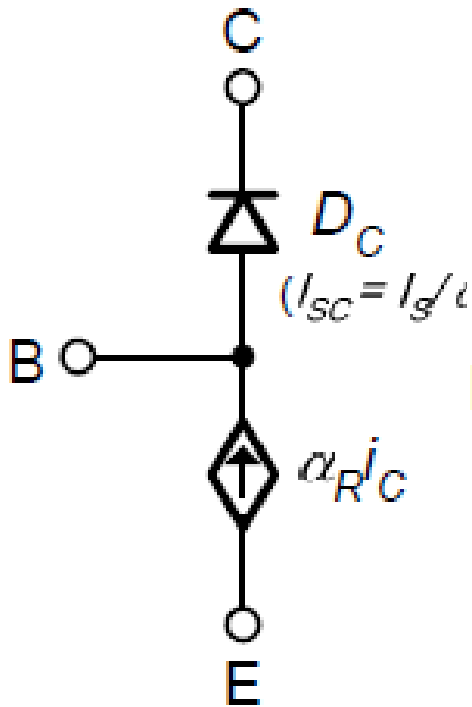


$$I_E = I_{DE} - \alpha_R I_{DC}$$

$$I_C = -I_{DC} + \alpha_F I_{DC}$$

$$I_B = (1 - \alpha_F) I_{DE} + (1 - \alpha_R) I_{DC}$$

Forward Active Mode

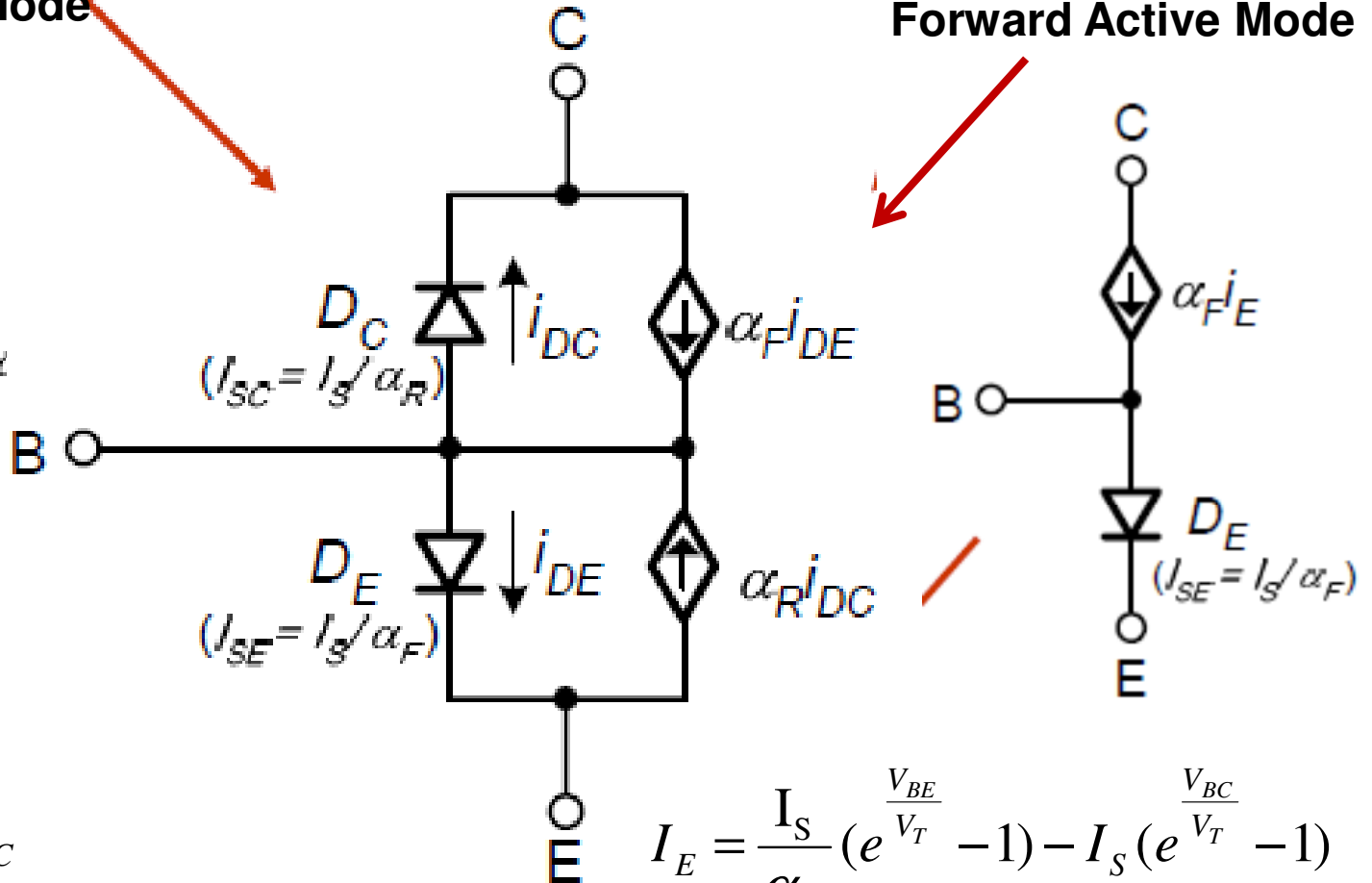


$$I_E = \frac{I_S}{\alpha_F} (e^{\frac{V_{BE}}{V_T}} - 1) - I_S (e^{\frac{V_{BC}}{V_T}} - 1)$$

$$I_C = I_S (e^{\frac{V_{BE}}{V_T}} - 1) - \frac{I_S}{\alpha_R} (e^{\frac{V_{BC}}{V_T}} - 1)$$

Ebers-Moll Model (Large-Signal Model)


BJT Forward Active Mode

BE forward-biased,
BC reverse-biased:

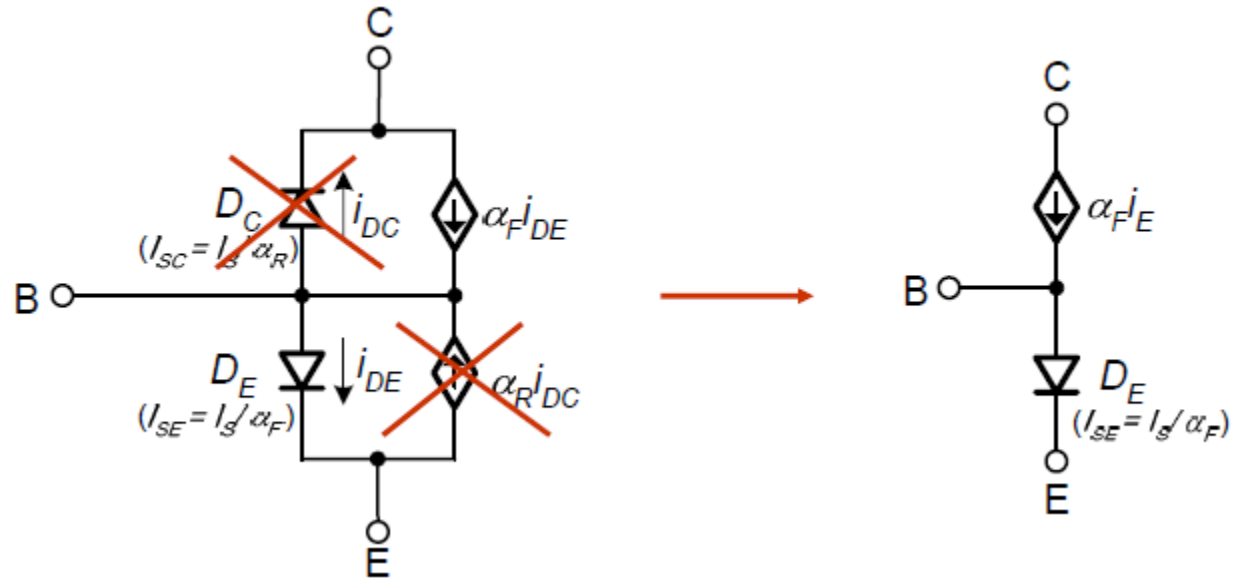

BJT Reverse Active Mode


BE reverse-biased,
BC forward-biased:

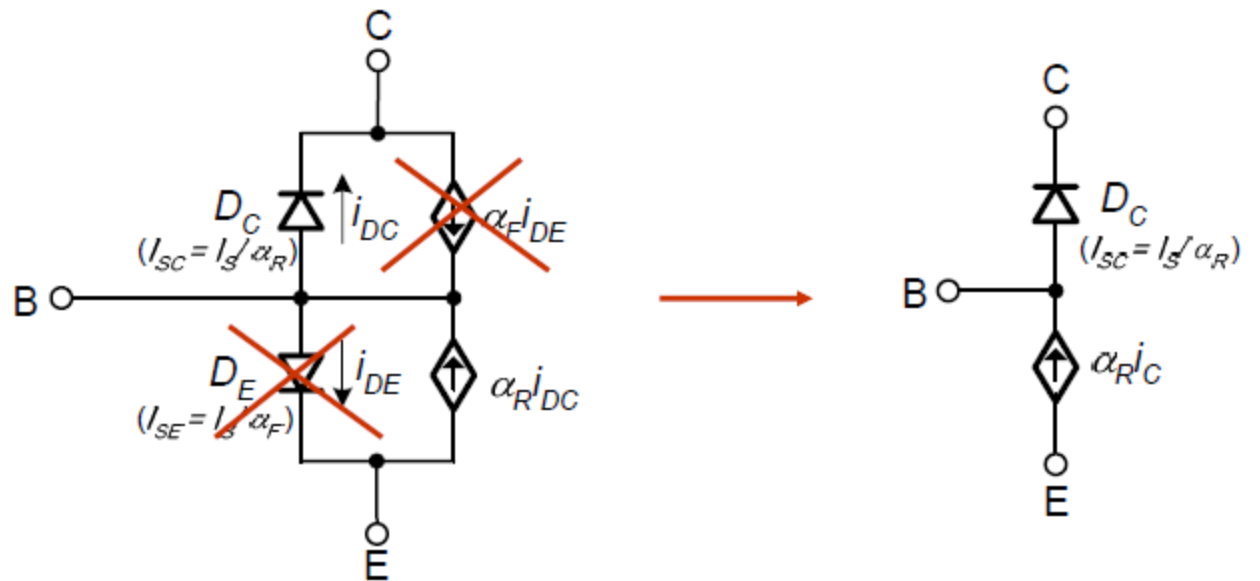

Ebers-Moll Model (Large-Signal Model)


BJT Cut-off Mode

BE reverse-biased,
BC reverse-biased:

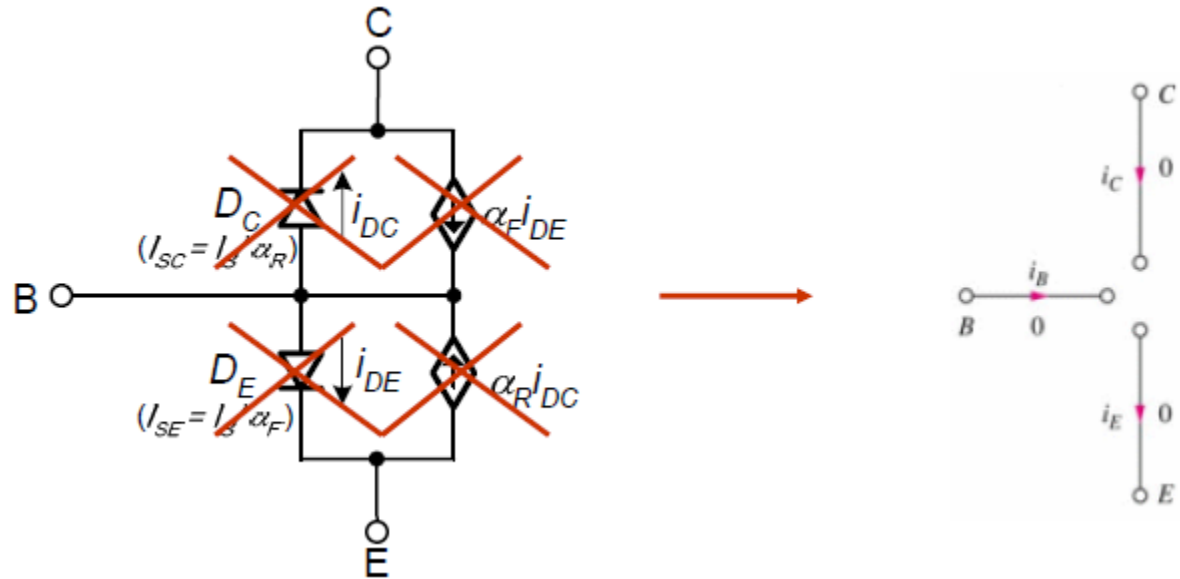


BJT Saturation Mode

BE forward-biased,
BC forward-biased:

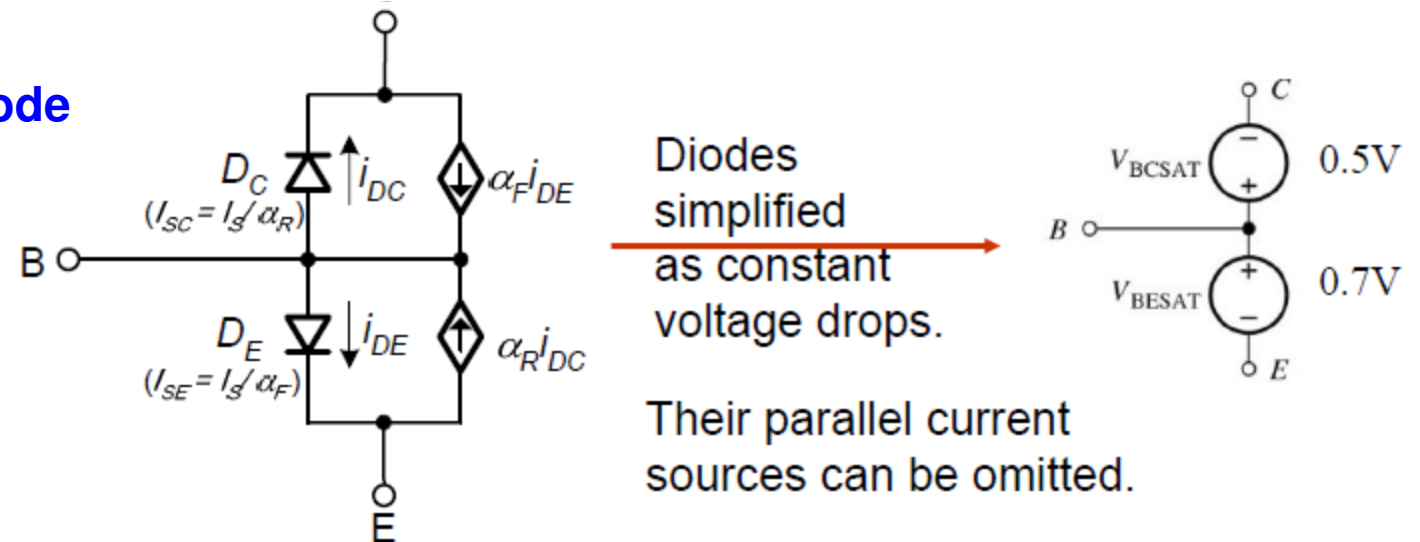

BJT with input ac signal

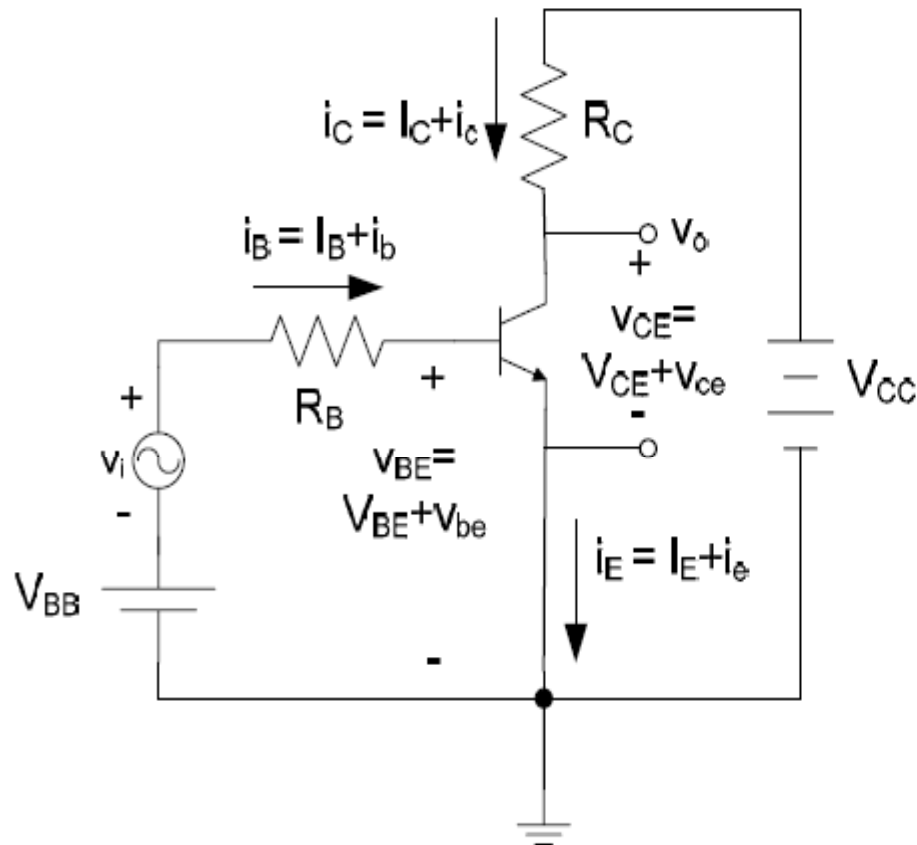

$$i_B = I_B + i_b$$

$$i_E = I_E + i_e$$

$$i_C = I_C + i_c$$

I_B, I_C, I_E - D.C. currents

i_b, i_c, i_e - A.C. currents

i_B, i_C, i_E - D.C + A.C. currents

Similarly,

V_{BE}, V_{CE} - D.C. Voltages

v_{be}, v_{ce} - A.C. Voltages

V_{BE}, V_{CE} - D.C + A.C Voltages

Biasing schemes for BJT

- **Biasing refers to the application of D.C. voltages to setup the operating point in such a way that output signal is undistorted throughout the whole operation.**
- **Also once selected properly, the Q point should not shift because of change of I_C due to**
 - (i) β variation**
 - (ii) Temperature variation**

Different biasing schemes

- (i) Fixed bias (base resistor biasing)**
- (ii) Collector base bias**
- (iii) Emitter bias**
- (iv) Voltage divider bias**

$$I_E = I_{DE} - \alpha_R I_{DC}$$

$$I_C = -I_{DC} + \alpha_F I_{DC}$$

$$I_B = (1 - \alpha_F) I_{DE} + (1 - \alpha_R) I_{DC}$$

$$I_E = \frac{I_S}{\alpha_F} (e^{\frac{V_{BE}}{V_T}} - 1) - I_S (e^{\frac{V_{BC}}{V_T}} - 1)$$

$$I_C = I_S (e^{\frac{V_{BE}}{V_T}} - 1) - \frac{I_S}{\alpha_R} (e^{\frac{V_{BC}}{V_T}} - 1)$$