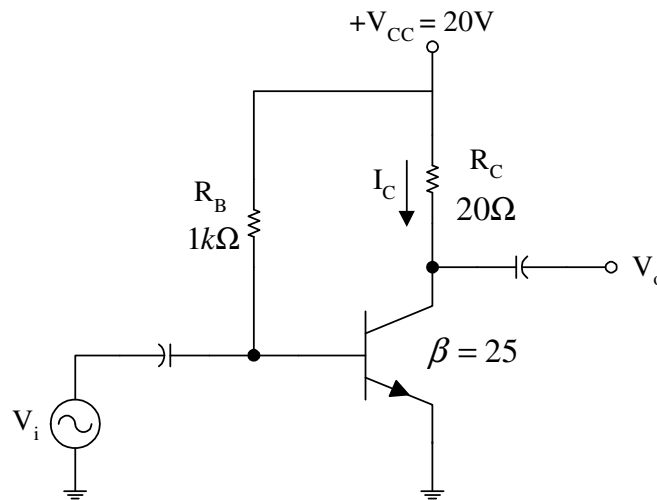



# PH-218 Analog & Digital Electronics

## Assignment-3 (Due date: 11th March 2011)

1. Calculate the input power, output power, and efficiency of the amplifier circuit for an input voltage that results in a base current of 10mA peak.



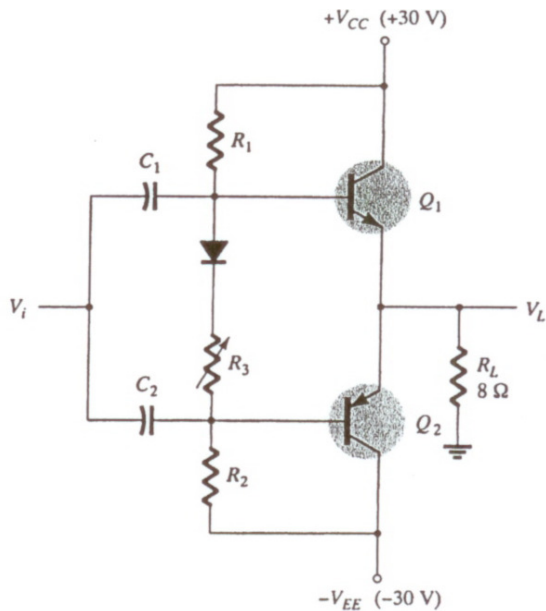2. A transformer-coupled class A amplifier drives a 16ohm speaker through a 3.87:1 transformer. Using a power supply of  $V_{CC}=36V$ , the circuit delivers 2W to the load. Calculate –
  - (a)  $P(ac)$  across transformer primary
  - (b)  $V_L(ac)$
  - (c)  $V(ac)$  at transformer primary
  - (d) The rms values of load and primary current
  - (e) Efficiency of the amplifier
3. For the class B power amplifier shown in fig. below, Calculate the following–
  - (a) Maximum  $P_o(ac)$
  - (b) Maximum  $P_i(dc)$
  - (c) Efficiency of the amplifier
  - (d) Maximum power dissipated by both the transistor



4. (a) Determine the maximum dissipation allowed for a 100W Si transistor (rated at 25°C) for a derating factor of 0.6W/°C at a case temperature of 150°C.

4(b) A 160-W Si power transistor operated with a heat sink ( $\theta_{sa} = 1.5\text{W}/^\circ\text{C}$ ) has  $\theta_{jc} = 0.5\text{W}/^\circ\text{C}$  and a mounting insulation of ( $\theta_{cs} = 0.8\text{W}/^\circ\text{C}$ ). What maximum power can be handled by the transistor at an ambient temperature of 80°C? The junction temperature should not exceed 200°C.

5. Assume collector to emitter voltage can be represented in terms of cosine harmonics as given below:  $V_{CE} = V_{CEQ} + V_0 + V_1 \cos(\omega t) + V_2 \cos(2\omega t)$   
Prove that second harmonic distortion can be expressed as

$$D_2 = \frac{\frac{1}{2}(V_{CE_{\max}} + V_{CE_{\min}}) - V_{CEQ}}{(V_{CE_{\max}} - V_{CE_{\min}})} \times 100\%$$

Calculate the second harmonic distortion for an output waveform having measured values of  $V_{CE_{\min}} = 2.4\text{ V}$ ,  $V_{CEQ} = 10\text{ V}$ , and  $V_{CE_{\max}} = 20\text{ V}$ .