

Analog & Digital Electronics

Course No: PH-218

Lec-16: Oscillator

Course Instructors:


❖ **Dr. A. P. VAJPEYI**



Department of Physics,
Indian Institute of Technology Guwahati, India

Positive Feedback

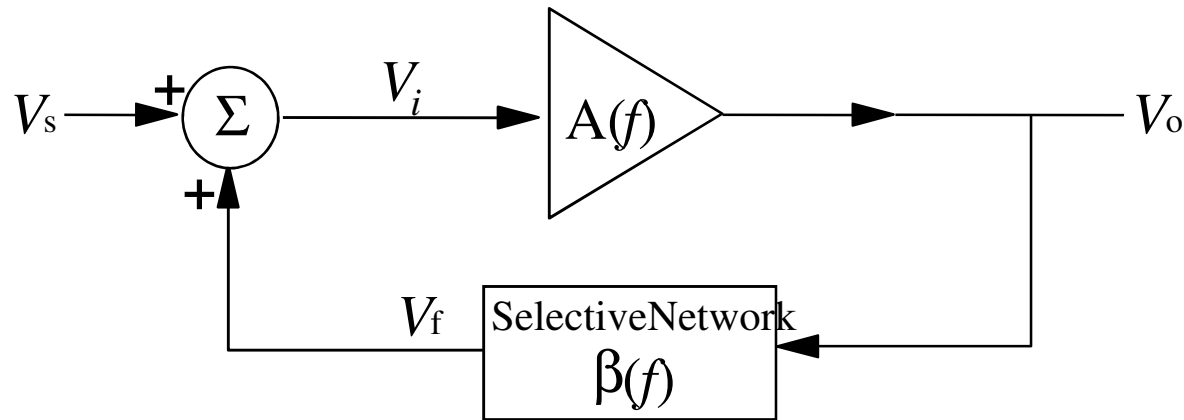- When input and feedback signal both are in same phase, It is called a positive feedback.
- Positive feedback is used in analog and digital systems.
- A primary use of +ve feedback is in the production of oscillators.



$$V_o = AV_i = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

Barkhausen Criterion: for oscillator $\beta A=1$ and +ve feedback

Oscillator Circuit

- Oscillator is an electronic circuit which converts dc signal into ac signal.
- Oscillator is basically a positive feedback amplifier with unity loop gain.
- For an inverting amplifier- feedback network provides a phase shift of 180° while for non-inverting amplifier- feedback network provides a phase shift of 0° to get positive feedback .

$$\frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

If $\beta A = 1$ then $V_o = \infty$; Very high output with zero input.


Use positive feedback through frequency-selective feedback network to ensure sustained oscillation at ω_o

Use of Oscillator Circuits

- ❖ Clock input for CPU, DSP chips ...
- ❖ Local oscillator for radio receivers, mobile receivers, etc
- ❖ As a signal generators in the lab
- ❖ Clock input for analog-digital and digital-analog converters

Oscillators

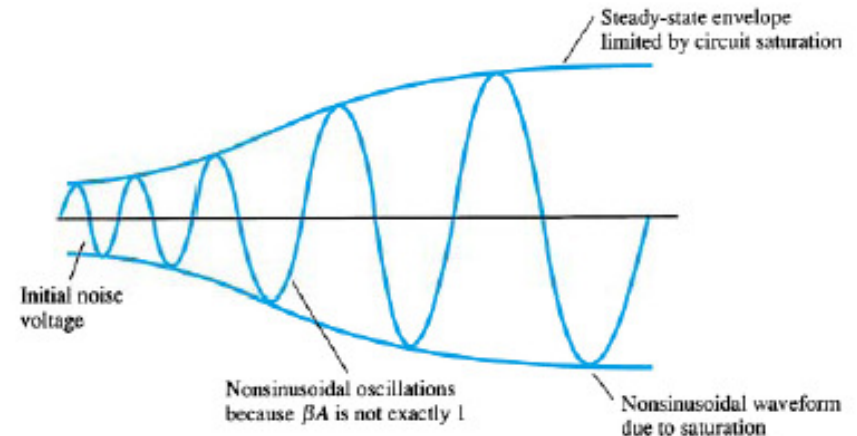- If the feedback signal is not positive and gain is less than unity, oscillations dampen out.
- If the gain is higher than unity then oscillation saturates.




Type of Oscillators

Oscillators can be categorized according to the types of feedback network used:

- RC Oscillators: Phase shift and Wien Bridge Oscillators
- LC Oscillators: Colpitt and Hartley Oscillators
- Crystal Oscillators

RC Oscillators

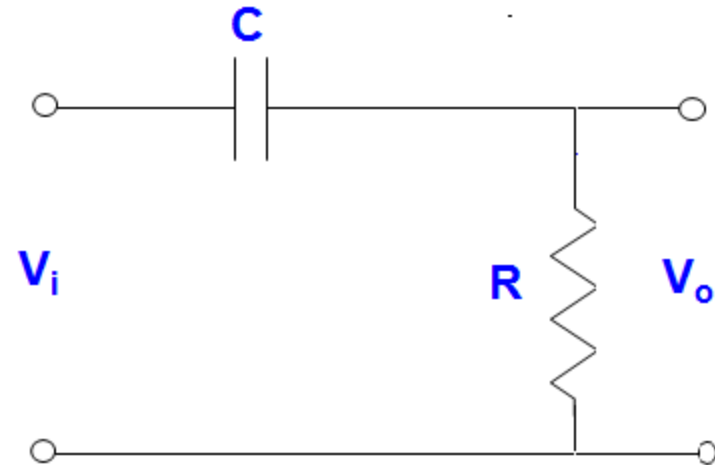
$$V_o = \left(\frac{R}{R - jX_c} \right) V_{in} \quad \text{and} \quad \phi = \tan^{-1} \left(\frac{X_c}{R} \right)$$



- $\Phi = 0^\circ$ if $X_c = 0$ and $\Phi = 90^\circ$ if $R = 0$
- However adjusting R to zero is impractical because it would lead to no voltage across R , thus in a RC circuit, phase shift is always $\leq 90^\circ$ and it is a function of frequency.
- Hence to get 180° phase shift from the feedback network, we need 3 RC circuits.
- RC oscillators build by using inverting amplifier and 3 RC circuits is known as phase shift oscillator.

RC Oscillators: Phase shift Oscillator

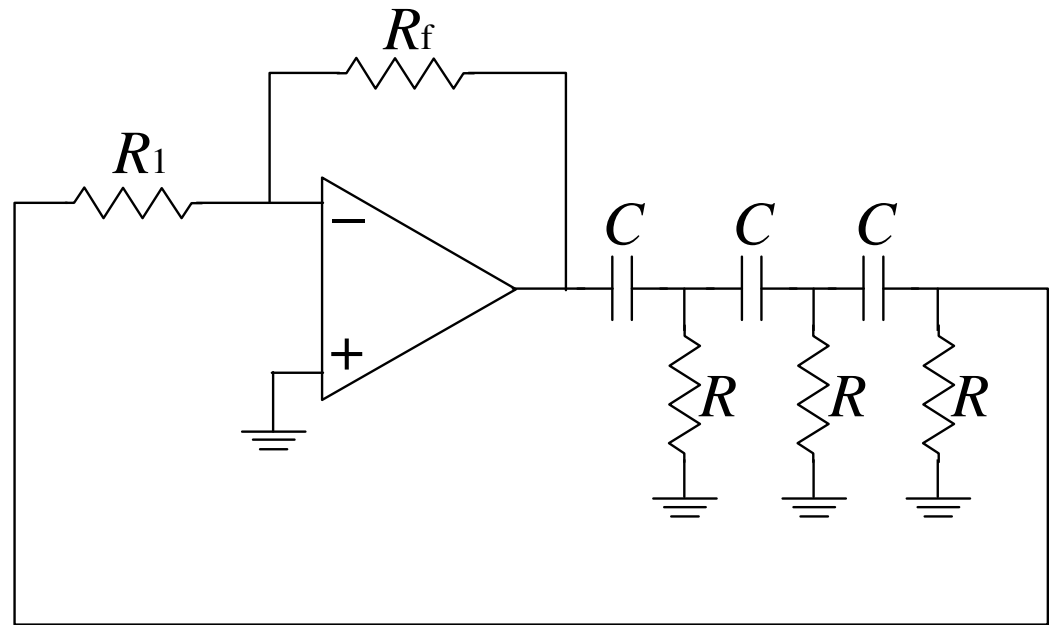- Use of an inverting amplifier.
- The additional 180° phase shift is provided by an RC ladder network.
- It can be used for very low frequencies and provides good frequency stability.



A phase shift of 180° is obtained at a frequency f , given by

$$f = \frac{1}{2\pi CR\sqrt{6}}$$

At this frequency the gain of the network is $\frac{V_o}{V_i} = -\frac{1}{29}$


RC Oscillators: Phase shift Oscillator

At node V_2

$$V_2 = V_o + I_3 X_c = V_o + \frac{I_3}{j\omega C}$$

But $I_3 = \frac{V_o}{R}$
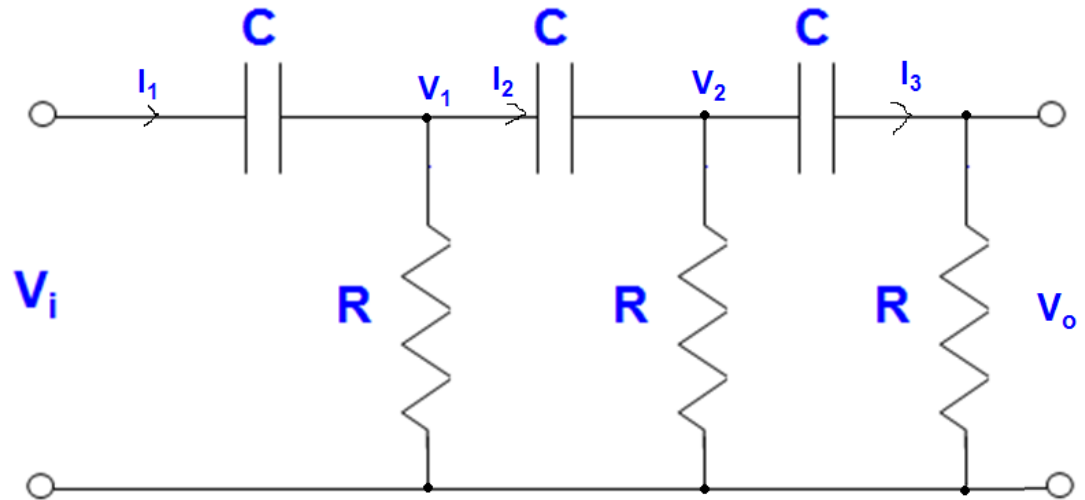
$$V_2 = V_o \left(1 + \frac{1}{j\omega CR} \right)$$



$$I_2 = I_3 + \frac{V_2}{R} = \frac{V_o}{R} + \frac{V_o}{R} \left(1 + \frac{1}{j\omega CR} \right)$$

$$I_2 = \frac{V_o}{R} \left(2 + \frac{1}{j\omega CR} \right)$$

At node V_1

$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega CR} - \frac{1}{\omega^2 C^2 R^2} \right)$$

RC Oscillators: Phase shift Oscillator

$$V_1 = V_2 + \frac{I_2}{j\omega C} = V_o \left(1 + \frac{3}{j\omega R} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$I_1 = I_2 + \frac{V_1}{R} = \frac{V_o}{R} \left(3 + \frac{4}{j\omega R} - \frac{1}{\omega^2 C^2 R^2} \right)$$

$$V_i = V_1 + \frac{I_1}{j\omega C} = V_o \left(1 + \frac{6}{j\omega R} - \frac{5}{\omega^2 C^2 R^2} - \frac{1}{j\omega^3 C^3 R^3} \right)$$

Output voltage should be real hence imaginary part equal to zero.


$$\frac{6}{j\omega R} - \frac{1}{j\omega^3 C^3 R^3} = 0$$

$$6\omega^2 C^2 R^2 = 1$$

$$\omega = \frac{1}{RC\sqrt{6}}$$

At this frequency: $V_i = -29 V_o$ therefore, $A_v = -29$

RC Oscillators: Wien Bridge Oscillator

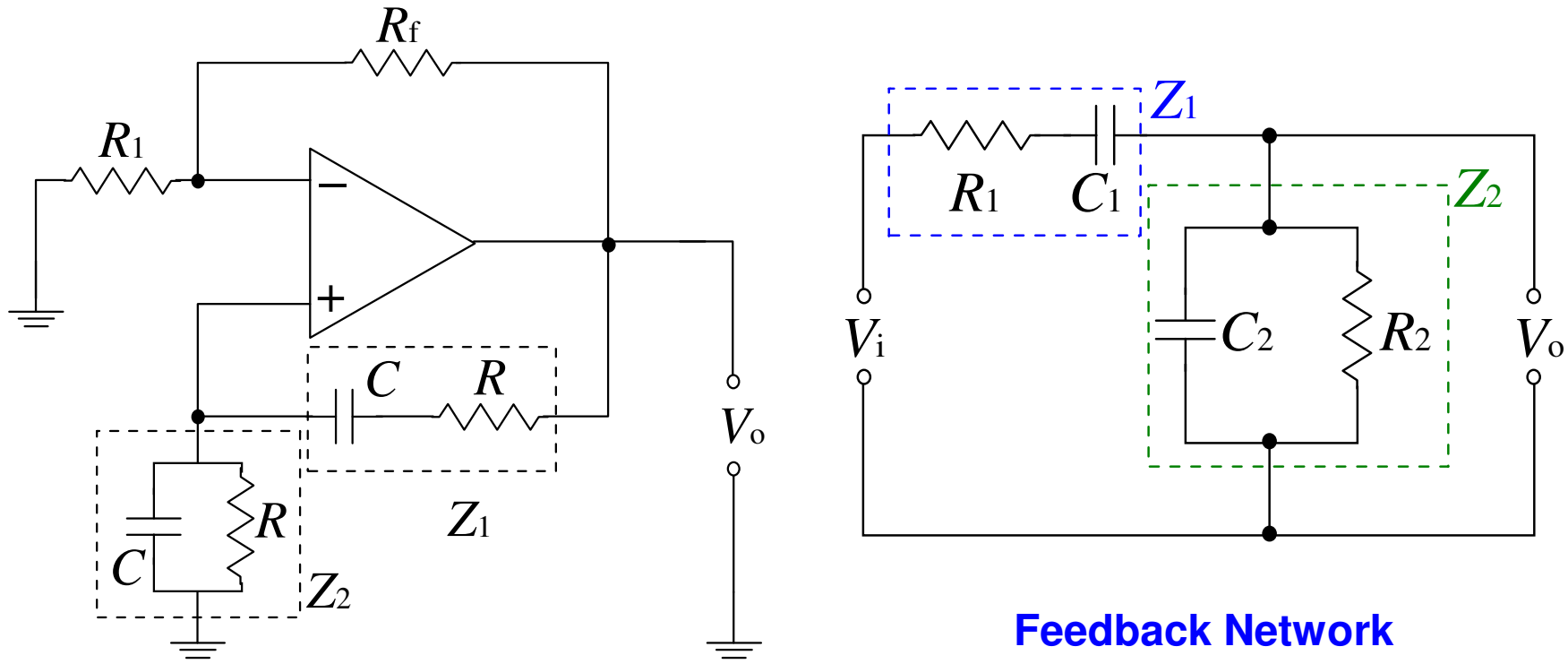


➤ Feedback network is a lead-lag circuit where R_1 , C_1 form the lag portion and R_2 , C_2 form the lead portion. Thus feedback network provides 0° phase shift.

RC Oscillators: Wien Bridge Oscillator

Let $X_{C1} = \frac{1}{\omega C_1}$ $X_{C2} = \frac{1}{\omega C_2}$ and

$$Z_1 = R_1 - jX_{C1}$$
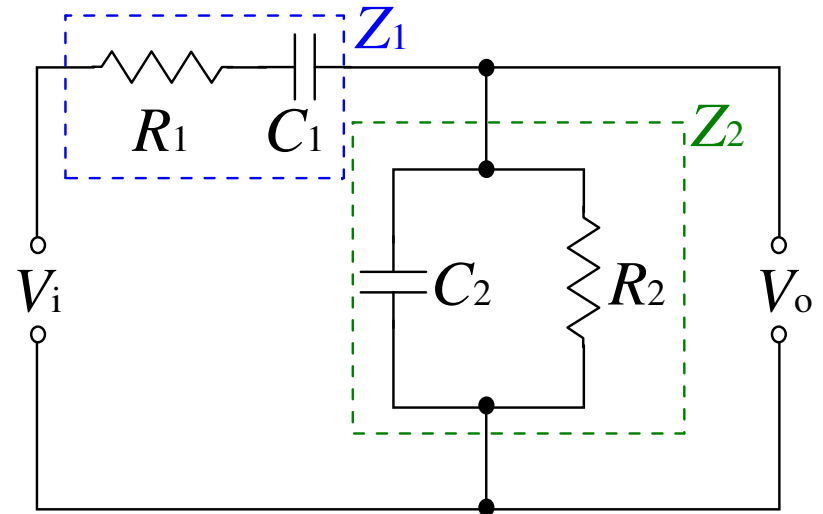
$$Z_2 = \left[\frac{1}{R_2} + \frac{1}{-jX_{C2}} \right]^{-1} = \frac{-jR_2 X_{C2}}{R_2 - jX_{C2}}$$



Therefore, the feedback factor,

$$\beta = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{(-jR_2 X_{C2} / R_2 - jX_{C2})}{(R_1 - jX_{C1}) + (-jR_2 X_{C2} / R_2 - jX_{C2})}$$

$$\beta = \frac{-jR_2 X_{C2}}{(R_1 - jX_{C1})(R_2 - jX_{C2}) - jR_2 X_{C2}}$$

$$\beta = \frac{R_2 X_{C2}}{R_1 X_{C2} + R_2 X_{C1} + R_2 X_{C2} + j(R_1 R_2 - X_{C1} X_{C2})}$$

RC Oscillators: Wien Bridge Oscillator

For **Barkhausen Criterion**, imaginary part = 0, $R_1 R_2 - X_{C1} X_{C2} = 0$

$$R_1 R_2 = \frac{1}{\omega C_1} \frac{1}{\omega C_2} \quad \boxed{\omega = 1 / \sqrt{R_1 R_2 C_1 C_2}}$$

Supposing, $R_1 = R_2 = R$ and $X_{C1} = X_{C2} = X_C$,



$$\beta = \frac{R X_C}{3 R X_C + j(R^2 - X_C^2)}$$

At this frequency: $\beta = 1 / 3$ and phase shift = 0°



Due to **Barkhausen Criterion**, gain $A_v \beta = 1$

Where A_v : Gain of the amplifier
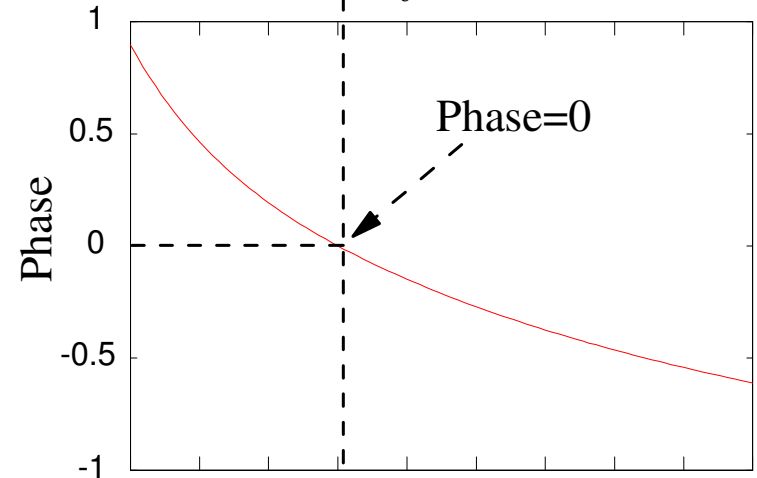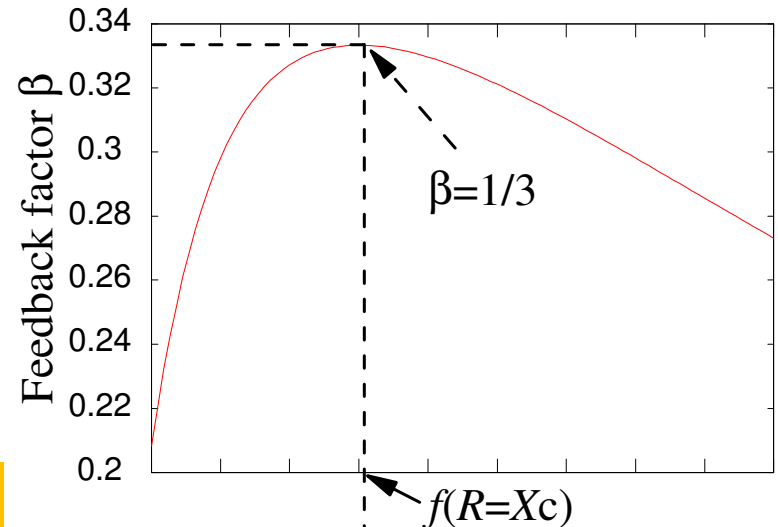
$$A_v \beta = 1 \Rightarrow A_v = 3 = 1 + \frac{R_f}{R_1} \quad \boxed{\frac{R_f}{R_1} = 2}$$



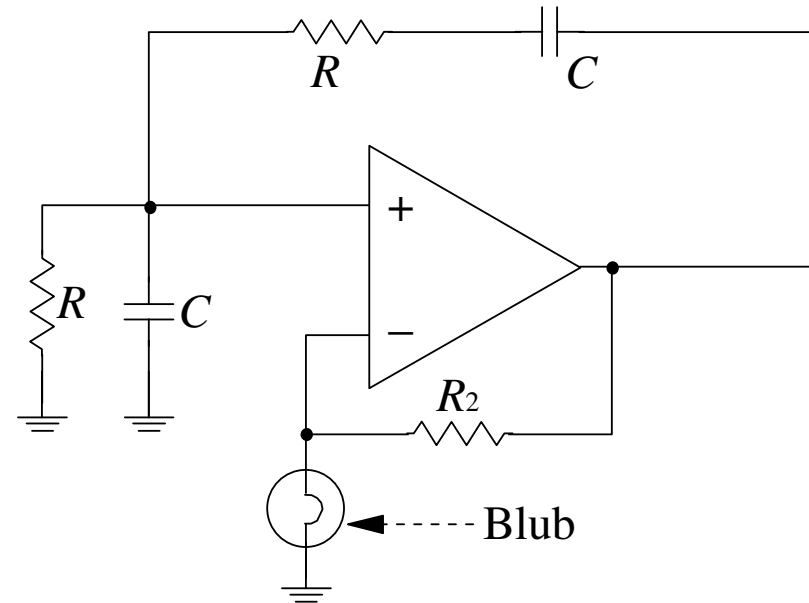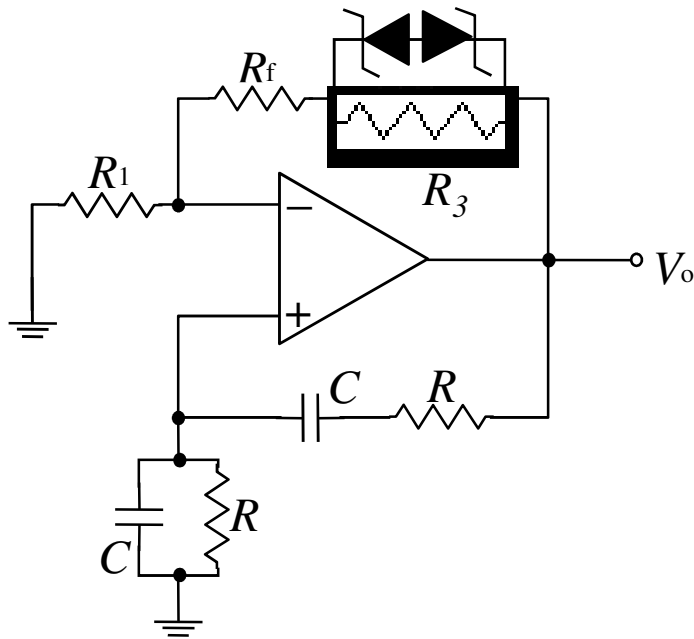Stabilization method for Wien Bridge Oscillator



When dc power is first applied, both zener diode is off.

$$A_v = 1 + \frac{R_f + R_3}{R_1} = 3 + \frac{R_3}{R_1} \quad \text{Because} \quad \frac{R_f}{R_1} = 2$$

Initially, a small +ve feedback signal develops from noise or turn-on transients. This feedback signal is amplified and continually reinforced, resulting in a buildup of the output voltage. When the output voltage reaches the zener breakdown voltage, zener diode conducts and effectively short out R3 and thus lowers the close loop voltage gain to 3.