

# Analog & Digital Electronics

Course No: PH-218

## Lec-31: Combinational Logic Modules

Course Instructor:

❖ **Dr. A. P. VAJPEYI**




Department of Physics,  
Indian Institute of Technology Guwahati, India

 
# Karnaugh map minimization method

A Karnaugh map consists of a grid of squares, each square representing one canonical minterm combination of the variables or their inverse

- Arranged with squares representing minterms which differ by only one variable to be adjacent both vertically and horizontally.
- Squares on one edge of the map are regarded as adjacent to those on the opposite edge.







# Karnaugh map minimization method

 

- The expression to be minimized should generally be in sum-of-product form.
- The function is 'mapped' onto the Karnaugh map by marking a 1 in those squares corresponding to the terms in the expression to be simplified.
- If two or more pairs are also adjacent, these can also be combined using the same theorem.
- The minimization procedure consists of recognizing multiple pairs in terms of 2, 4 or 8 cells.

# Karnaugh map minimization method

    

# Examples: Karnaugh map minimization method

**Example:** Simplify the Boolean function  $X = A'B + A'B'C' + ABC' + AB'C'$

**Solution:** First write the Boolean function in terms of canonical minterms

$$A'B = A'B(C + C') = A'BC + A'BC'$$

$$X = A'BC + A'BC' + A'B'C' + ABC' + AB'C'$$

Terms	C'	C
A'B'	1	
A'B	1	1
AB	1	
AB'	1	

$$X = C' + A'B$$


# Binary Adders: Half Adder Circuit

*Half-adder: A logic circuit for the addition of two one bit numbers is referred to as an half-adder. The circuit accepts two inputs, A and B, and generates two outputs, SUM and CARRY according to the table.*



□□ Half adder truth table

<i>Inputs</i>		<i>Outputs</i>	
<i>A</i>	<i>B</i>	<i>SUM</i>	<i>CARRY</i>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


$$\text{Sum} = A B' + A' B$$

$$\text{Carry} = A B$$


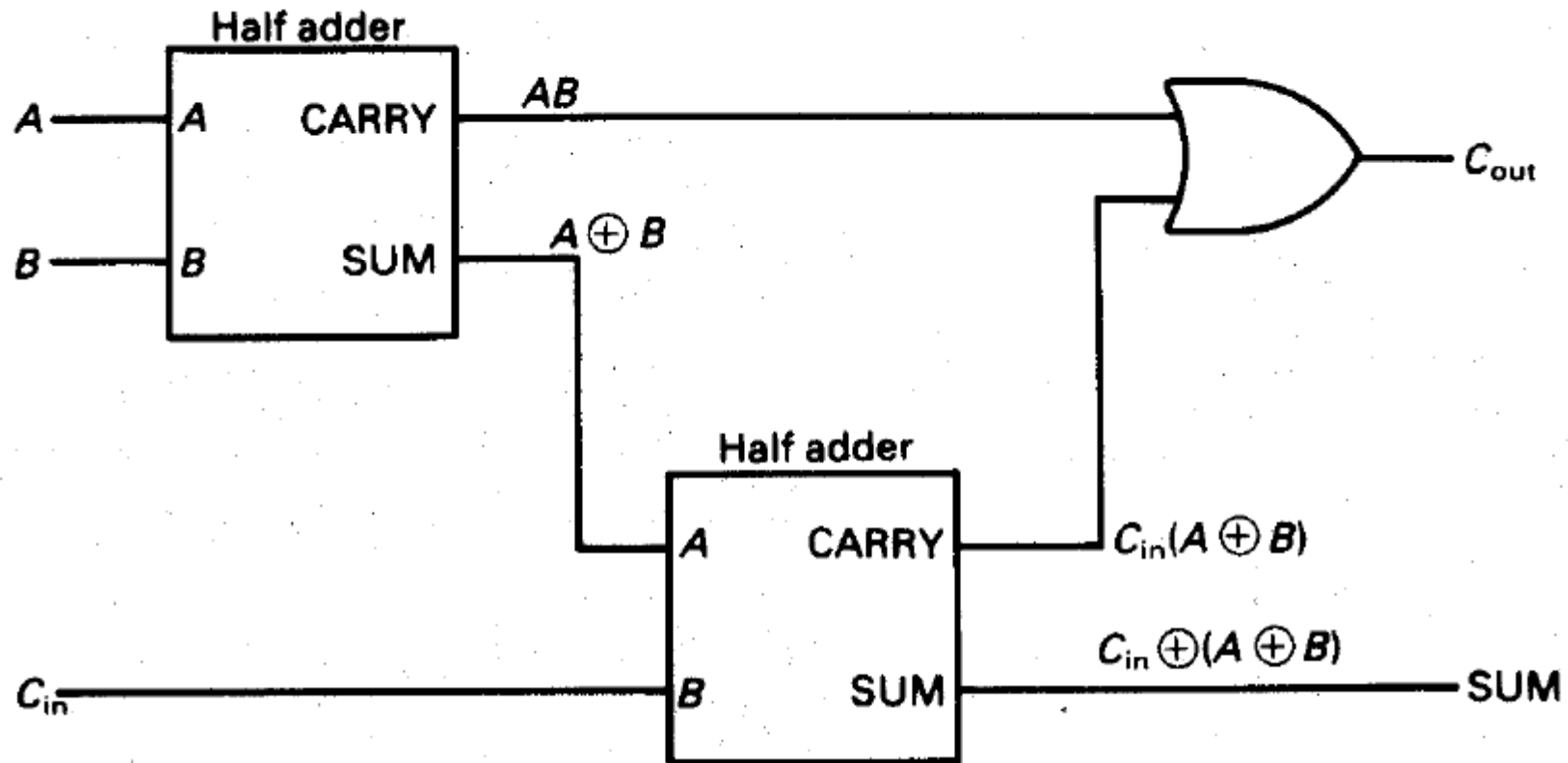
# Binary Adders: Full Adder Circuit

*Full adder: adds two binary digits A and B together with a 'carry-in' from a previous addition. A full adder has three inputs, A, B and 'CARRY-IN' ( $C_{in}$ ), and two outputs, SUM and 'CARRY OUT' ( $C_{out}$ )*



$$Sum = C_{in} \oplus (A \oplus B) \quad | \quad C_{out} = C_{in}(A \oplus B) + AB$$

# Binary Adders: Full Adder Circuit

  

$$Sum = A' B' C_{in} + A' B C_{in} + A B' C_{in} + A B C_{in}$$

$$C_{out} = A' B C_{in} + A B' C_{in} + A B C'_{in} + A B C_{in}$$

$$Sum = C_{in} \oplus (A \oplus B)$$

$$C_{out} = C_{in}(A \oplus B) + AB$$

Inputs			Outputs	
A	B	C <sub>in</sub>	SUM	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Magnitude Comparator



A magnitude comparator is a combinational circuit that compares two numbers  $A$  &  $B$  to determine whether:  $A > B$ , or  $A = B$ , or  $A < B$

Consider two numbers,  $A$  and  $B$ , with four digits each;  $A = A_3 A_2 A_1 A_0$  and  $B = B_3 B_2 B_1 B_0$

An exclusive NOR gate is the easiest way to compare the equality of the bits.

## X-NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

  

Inputs: First  $n$ -bit number  $A$   
Second  $n$ -bit number  $B$

Outputs: 3 output signals (GT, EQ, LT), where:


1.  $GT = 1$  IFF  $A > B$
2.  $EQ = 1$  IFF  $A = B$
3.  $LT = 1$  IFF  $A < B$

**Note: Exactly One of these 3 outputs equals 1, while the other 2 outputs are 0's**
 
# Equality Comparator

The equality relation of each pair of bits can be expressed logically with an equivalence function:  $x_i = A_i B_i + A_i' B_i'$ ;  $i = 0, 1, 2, 3$

where  $x_i = 1$  only if the pair of bits in position  $i$  are equal, i.e., if both are 1's or both are 0's




4-Bit Equality Comparator
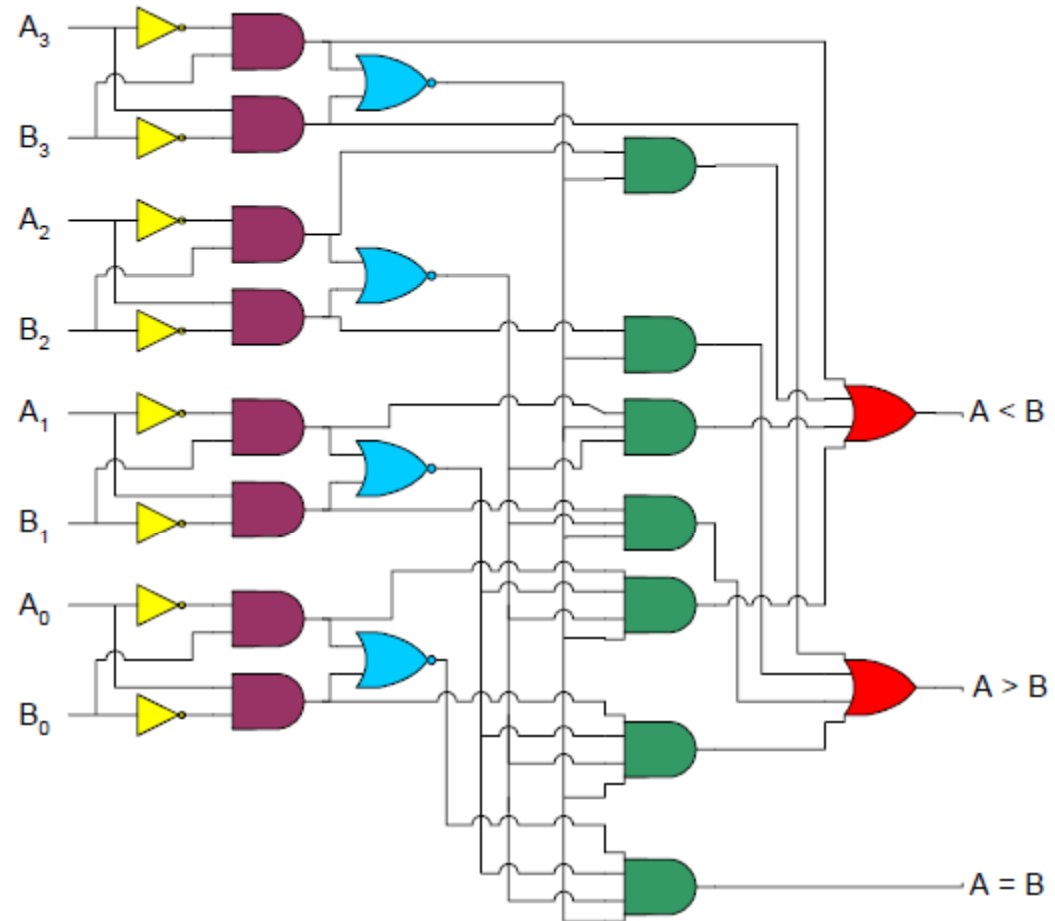
# Magnitude Comparator

➤ To determine if *A is greater than or less than B*, we inspect the relative magnitudes of pairs of significant digits starting from the most significant position.

➤ The sequential comparison can be expressed logically by the following two Boolean functions



$$GT = A_3 B'_3 + X_3 A_2 B'_2 + X_3 X_2 A_1 B'_1 + X_3 X_2 X_1 A_0 B'_0$$

$$LT = A'_3 B_3 + X_3 A'_2 B_2 + X_3 X_2 A'_1 B_1 + X_3 X_2 X_1 A'_0 B_0$$

# Magnitude Comparator

## Design of the GT output (A > B) 4-bit magnitude comparator

If  $A_3 > B_3$ , then  $A > B$  (GT=1) irrespective of the relative values of the other bits of A & B. Consider, for example,  $A = 1000$  and  $B = 0111$  where  $A > B$ .

This can be stated as GT=1 if  **$A_3 B'_3 = 1$**

If  $A_3 = B_3$  ( $X_3 = 1$ ), we compare the next significant pair of bits ( $A_2$  &  $B_2$ ).

If  $A_2 > B_2$  then  $A > B$  (GT=1) irrespective of the relative values of the other bits of A & B. Consider, for example,  $A = 0100$  and  $B = 0011$  where  $A > B$ . This can

be stated as GT=1 if  **$X_3 A_2 B'_2 = 1$**

If  $A_3 = B_3$  ( $X_3 = 1$ ) and  $A_2 = B_2$  ( $X_2 = 1$ ), we compare the next significant pair of bits ( $A_1$  &  $B_1$ ). If  $A_1 > B_1$  then  $A > B$  (GT=1) irrespective of the relative values of the remaining bits  $A_0$  &  $B_0$ . Consider, for example,  $A = 0010$  and  $B = 0001$

where  $A > B$ . This can be stated as GT=1 if  **$X_3 X_2 A_1 B'_1 = 1$**

If  $A_3 = B_3$  ( $X_3 = 1$ ) and  $A_2 = B_2$  ( $X_2 = 1$ ) and  $A_1 = B_1$  ( $X_1 = 1$ ), we compare the next pair of bits ( $A_0$  &  $B_0$ ). If  $A_0 > B_0$  then  $A > B$  (GT=1). This can be stated as


GT=1 if  **$X_3 X_2 X_1 A_0 B'_0 = 1$**

To summarize, GT = 1 (A > B) IFF:

$$\text{GT} = A_3 B'_3 + X_3 A_2 B'_2 + X_3 X_2 A_1 B'_1 + X_3 X_2 X_1 A_0 B'_0$$

# Magnitude Comparator

Find A\_GT\_B

 

If A = 1001 and  
B = 0111

is A > B?  
Why?

Because A<sub>3</sub> > B<sub>3</sub>  
i.e. A<sub>3</sub> & !B<sub>3</sub> = 1

Therefore, one term in the  
logic equation for A\_GT\_B is A<sub>3</sub> & !B<sub>3</sub>

$$A\_GT\_B = A_3 \& !B_3 + \dots$$

If A = 1101 and B = 1011; is A > B? Why?

Because A<sub>3</sub> = B<sub>3</sub> and A<sub>2</sub> > B<sub>2</sub>  
i.e. C<sub>3</sub> = 1 and A<sub>2</sub> & !B<sub>2</sub> = 1

Therefore, the next term in the logic  
equation for A\_GT\_B is C<sub>3</sub> & A<sub>2</sub> & !B<sub>2</sub>

$$A\_GT\_B = A_3 \& !B_3 + C_3 \& A_2 \& !B_2 + \dots$$

If A = 1010 and B = 1001; is A > B? Why?

Because A<sub>3</sub> = B<sub>3</sub> and A<sub>2</sub> = B<sub>2</sub> and A<sub>1</sub> > B<sub>1</sub>  
i.e. C<sub>3</sub> = 1 and C<sub>2</sub> = 1 and A<sub>1</sub> & !B<sub>1</sub> = 1

$$A\_GT\_B = A_3 \& !B_3 + C_3 \& A_2 \& !B_2 + C_3 \& C_2 \& A_1 \& !B_1 + \dots$$


If A = 1011 and B = 1010; is A > B? Why?

Because A<sub>3</sub> = B<sub>3</sub> and A<sub>2</sub> = B<sub>2</sub> and A<sub>1</sub> = B<sub>1</sub>  
and A<sub>0</sub> > B<sub>0</sub> i.e. C<sub>3</sub> = 1 and C<sub>2</sub> = 1 and C<sub>1</sub> = 1 and A<sub>0</sub> & !B<sub>0</sub> = 1
 
# Multiplexers / Data Selectors

A data selector or multiplexer is a logic circuit which allows one of several data inputs to be selected and fed to a single output.


By applying control signals, any one of the input can be steered to the output.



(a) Logic diagram

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

 

(c) Block diagram

# Multiplexers / Data Selectors

**A general procedure for implementing any Boolean function of  $n$  variables with a  $2^{n-1}$  to 1 multiplexer**

- Express the function in its sum of minterms
- List the inputs of the multiplexer and under them list all the minterms in two rows
- In the first row,  $A$  is complemented
- In the second row,  $A$  is uncomplemented
- Circle all the minterms of the function
  - » If the two minterms in a column are not circled, apply 0 to the corresponding multiplexer input
  - » If the two minterms are circled, apply 1 to the corresponding multiplexer input
  - » If the bottom minterm is circled and the top is not circled, apply  $A$  to the corresponding multiplexer input
  - » If the top minterm is circled and the bottom is not circled, apply  $A'$  to the corresponding multiplexer input


**For a  $n:1$  multiplexer, number of control signals  $m$  is given by:  $n = 2^m$**

# Multiplexers / Data Selectors

Implement the function of three variables:  $F(A,B,C) = \Sigma(1, 3, 5, 6)$   
with a 4-to-1 multiplexer

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

(b) Truth table

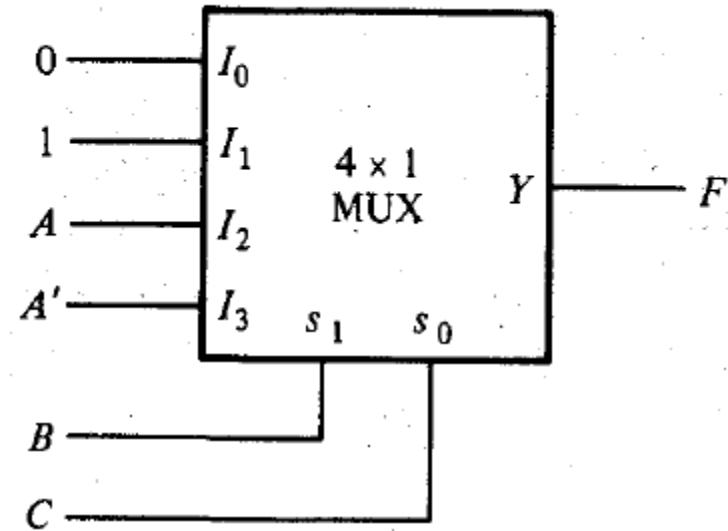

(a) Multiplexer implementation

	$I_0$	$I_1$	$I_2$	$I_3$
$A'$	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	$A'$



# Demultiplexer

A demultiplexer is a circuit that receives information on a single line and transmits this information on one of  $2^n$  possible output lines

