

# Analog & Digital Electronics

Course No: PH-218

Lec-9: BJT Single Stage CE Amplifier

Course Instructors:

❖ **Dr. A. P. VAJPEYI**



Department of Physics,  
Indian Institute of Technology Guwahati, India

# Amplifier

An amplifier is a circuit which magnify (amplify) the input signal.



## Characteristics of an amplifiers

1. Gain ( $A$ ) =  $V_{out} / V_{i_n}$  - Large
2. Input Resistance ( $R_{in}$ ) - Large
3. Output Resistance ( $R_{out}$ ) - Small
4. Bandwidth (Frequency response) - Large


## Families of amplifiers

BJT Mode	Input	Output
Common-Emitter	Base	Collector
Common-Base	Emitter	Collector
Common-Collector	Base	Emitter

# Common emitter BJT Amplifier

The higher the freq., the lower the capacitor impedance.

$$X_C = \frac{1}{2\pi fC}$$

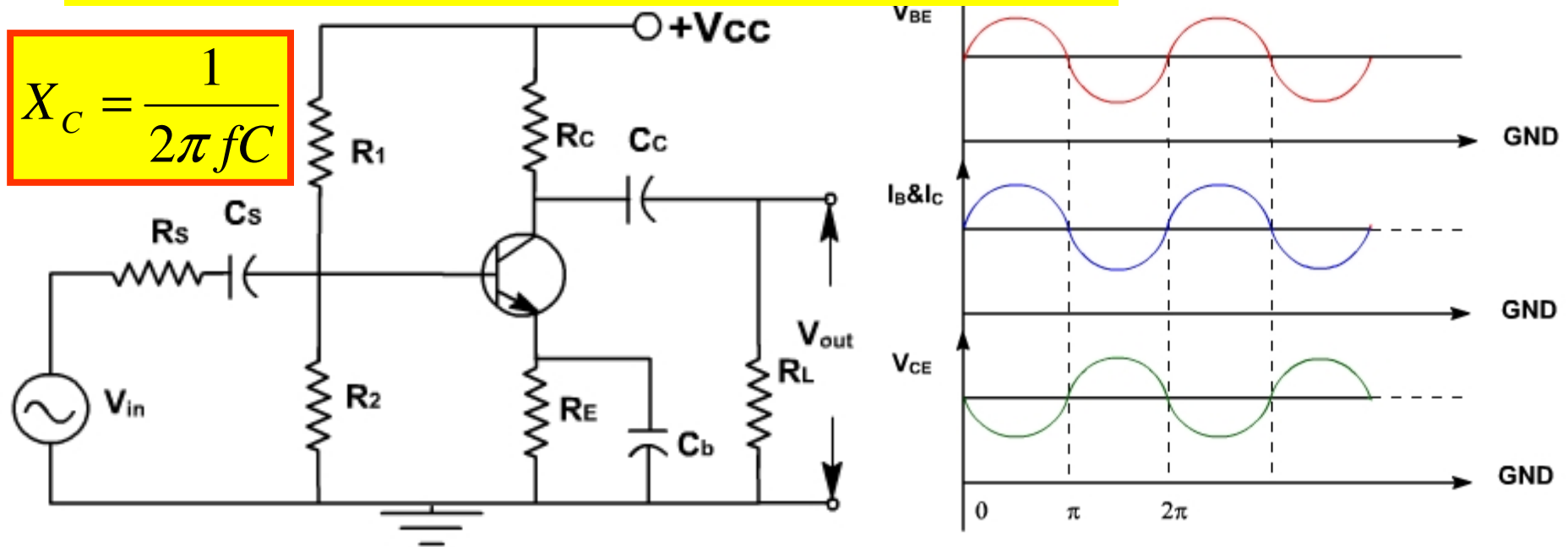

- The coupling capacitor ( $C_s$  and  $C_C$ ) is used to pass the ac input signal and block the dc voltage from the preceding circuit.
- This prevents dc in the circuitry on the left of the coupling capacitor from affecting the bias.
- The emitter bypass capacitor ( $C_b$ ) is used to bypass the  $R_E$  and short circuits the ac signal through  $C_b$  since voltage gain decreases because of presence of  $R_E$


## Common emitter BJT Amplifier

- Transistor is biased with a Q point near the middle of a dc load line.
- When ac source is coupled to the base. This produces fluctuations in the base current and hence in the collector current of the same shape and frequency.
- During positive half cycle, base current increase, causing the collector current to increase. This produces a large voltage drop across the collector resistor; therefore, the voltage output decreases and negative half cycle of output voltage is obtained.
- Conversely, on the negative half cycle of input voltage less collector current flows and the voltage drop across the collector resistor decreases, and hence collector voltage increases we get the positive half cycle of output voltage.



**The ac output voltage is inverted with respect to the ac input voltage, meaning it is 180° out of phase with input.**

# AC Load Line for Common emitter BJT Amplifier

## DC Equivalent ckt

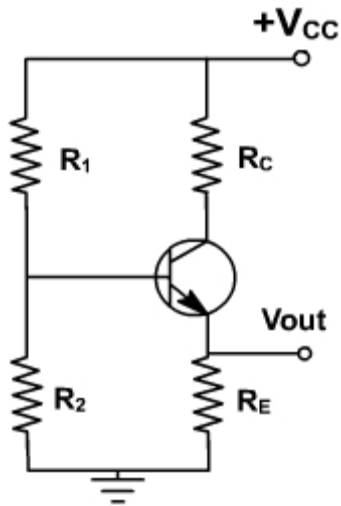

## AC Equivalent ckt

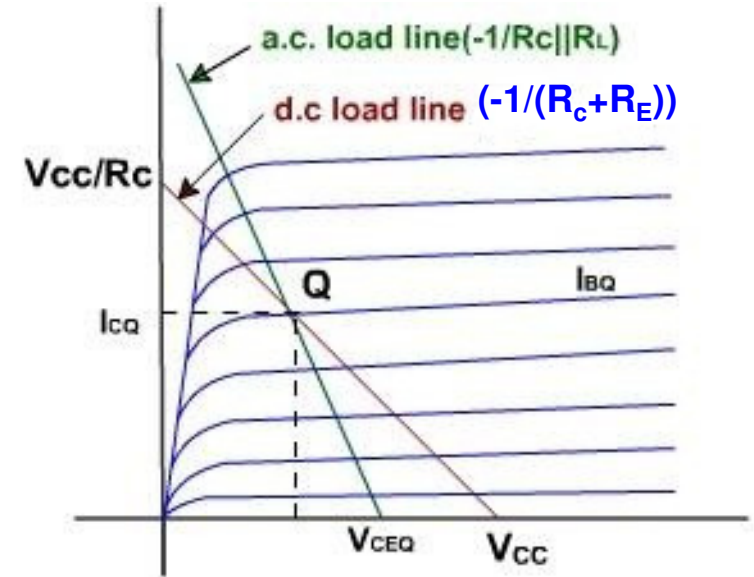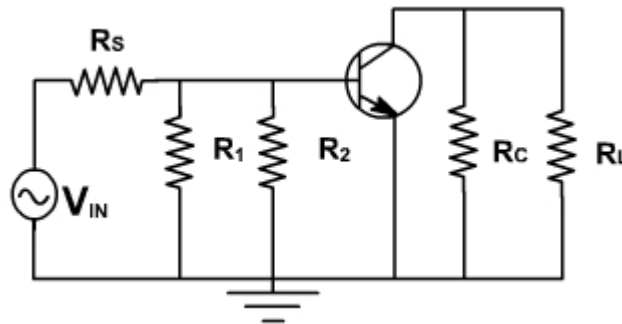

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

and 
$$I_C = -\frac{V_{CE}}{R_C + R_E} + \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE} = 0, \quad I_C = \frac{V_{CC}}{R_C + R_E}$$

and 
$$I_C = 0, \quad V_{CE} = V_{CC}$$

When considering the ac equivalent circuit, the output impedance becomes  $R_C \parallel R_L$  which is less than  $(R_C + R_E)$ . In the absence of ac signal, this load line passes through Q point. Therefore ac load line is a line of slope  $(-1 / (R_C \parallel R_L))$  passing through Q point. Under this condition, Q-point is not in the middle of load line, therefore Q-point is selected slightly upward, means slightly shifted to saturation side.

# Performance Parameters of a CE BJT Amplifier

Input Impedance ( $Z_{in}$ )


$$Z_i = [R_1 \parallel R_2 \parallel (\beta + 1)r_e]$$

Output Impedance ( $Z_{out}$ )

$$Z_{out} = (R_C \parallel r_o)$$


Voltage Gain ( $A_v$ )
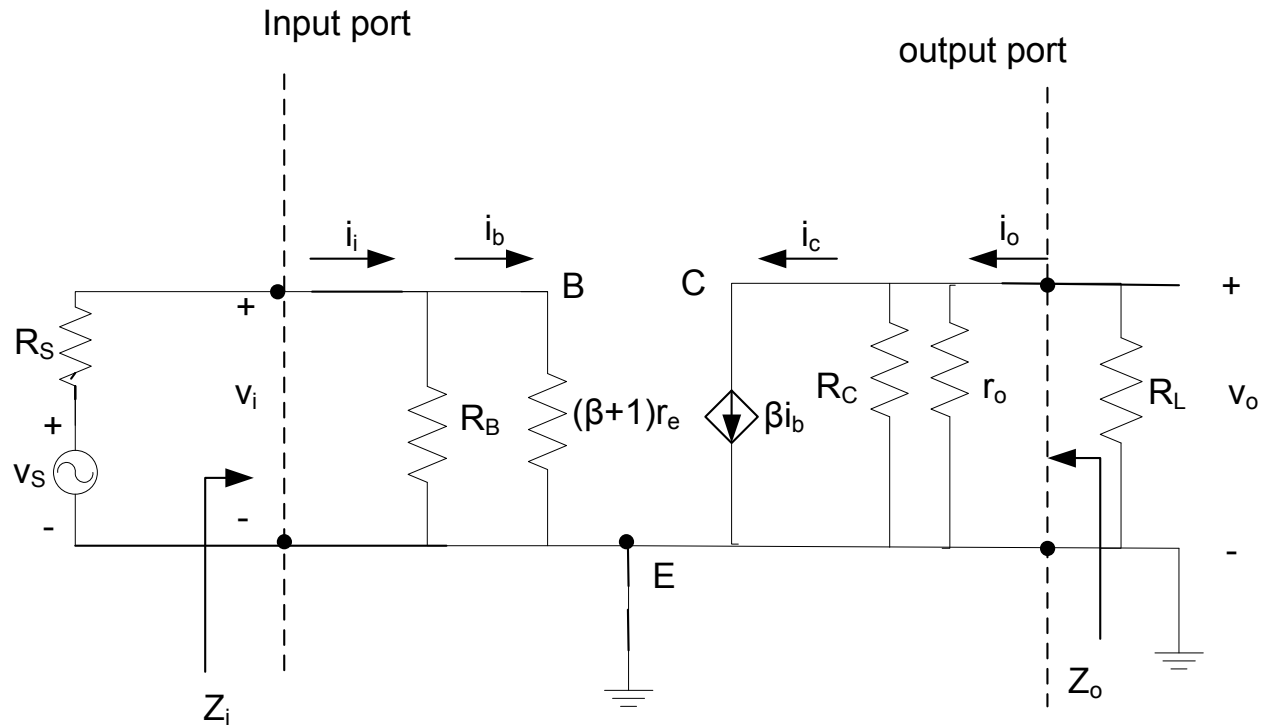
$$A_v = \frac{-\beta R_C \parallel r_o \parallel R_L}{(\beta + 1)r_e} \approx \frac{-R_C \parallel r_o \parallel R_L}{r_e}$$


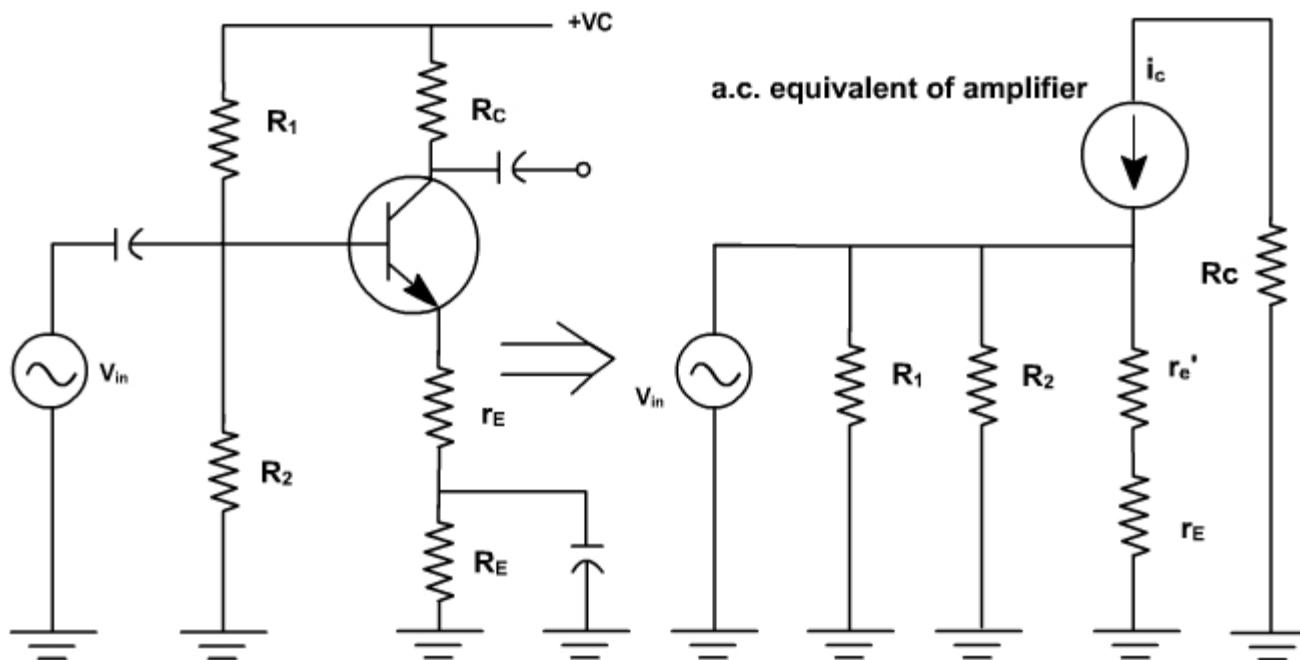
# Swamped CE BJT Amplifier

**Swamped amplifier** is an amplifier that uses a partially bypassed emitter resistance to increase ac emitter resistance. Also referred to as a **gain-stabilized amplifier**.



$$A_v = -\frac{R_c}{(r_E + r_e')}$$


$$r_e' = \frac{V_T}{I_E}$$

$r_E$  provides negative feedback

➤ Any change in  $r_e'$  will change the voltage gain in CE amplifier.

➤ To make it stable, a resistance  $r_E$  is inserted in series with the emitter and therefore emitter is no longer ac grounded.

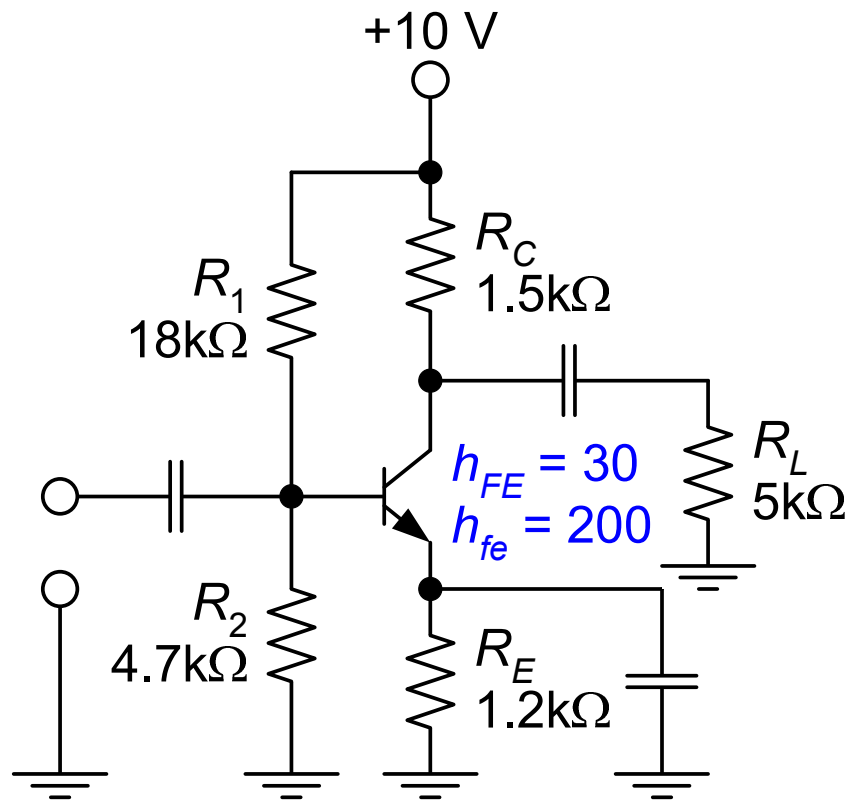Calculate the voltage gain of the amplifier.



$$\begin{aligned}
 V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\
 &= 10\text{V} - 1.005\text{mA} \times 1.5\text{k}\Omega - 1.038\text{mA} \times 1.2\text{k}\Omega \\
 &= 7.247\text{V} \quad (\text{active})
 \end{aligned}$$

$$\begin{aligned}
 V_{th} &= V_{CC} \frac{R_2}{R_1 + R_2} = 10\text{V} \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} \\
 &= 2.070\text{V} \\
 R_{th} &= R_1 \parallel R_2 = 4.7\text{k}\Omega \parallel 18\text{k}\Omega \\
 &= 3.727\text{k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 I_B &= \frac{V_{th} - V_{BE}}{R_{th} + (h_{FE} + 1)R_E} = \frac{2.070\text{V} - 0.7\text{V}}{3.727\text{k}\Omega + 31 \times 1.2\text{k}\Omega} \\
 &= 33.49\mu\text{A}
 \end{aligned}$$


$$\begin{aligned}
 I_C &= h_{FE} I_B = 30 \times 33.49\mu\text{A} = 1.005\text{mA} \\
 I_E &= (h_{FE} + 1) I_B = 31 \times 33.49\mu\text{A} = 1.038\text{mA}
 \end{aligned}$$

$$\begin{aligned}
 r'_e &= \frac{25\text{mV}}{I_E} = \frac{25\text{mV}}{1.038\text{mA}} = 24.08\Omega \\
 r_C &= R_C \parallel R_L = 1.5\text{k}\Omega \parallel 5\text{k}\Omega = 1.154\text{k}\Omega
 \end{aligned}$$

$$A_v \cong -\frac{r_C}{r'_e} = -\frac{1.154\text{k}\Omega}{24.08\Omega} = -47.91$$




# The Effects of Loading

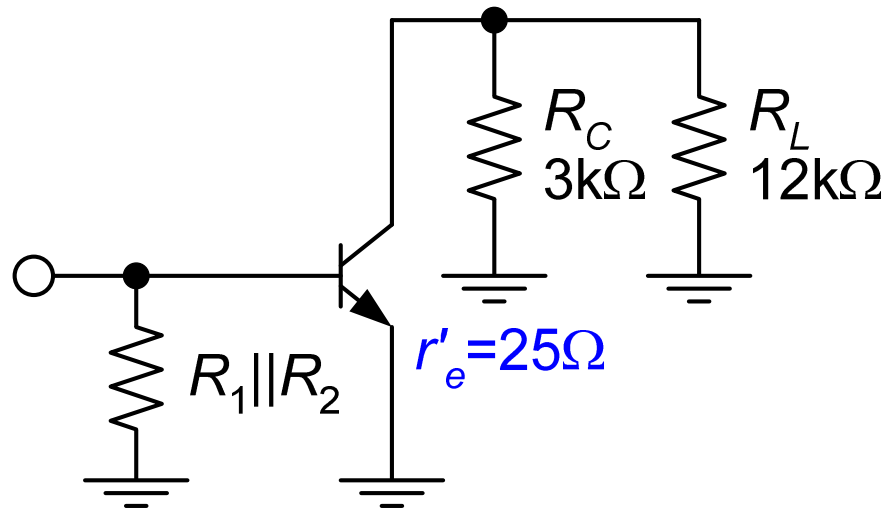

$$r_c = R_C \parallel R_L = 2.4\text{k}\Omega$$

$$A_v = -\frac{r_c}{r'_e} = -96$$

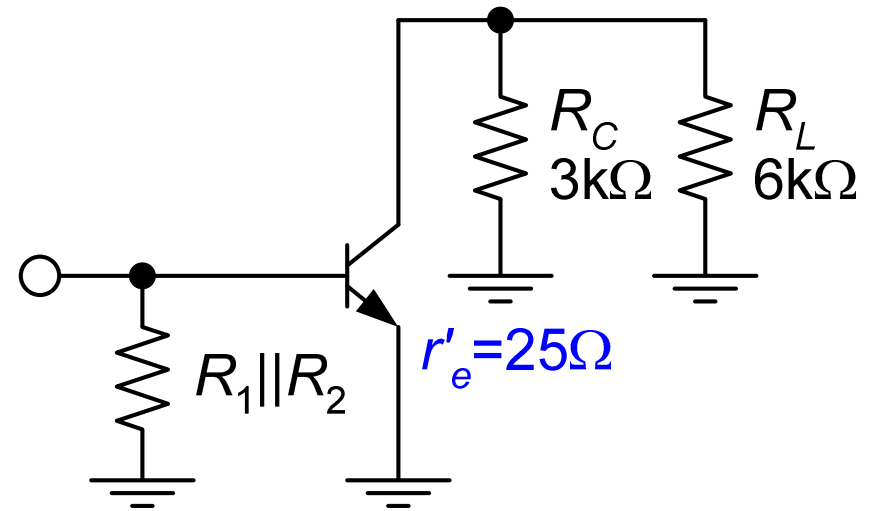

$$r_c = R_C \parallel R_L = 2\text{k}\Omega$$

$$A_v = -\frac{r_c}{r'_e} = -80$$


The lower the load resistance is, the lower the voltage gain.

No load

$$r_c = R_C = 3\text{k}\Omega$$

$$A_v = -\frac{r_c}{r'_e} = -\frac{3\text{k}\Omega}{25\Omega} = -120 \text{ (max. gain)}$$

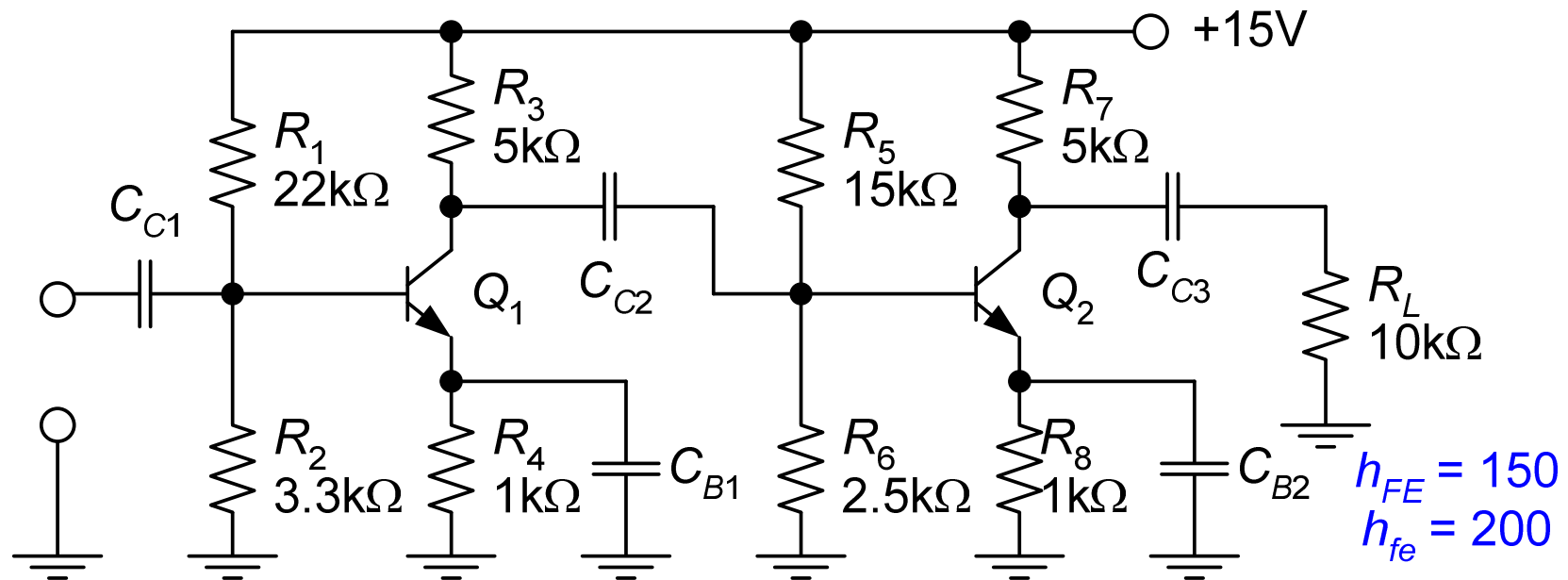Determine  $A_v$  of the 1<sup>st</sup> stage. Assume that  $r'_e$  for the 1<sup>st</sup> stage is  $19.8 \Omega$  and  $r'_e$  for the 2<sup>nd</sup> stage is found to be  $17.4 \Omega$ . For the 2<sup>nd</sup> stage,  $h_{fe}$  is 200.



$$Z_{in(base)} = (h_{fe} + 1)r'_e = 201 \times 17.4 = 3.497 \text{ k}\Omega$$

$$Z_{in} = R_5 \parallel R_6 \parallel Z_{in(base)} = 1.329 \text{ k}\Omega$$

$$r_C = R_3 \parallel Z_{in} = 5 \text{ k}\Omega \parallel 1.33 \text{ k}\Omega = 1.05 \text{ k}\Omega$$

$$A_v = -\frac{r_C}{r'_e} = -\frac{1.05 \text{ k}\Omega}{19.8 \Omega} = -53.03$$