

Processor Design


A. Sahu
CSE, IIT Guwahati

Please be updated with
<http://jatinga.iitg.ernet.in/~asahu/cs222/>

Outline

- **Components of CPU**
 - Register, Multiplexor, Decoder, IM/DM
 - Adder, subtractor, **Variety of Adder**
 - **Multipplier : Serial, Parallel**
 - **ALU and Floating Point**
- **Processor Design**
 - Single Cycle (Data Path and Control)
 - Multi-cycle (Data Path)
 - Pipeline (Data Path)

Flow of Our Course

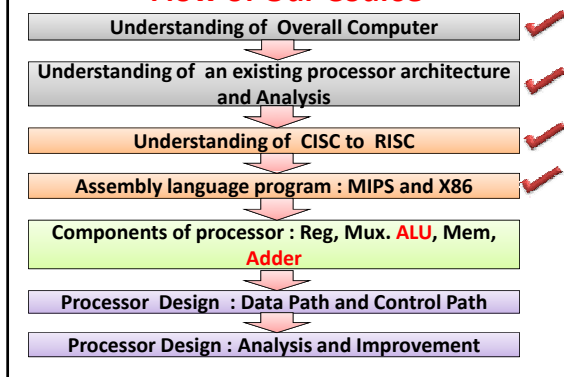


Processor Design & ALU Design

- **Topic ALU Design** $\leftarrow \rightarrow$ **Processor Design**
- **ALU Design**
 - Adder/ Substrator, Multiplier
 - Floating point, ALU (Int/float) Design
- **Processor Design**
 - Single Cycle (Data Path & Control Path)
 - Multi Cycle (Only Data Path)
 - Pipelined (Only Data path)


Components for MIPS subset

- Register
- Adder
- ALU
- Multiplexer
- Register file
- Program memory
- Data memory
- Bit manipulation components


MIPS Components - Register

 


MIPS Components - Adder

 


MIPS Components - ALU

 


MIPS components - Multiplexers

 


MIPS Components - register file

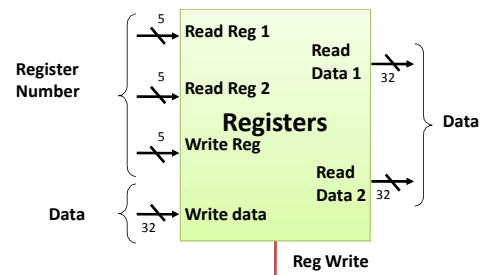

MIPS Components: Program memory

 

 MIPS Components - Bit manipulation circuits



Processor Design

13

Processor Design

- **A simple implementation: Single Cycle**
 - Data path and control
- Performance considerations
- Multi-cycle design
 - Data path and control
- Micro-programmed control
- Exception handling

14

Simple Processor Design

- MIPS subset for implementation
- Design overview
- Division into data path and control
- Building blocks - combinational and sequential
- Clock and timings
- Components required for MIPS subset


MIPS subset for implementation

- Arithmetic - logic instructions
 - **add, sub, and, or, slt**
 - Memory reference instructions
 - **lw, sw**
 - Control flow instructions
 - **beq, j**
- Incremental changes in the design to include other instructions will be discussed later

Generic Implementation


- Use the program counter (PC) to supply instruction address
- Get the instruction from memory
- Read registers
- Use the instruction to decide exactly what to do

Design overview

 

18

Division into Data path and Control

 

A Processor Design Method


Build the datapath step by step as follows

- Start with R - class instructions
- Include other instructions one by one
- Identify control signals
- Interconnect datapath and controller

MIPS subset for implementation

- Arithmetic - logic instructions
 - add, sub, and, or, slt
- Memory reference instructions
 - lw, sw
- Control flow instructions
 - beq, j

Division into data path and control

 


Datapath for add,sub,and,or,slt

- fetch instruction
 - address the register file
 - pass operands to ALU
 - pass result to register file
 - increment PC
- } actions required


Format: add \$t0, \$s1, \$s2

000000	10001	10010	01000	00000	100000
op	r _{dst}	r _{src1}	r _{src2}	shamt	funct


Fetching instruction

 


Addressing RF

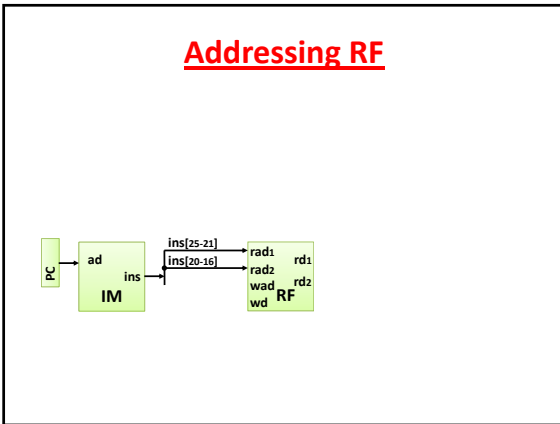


Passing operands to ALU

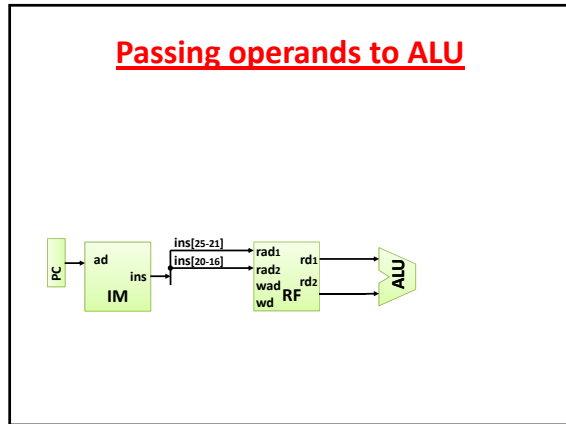

Passing the result to RF

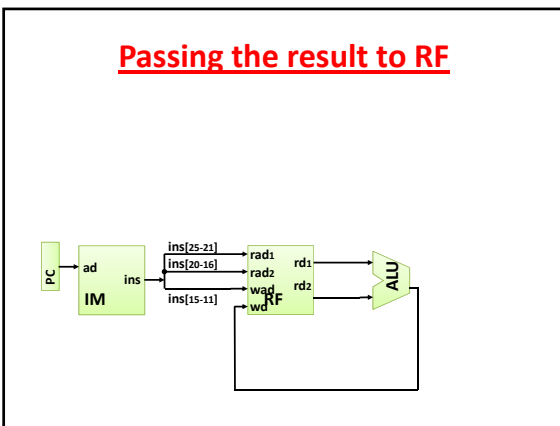

Incrementing PC

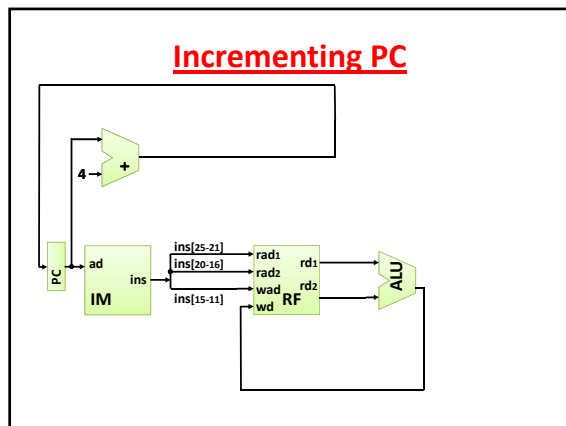


Load and Store instructions


- format : I
- Example: lw \$t0, 32(\$s2)

35	18	9	32
op	r _{dst}	r _{src1}	16 bit number

Adding "sw" instruction

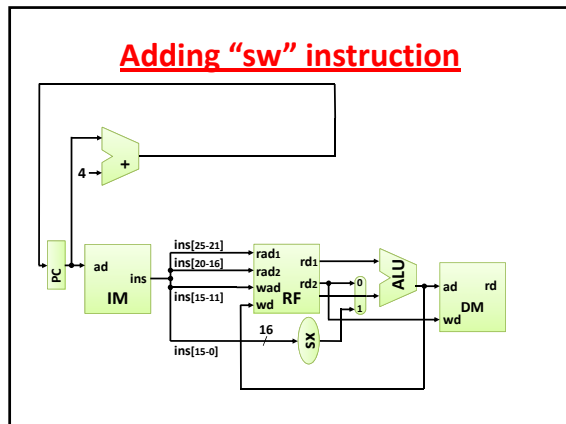

Adding "lw" instruction

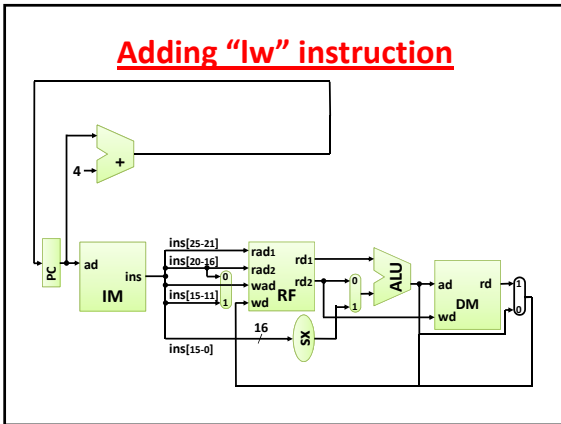


Format of beq instruction

- beq I-format




$$PC = (PC+4) + \text{SignXtend16to32}(\text{level} * 2)$$

Adding "beq" instruction

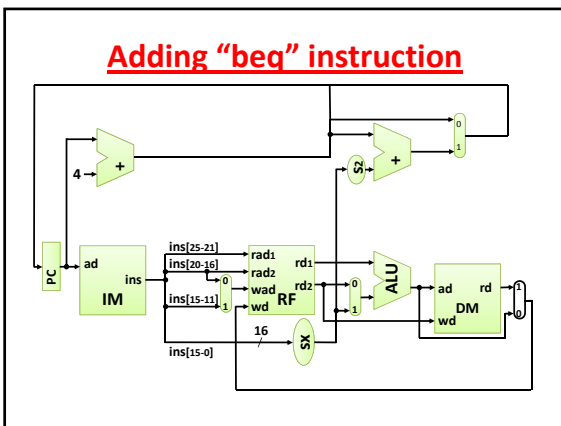


 MIPS components - bit manipulation circuits



Format of jump instruction

- j J-format

 




$$PC = \text{Higher 4bit PC Old PC} + \text{Level} \ll 2$$

$$= 4 \text{ bit from PC} + 16 \text{ bit Level} + 2 \text{ bit } 00$$

$$= 32 \text{ bits}$$

Adding "j" instruction

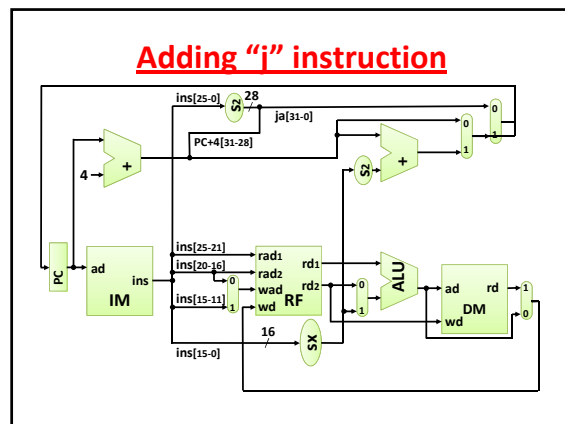

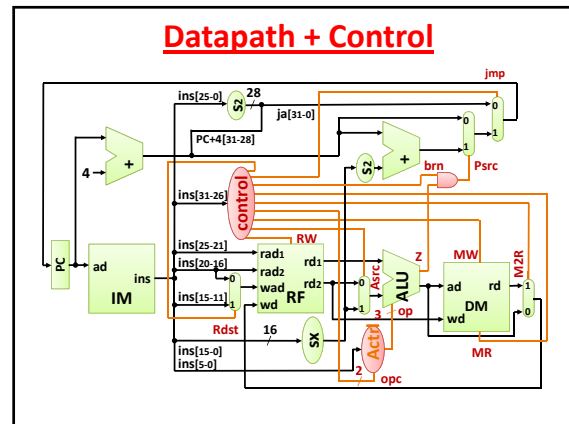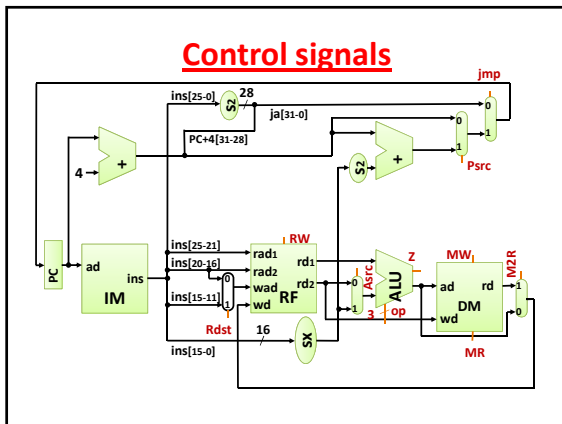

Summary

Processor designed for {add, sub, and, or, slt, lw, sw, beq, j}

- Step by step approach
- Started with {add, sub, and, or, slt}
- Added {sw, lw}, then added {beq, j}
- Identified control signals and connected to a controller (black box).