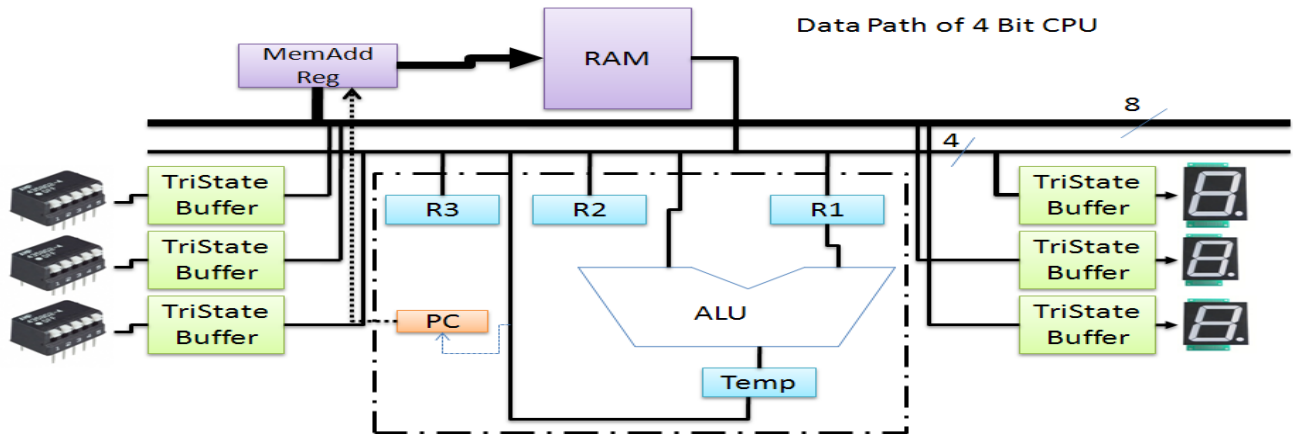


CS223 Project

Design a 4 bit CPU consisting of 16 instructions namely (*ADD, SUB, AND, NOT, OR, LOAD, STORE, J, JZ, CALL, RETURN, MOVR1toR2, MOVR1toR3, MOVR2toR1, MOVR3toR1*) with three register R1, R2 and R3. You can design the circuit with micro-instruction control or FSM/hardwired control (which clock cycle what micro-operations). **MUL instruction not required.**

- (a) Design I/O subsystem for CU with 8 bit address and 4 bit data bus. Data and Address may be supplied from DIP switches and also Data/Address to be displayed on three 7-segment displays.
- (b) Interface 4 register, an ALU and a memory chip to above designed I/O subsystem



You should be able to run two program (a) multiplications of two number and display the result at LEDs (b) recursive sum up to N (SUM N=N+SUM(n-1) till N==0).

As EPROM **programmings cum eraser are** not working properly, so you have to use a single RAM for both storing program and micro-program. It may be tricky to use in this way. It is mandatory to use PC parallel port to download user program and control memory to RAM using a C/CPP program. FRC connector is available in the lab.

```
#include<stdio.h>
#include <dos.h>
void main() {
    outputb(0x378,0xFF); //0x378 is parallel port
                        //& 0xFF is data
    delay(5);
}
```

- TCC -o download.exe download.cpp
- Download.exe Program.exe

You can have a FILE which contain binary of your program starting at address A1 and sequence of micro-control operations for 4bit CPU starting at address A2. From parallel port first generate address then download data to the RAM. For writing 2KB data you may require $5 * 2000 = 10000ms = 10s$. Data can be viewed by connecting LEDs : Pin2 --- LED ---Pin18, pin3 ---LED---pin19, ...

Pin	Direction	
2	Data 0	In/Out Data.0
3	Data 1	In/Out Data.1
4	Data 2	In/Out Data.2
5	Data 3	In/Out Data.3
6	Data 4	In/Out Data.4
7	Data 5	In/Out Data.5
8	Data 6	In/Out Data.6
9	Data 7	In/Out Data.7

Parallel Port Viewer
Choose LPT Number: LPT1 378h
Choose Data Port In/Out mode: Data Out
DATA Port (278h/378h)
STATUS Port (279h/379h)
CONTROL Port (27Ah/37Ah)