

# INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

Department of Electronics & Electrical Engineering

EE102: Basic Electronics Laboratory

## Expt.No. 6: Operational Amplifier Circuits

### Objectives:

1. To study inverting and non-inverting amplifier circuits with an Op-Amp.
2. To study a non-inverting high pass filter circuit made using an Op-Amp.

### Materials Required:

1. Equipment: Breadboard, Function Generator, Oscilloscope, DC Supply
2. Components: LM741 Op Amp (One), 1k $\Omega$  (One), 10k $\Omega$  (One), 12k $\Omega$  (Two), 100k $\Omega$  (One), 0.1 $\mu$ F (One)

### Precautions and Guidelines:

1. The Op-Amp generally works on split power supply (e.g.  $\pm 12$  V). Both positive and negative power supplies must be present whenever op-amp is powered.
2. The range of power supply is from  $\pm 5$  V to  $\pm 15$  V. Do not forget to connect the common terminal of the power supply to the ground on the breadboard.
3. Connecting only one side of power supply or interchanging positive and negative power supplies damages the Op-Amp.
4. For connecting power supply, you have to follow the procedure as given below.
  - a. Disconnect the power supply to Op-Amps.
  - b. Switch on the power supply.
  - c. Set the output voltage as required (e.g.  $\pm 12$  V).
  - d. Switch off the power supply.
  - e. Connect the power supply to Op-Amps.
  - f. Switch on the power supply.
5. Keep ground terminals of the oscilloscope probes and function generator output, and power supply common connected together throughout the experiment.

### Pre-Lab Work:

1. Obtain theoretical values of  $V_o/V_i$  for step 5 of Part A.
2. Obtain theoretical values of  $V_o/V_i$  for step 5 of Part B.
3. Obtain the theoretical value of cut-off frequency for the circuit in Part C.

### Part A: Inverting Amplifier

1. Assemble the circuit shown in Fig.1 with  $R_1 = 10$ k $\Omega$  and  $R_2 = 1$ k $\Omega$ . Make sure the power supply ground is connected to the circuit ground.
2. Apply 200mV<sub>p-p</sub>, 1kHz sine wave at  $V_i$  from the function generator and see the output.
3. Observe  $V_o$  and  $V_i$ , and determine voltage gain  $A = V_o/V_i$ . Also obtain A for  $V_i$  values of 100mV<sub>p-p</sub> and 300mV<sub>p-p</sub>.

4. Change  $R_1$  &  $R_2$  to  $100\text{k}\Omega$  &  $10\text{k}\Omega$  and determine  $A$  for  $V_i = 100\text{mV}_{\text{p-p}}$ ,  $200\text{mV}_{\text{p-p}}$  and  $300\text{mV}_{\text{p-p}}$ .
5. Now apply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{mV}_{\text{p-p}}$ ) to the point 'X' through the potential divider circuit as shown in Fig.2 and note the values of  $V_o$  for
  - i.  $R_1 = 100\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$
  - ii.  $R_1 = 10\text{k}\Omega$  and  $R_2 = 1\text{k}\Omega$
6. Compute  $V_o/V_i$  for (i) and (ii).

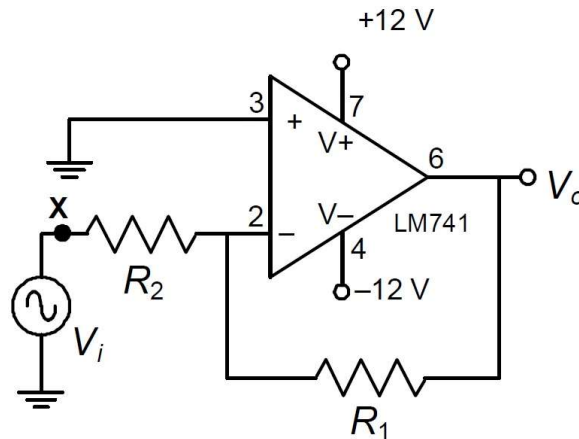


Fig.1

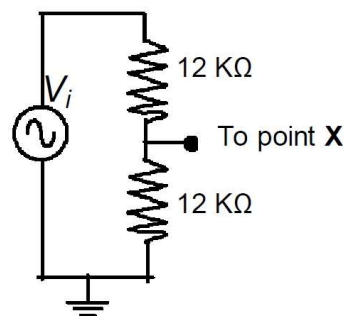


Fig.2

### Part B: Non-Inverting Amplifier

1. Assemble the circuit shown in Fig. 3 with  $R_1 = 10\text{k}\Omega$  and  $R_2 = 1\text{k}\Omega$ . Make sure the power supply ground is connected to the circuit ground.
2. Apply  $200\text{mV}_{\text{p-p}}$ ,  $1\text{kHz}$  sine wave at  $V_i$  from the function generator and see the output.
3. Observe  $V_o$  and  $V_i$ , and determine voltage gain  $A = V_o/V_i$ . Also obtain  $A$  for  $V_i$  values of  $100\text{mV}_{\text{p-p}}$  and  $300\text{mV}_{\text{p-p}}$ .
4. Change  $R_1$  &  $R_2$  to  $100\text{k}\Omega$  &  $10\text{k}\Omega$  and determine  $A$  for  $V_i = 100\text{mV}_{\text{p-p}}$ ,  $200\text{mV}_{\text{p-p}}$  and  $300\text{mV}_{\text{p-p}}$ .
5. Now apply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{mV}_{\text{p-p}}$ ) to the point 'X' through the potential divider circuit as shown in Fig.2 and note the values of  $V_o$  for
  - i.  $R_1 = 100\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$
  - ii.  $R_1 = 10\text{k}\Omega$  and  $R_2 = 1\text{k}\Omega$
6. Compute  $V_o/V_i$  for (i) and (ii).

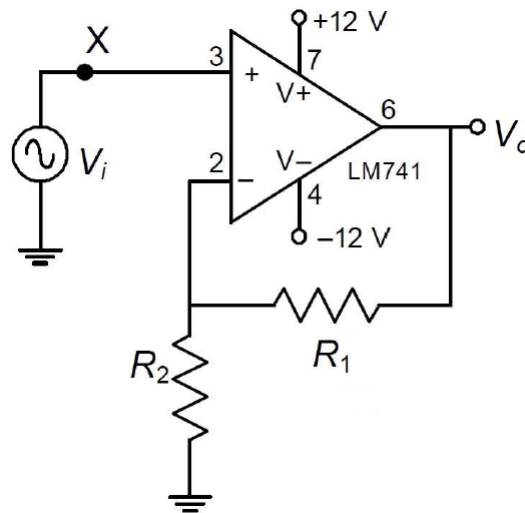


Fig.3

### Part C: Non-Inverting High Pass Filter

1. Assemble the circuit shown in Fig.4 with  $R_1 = 10\text{k}\Omega$ ,  $R_F = 100\text{k}\Omega$ ,  $R = 1\text{k}\Omega$  and  $C = 0.1\mu\text{F}$ . Make sure the power supply ground is connected to the circuit ground.
2. Connect Channel 1 of CRO to the input and Channel 2 to the output of the circuit.
3. Apply  $200\text{mV}_{\text{p-p}}$  at the input. Vary the frequency below and above the calculated cut-off frequency.
4. Observe corresponding  $V_o$  and  $V_i$ , and determine voltage gain  $A = V_o/V_i$ .
5. Plot gain vs frequency graph and mark the cut-off frequency.

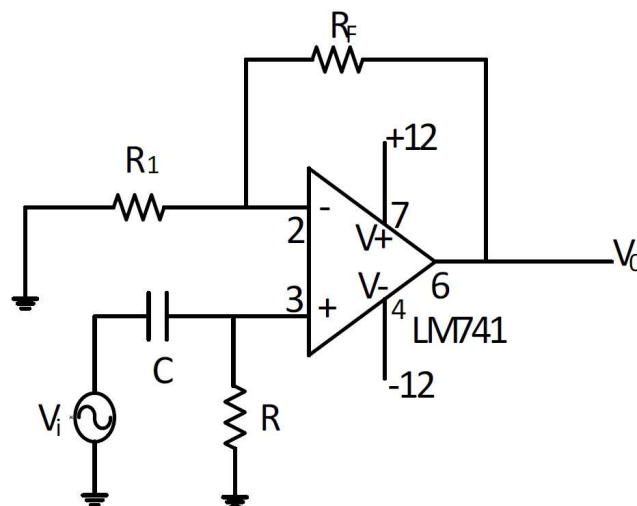


Fig.4

### Part D: Lab Report

Prepare and submit a lab report as specified in the general instructions regarding the lab. Include the answers to the following questions in the report:

1. For a source with high internal impedance which configuration (inverting or non-inverting) will be suitable for designing a good amplifier?