

# INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

Department of Electronics & Electrical Engineering

EE102: Basic Electronics Laboratory

Expt.No. 7 & 8: Common Emitter Amplifier

## Objectives:

1. To carry out an approximate DC and AC analysis of the given CE amplifier.
2. To determine the voltage gain, the “maximum undistorted peak-to-peak output voltage swing” (MUOVs) and the maximum input voltage for undistorted output.
3. To study the effect of emitter bypass capacitor on voltage gain.

## Materials Required:

1. Equipment: Breadboard, Function Generator, Oscilloscope, Multi-Output Power Supply, Digital Multimeter.
2. Components: NPN type 2N2222A (One), 470 $\Omega$  (One), 1k $\Omega$  (One), 2.2k $\Omega$  (One), 22k $\Omega$  (One), 100k $\Omega$  (One), 10 $\mu$ F (Two), 22 $\mu$ F (One), 1k $\Omega$  Pot (One)

## Precautions and Guidelines:

1. You are expected to come to the Lab with a neat report showing all calculations regarding the Pre Lab Work.
2. You will be allowed to perform the experiment only after the instructor has checked the report.

## Pre-Lab Work:

1. Carry out an approximate DC analysis by using the values given in Fig.1 and by making use of the assumptions  $I_{R1}, I_{R2} \gg I_B$ , so that  $I_{R1} \approx I_{R2}$  and  $V_{BE} \approx 0.65V$ . Estimate the DC quantities (quiescent values)  $V_B, V_E, V_C, I_E$  ( $\approx I_C$ ).
2. Draw the small signal equivalent of the circuit in Fig.1 and compute the voltage gain as
$$A_v = -(\beta \cdot R_C) / (r_b) \approx - (R_C) / (r_e) = - (R_C \cdot I_E) / (V_T) \approx - (R_C \cdot I_C) / (V_T)$$
Take  $V_T \approx 25mV$  (at room temp).
3. Compute MUOVs = 2 x Min { $V_{CC} - V_C, V_C - V_E$ }.
4. How do you decide that the + terminal of  $C_1$  (an electrolytic capacitor) should be connected to the  $R_1$ - $R_2$  node and the - terminal to the source  $v_i$ ? Likewise, for  $C_2$  and  $C_E$ .

## Part A: Measuring DC Quantities (Quiescent Values)

1. Before assembling the circuit, measure the actual values of the resistors by means of a Digital Multimeter (DMM). The actual values thus determined are to be used in calculating the currents.
2. Assemble the circuit, apply  $V_{CC}$  and note the following: (a) measure  $V_{BE}$  using a DMM and it should be around 0.6V ~ 0.7V indicating that BE junction is forward biased. (b) Measure  $V_C$  and check if  $V_E < V_C < V_{CC}$ . A value of  $V_C$  midway between  $V_E$  and  $V_{CC}$  is preferable.

3. Measure  $V_B$ ,  $V_E$ ,  $V_C$  and  $V_{CC}$  and determine  $I_B$ ,  $I_E$ ,  $I_C$  and hence  $\beta$  ( $\beta=I_C/I_B$ ).
4. Compute  $A_v$  using the experimentally determined values of  $R_C$  and  $I_C$ . Use  $V_T=25\text{mV}$ .

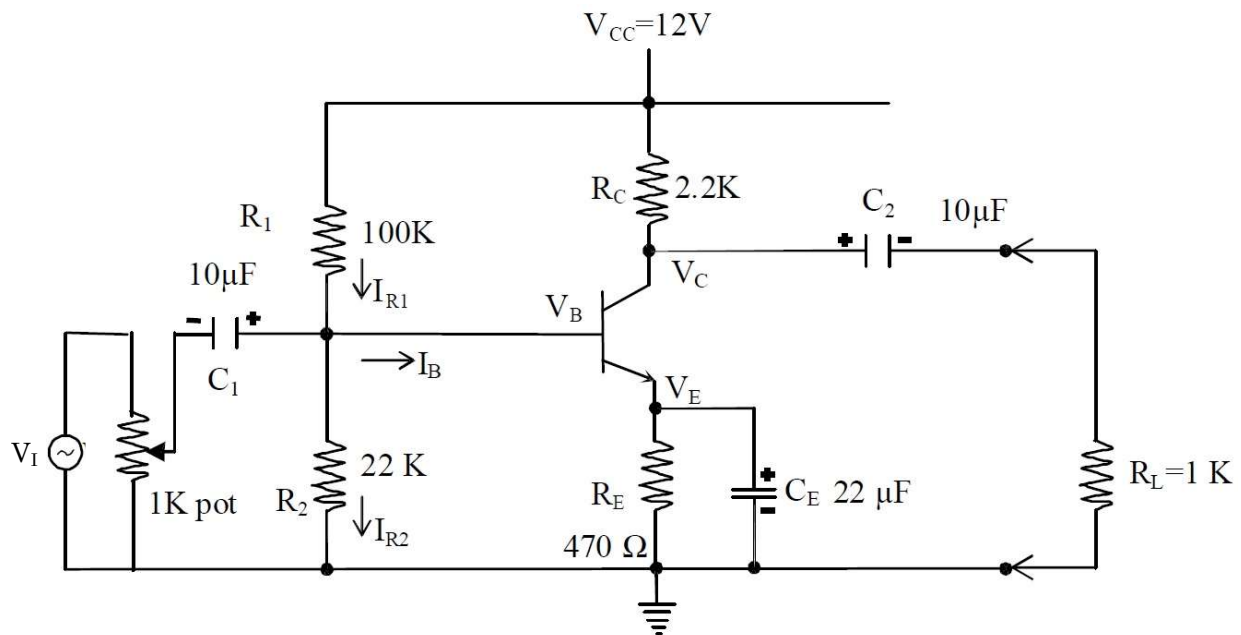


Fig.1

#### Part B: Voltage Gain Without Load Resistance

1. Disconnect  $C_2$ . Adjust Function Generator to get approximately 10-20mV peak-to-peak sinusoid at 1kHz (display in Channel 1 of CRO). Apply this voltage at amplifier input  $V_I$ .
2. Display the collector voltage in Channel 2 of CRO (use DC coupling). Note the  $180^\circ$  phase difference between the input and the output.
3. Adjust  $V_{I,p-p}$  amplitude to get a convenient value for peak-to-peak collector voltage  $V_{C,p-p}$  (say 2V). Use appropriate vertical sensitivity (V/div). Note the corresponding  $V_{I,p-p}$  (mV).
4. Experimentally obtained voltage gain is therefore computed as:

$$A_v = - (V_{C,p-p}) / (V_{I,p-p}).$$

#### Part C: Maximum Undistorted Output Voltage Swing (MUOVS)

1. Increase  $V_{I,p-p}$  slowly till you observe a slight flattening of  $V_{C,p-p}$  waveform at its peaks (either positive peaks or negative peaks). The peak-to-peak value of the output signal (just at the onset of distortion/clipping) is the MUOVS. Measure the corresponding  $V_{I,p-p}$ , the peak-to-peak input voltage.
2. Now increase  $V_{I,p-p}$  beyond this point and observe the output waveform. The sinusoid gets increasingly flattened and becomes more like a square wave (overdriving an amplifier leads to heavy distortion).

#### Part D: Voltage Gain With Load Resistance

1. The output of an amplifier normally drives a load resistance  $R_L$  which may represent an actual load like an ear-phone or a loudspeaker, or the input impedance of another stage of the amplifier.

2. Connect  $R_L$  (see Fig.1) to the collector through the coupling capacitor  $C_2$  ( $C_2$  blocks the DC voltage at the collector and allows only the AC i.e. the signal component to pass through).
3. Measure  $A_V$  with  $R_L$  connected. (you would observe a reduced  $A_V$  since  $R_{C,eff} = R_C || R_L$ ).

#### Part E: Effects of $C_E$ on $A_V$

1. Get back to the conditions in Part A i.e.  $V_I$  at 1 kHz, its amplitude adjusted to get  $V_{C,p-p} \approx 2V$ .
2. Now, remove  $C_E$  (with circuit powered) and note the drastic reduction in  $V_{C,p-p}$ . You have to change to appropriate V/div in your CRO. Determine the gain of the CE amplifier with unbypassed  $R_E$ .
3. Compare your observation with the theoretical value
 
$$A_V = -\alpha R_C / (R_E + r_e) \approx -R_C / R_E.$$
4. Display and sketch  $V_{I,p-p}$  and  $V_E$  waveforms. Note the amplitudes and the phase-relationship between them.
5. Display and sketch  $V_E$  and  $V_C$ . Note the amplitudes and the phase relationship. Please note that you are in DC coupling mode of the CRO. Please ensure that when you pressed the ground options in Channel 1 and Channel 2, both the horizontal traces (of the channels) are coinciding. Also ensure that the V/div of Channel 1 is equal to V/div of Channel 2.
6. Increase  $V_{I,p-p}$  gradually and observe how  $V_E$  and  $V_C$  change. Continue to increase  $V_{I,p-p}$  till you observe the +ve peak of  $V_E$  (almost) touching the negative peak of  $V_C$ . When this occurs, we say that the BJT has gone into saturation ( $V_{CE} \approx 0$ ).
7. What do you observe if  $V_{I,p-p}$  is increased beyond this point?

#### Part F: Lab Report

Prepare and submit a lab report as specified in the general instructions regarding the lab. Include the answers to the following questions in the report:

1. Why is  $V_C$  such that  $V_E < V_C < V_{CC}$  a preferred value in step 2 of Part A?
2. Compare the experimentally determined values of the currents and voltages in step 3 of part A with those you obtained through approximate analysis.
3. Compare the experimentally determined value of  $\beta$  in step 3 of part A with the approximate value given by the Lab Instructor.
4. Compare the experimentally determined value of the voltage gain  $A_V$  in step 4 of Part B with the computed values obtained in step 4 of Part A. Also compare this value with the value estimated in the Pre Lab Work.
5. What is the utility of knowing MUOVs in the design of an amplifier?