

EE1103H & 1104H

– Electric Circuits


Lecture - 18

Phasor Diagram

Find I_R , I_L , I_C and I_S as functions of V_s .


Draw phasor diagram of the circuit.

Determine $v_s(t)$ and $i_L(t)$.

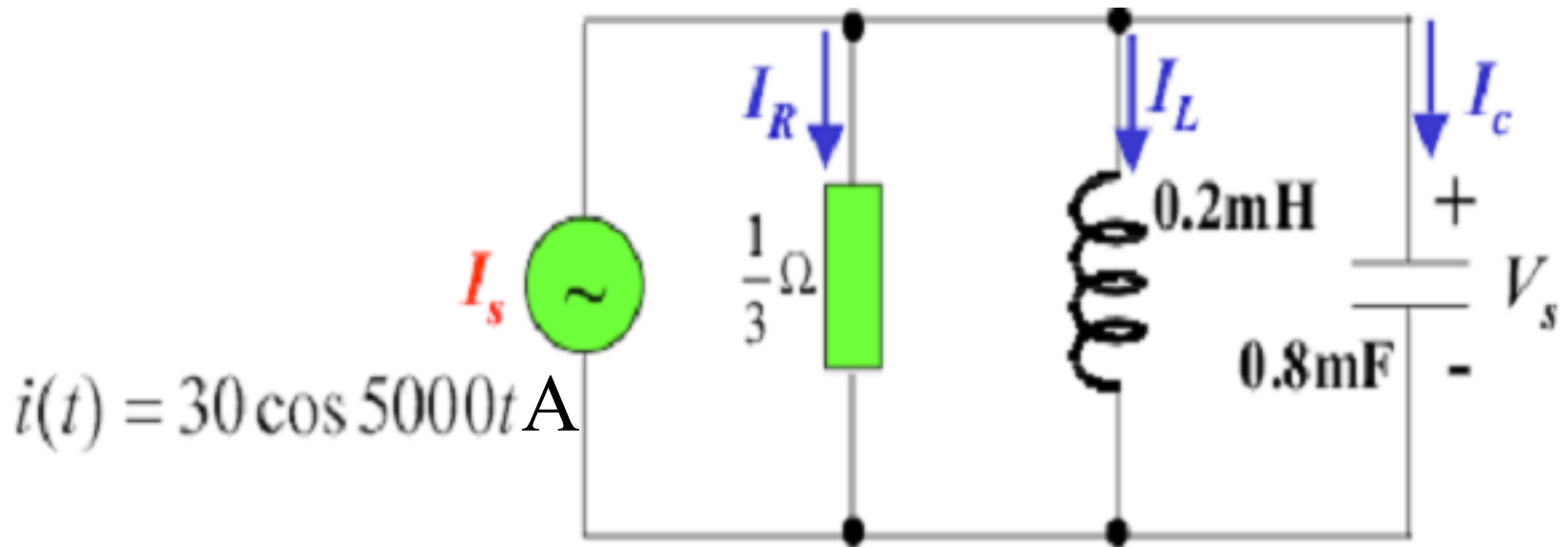

Solution

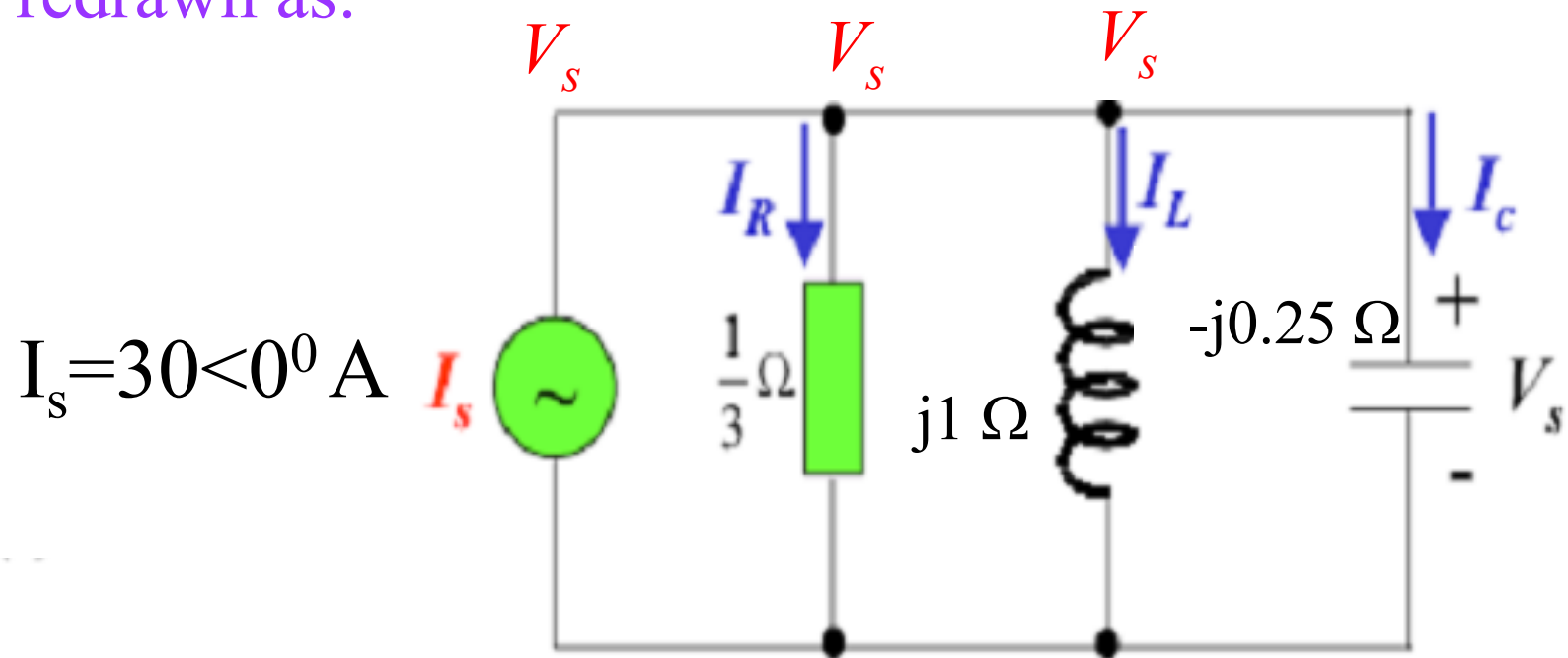The circuit in its equivalent PHASOR form can be redrawn as:



Current through the resistor $I_R = 3V_s$ Answers

Current through the inductor $I_L = -jV_s$

Current through the capacitor $I_C = j4V_s$


But, Current source $I_s = I_R + I_L + I_C = (3 + j3)V_s$

$$\Rightarrow V_s = I_s / (3 + j3) = 30 / (3 + j3)$$

$$\Rightarrow V_s = \frac{10}{\sqrt{2}} \angle -\frac{\pi}{4}$$

Answers

The PHASOR
DIAGRAM can be
drawn as:

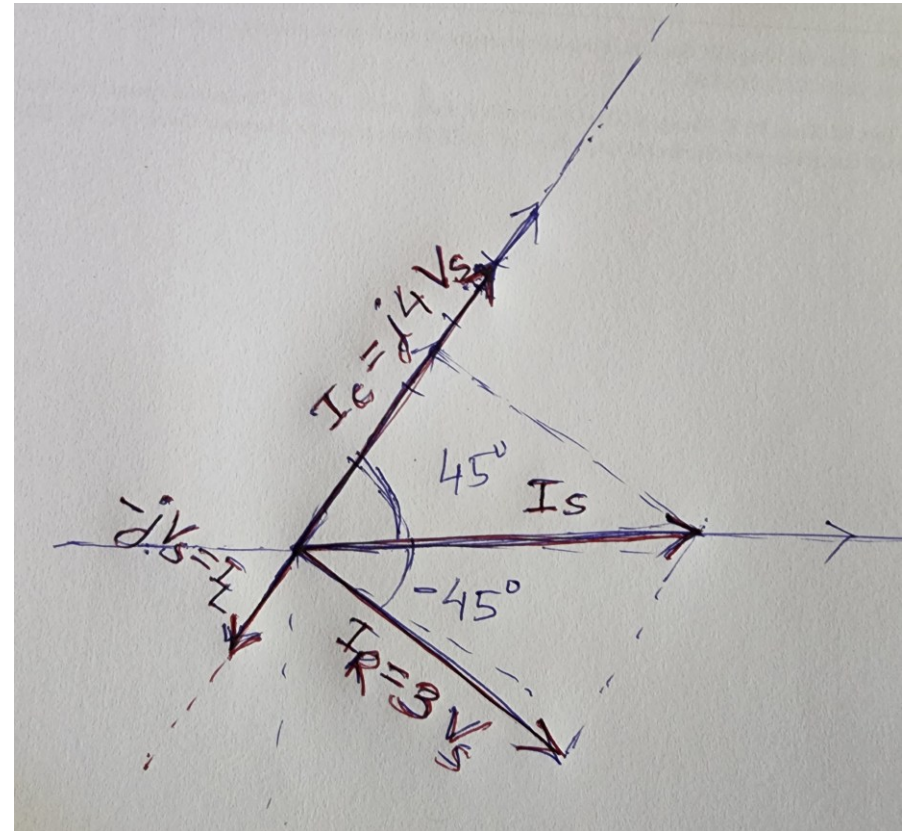


$$v_s(t) = \frac{10}{\sqrt{2}} \cos(5000t - \frac{\pi}{4}) \text{ V}$$

$$i_L(t) = \frac{10}{\sqrt{2}} \cos(5000t - \frac{3\pi}{4}) \text{ A}$$


Example: Benefits of Phasor Representation

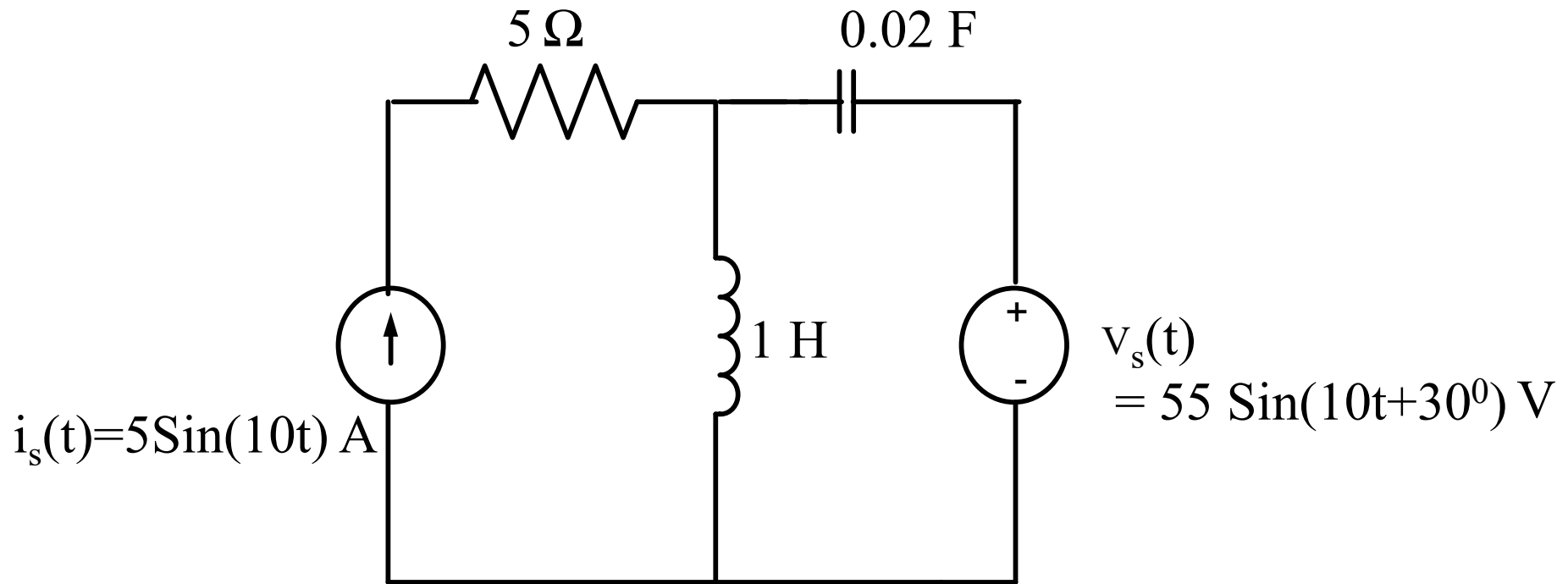- (a) Find voltage across the current source in phasor form.
- (b) Find voltage across the inductor in phasor form.



Solution using Thevenin's Theorem

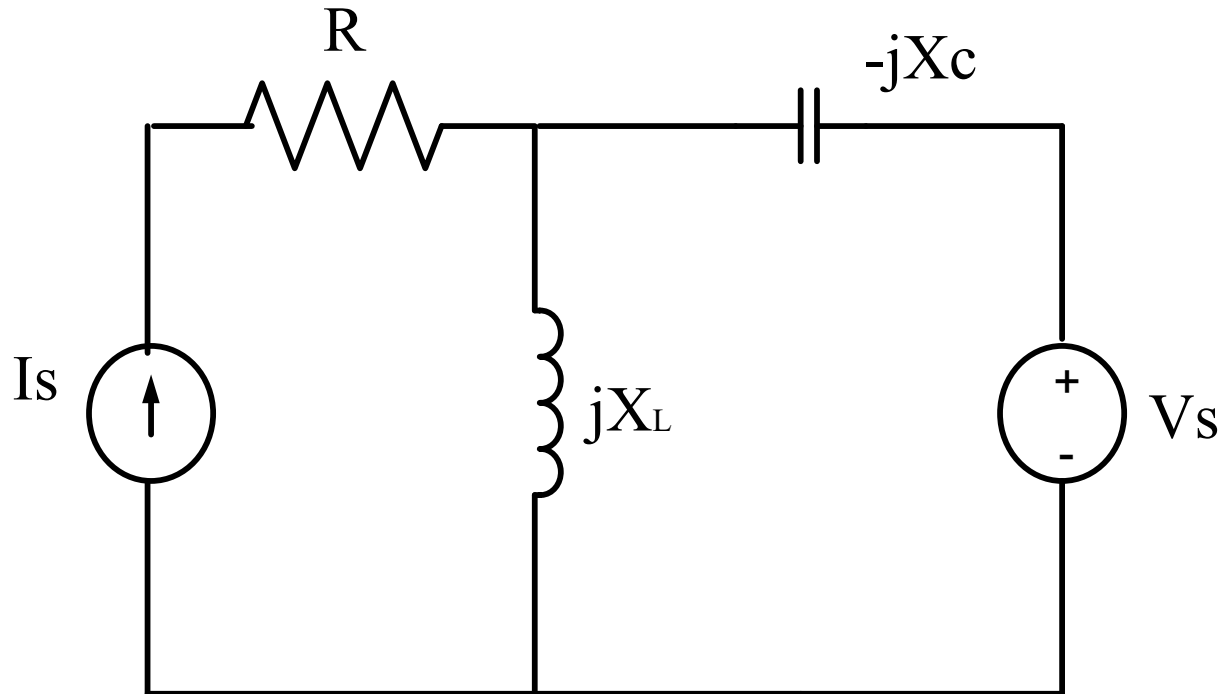
The given ac circuit in PHASOR form can be drawn as:



where $I_s = 5 \angle 0^\circ$ A; $V_s = 55 \angle 30^\circ$ V; $R = 5 \Omega$

$$X_L = \omega L = 10 \Omega \quad \text{and} \quad X_C = \frac{1}{\omega C} = 5 \Omega$$

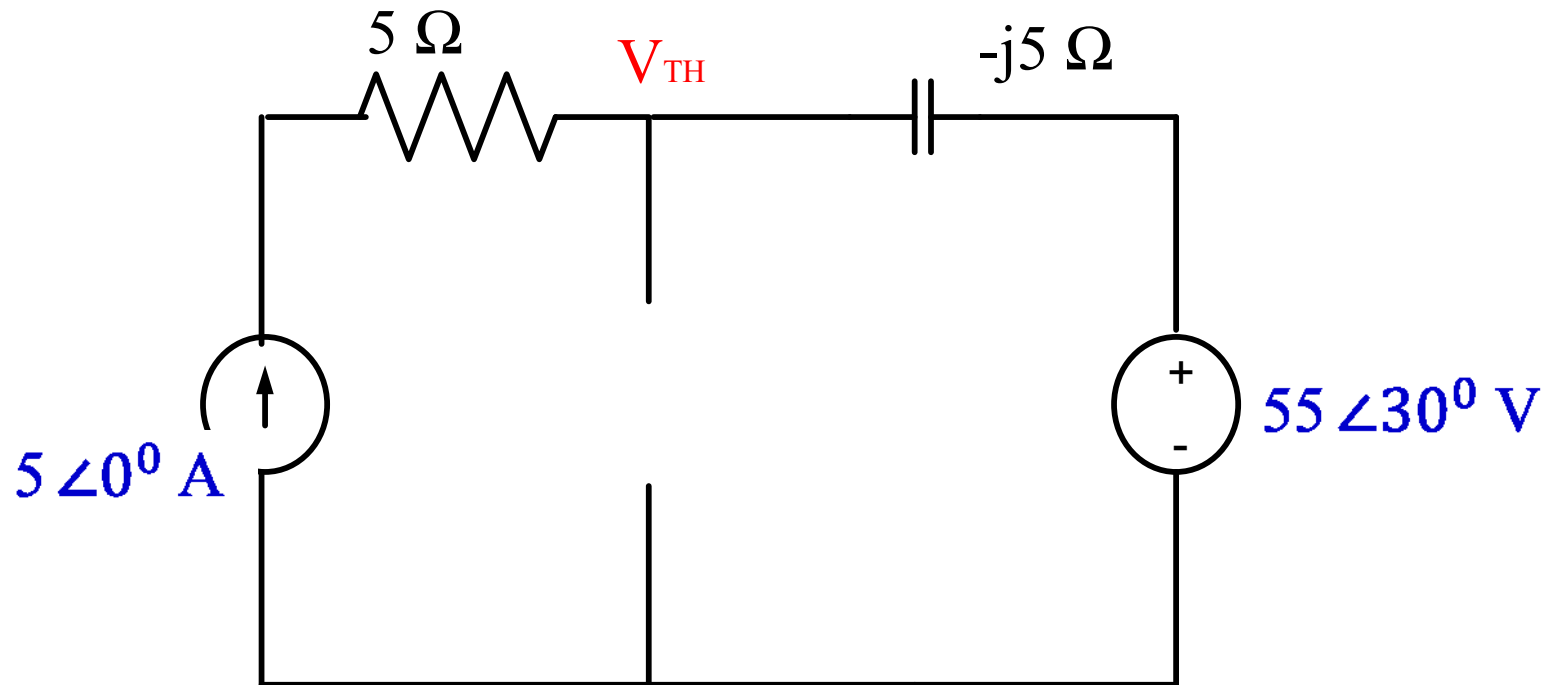The given ac circuit in PHASOR form with the **INDUCTOR** detached to find Thevenin Voltage (V_{TH}) and Thevenin Impedance Z_{TH} :




Current supplied by the voltage source:
$$\frac{55 \angle 30^\circ - V_{TH}}{-j5} = -5$$

$$\Rightarrow V_{TH} = 55 \angle 30^\circ - j25$$

After setting the **INDEPENDENT SOURCES to ZERO**, impedance seen from the open circuit nodes become: $Z_{TH} = -j5\Omega$.

Voltage across the Inductor

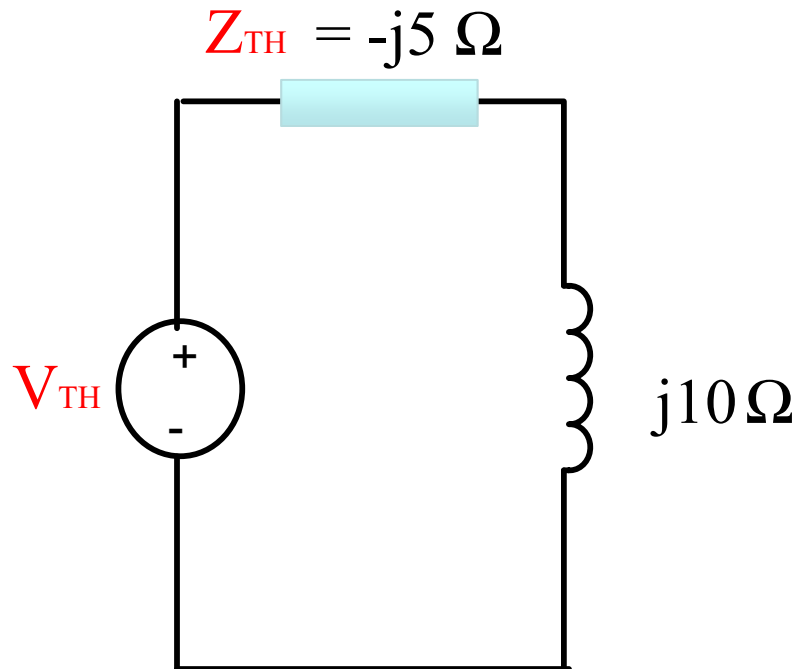


Thevenin Equivalent

$$\begin{aligned} &= \frac{V_{TH}}{(-j5 + j10)} \times j10 = 2V_{TH} \\ &= 110 \angle 30^\circ - j50 \\ &= 95.394 \angle 3^\circ \text{ V} \quad (\text{Answer}) \end{aligned}$$

$$\begin{aligned} &\text{Voltage across the current source} \\ &= 25 + (95.394 \angle 3^\circ) \\ &= 120.367 \angle 2.381^\circ \text{ V} \quad (\text{Answer}) \end{aligned}$$

Solution by Nodal Analysis Method

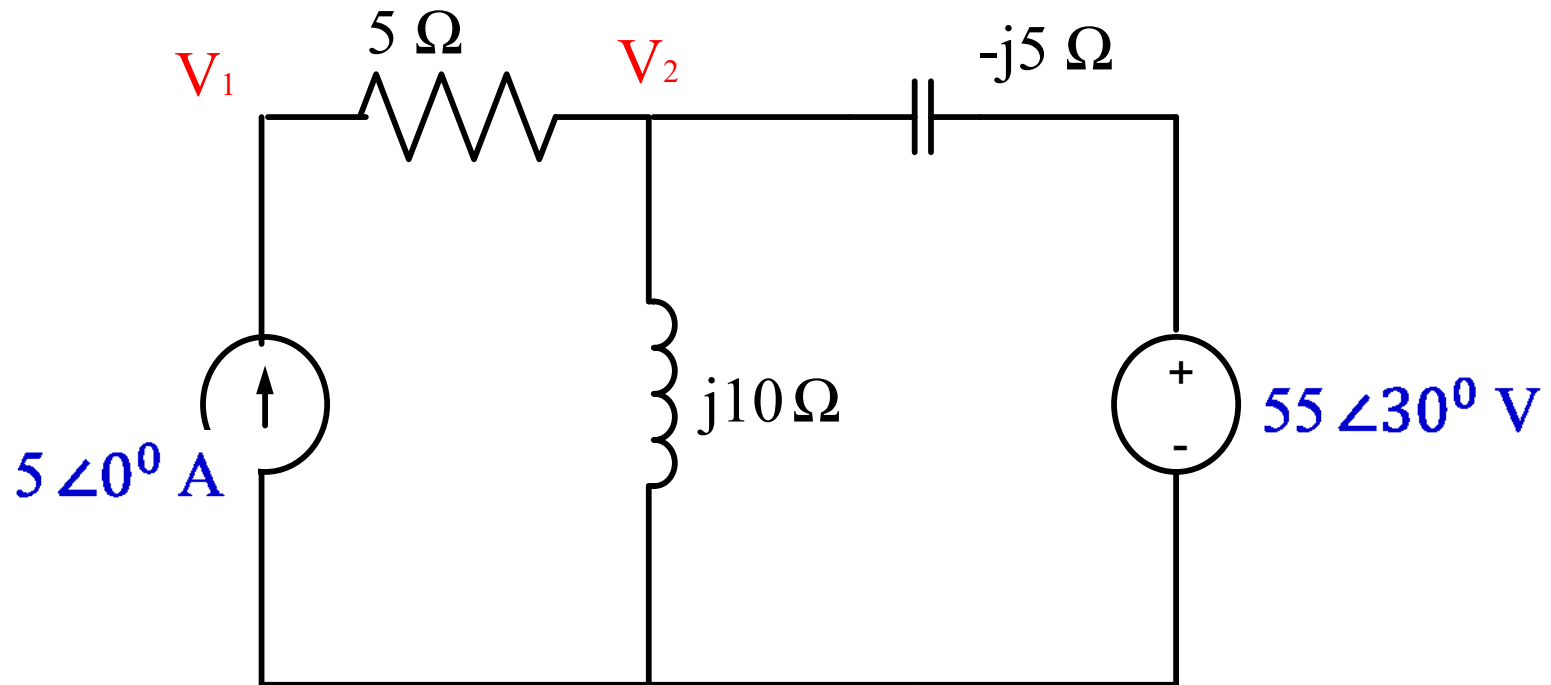The given ac circuit in PHASOR form can be drawn as:



Using NODAL Analysis at Node V_2

$$5\angle 0^\circ + \frac{55\angle 30^\circ - V_2}{-j5} = \frac{V_2}{j10}$$

$$\Rightarrow j50 - 2(55\angle 30^\circ - V_2) = V_2$$


$$\Rightarrow V_2 = 95.263 + j5$$

$$\text{So, } V_2 = 95.394 \angle 3^\circ \text{ V} \quad (\text{Answer})$$

$$\begin{aligned}\text{Also, } V_1 &= 5X5 + V_2 = 120.263 + j5 \\ &= 120.367 \angle 2.381^\circ \text{ V}\end{aligned}$$

Instantaneous Power, Average Power Complex Power, Apparent Power and Power Factor

Instantaneous Power

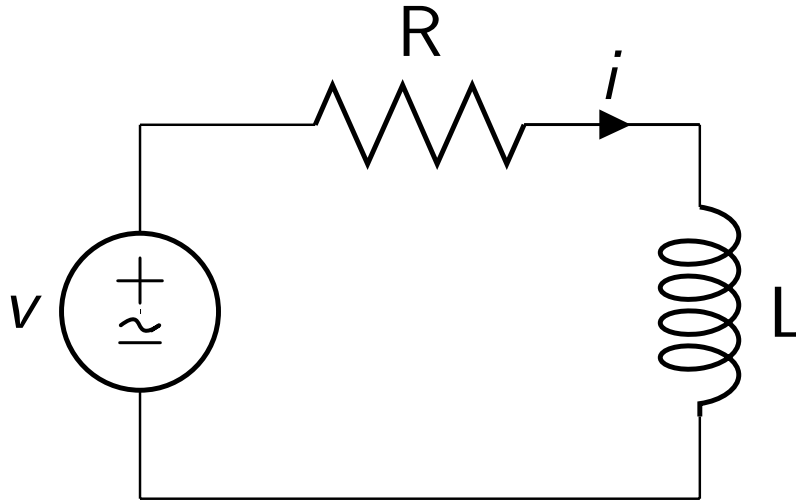

Let $v = V_m \sin(\omega t + \theta)$

Then $i = I_m \sin(\omega t + \phi)$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \text{ and } \theta - \phi = \tan^{-1} \frac{\omega L}{R}$$

Instantaneous Power

$$p(t) = v(t)i(t)$$

$$p(t) = V_m \sin(\omega t + \theta) I_m \sin(\omega t + \phi)$$


$$p(t) = \frac{V_m I_m}{2} (\cos(\theta - \phi) - \cos(2\omega t + \theta + \phi))$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) - \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

Average Power=Real Power $P = \frac{1}{T} \int_0^T p(t) dt$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{rms} I_{rms} \cos(\theta - \phi)$$

EXAMPLE: Instantaneous Power

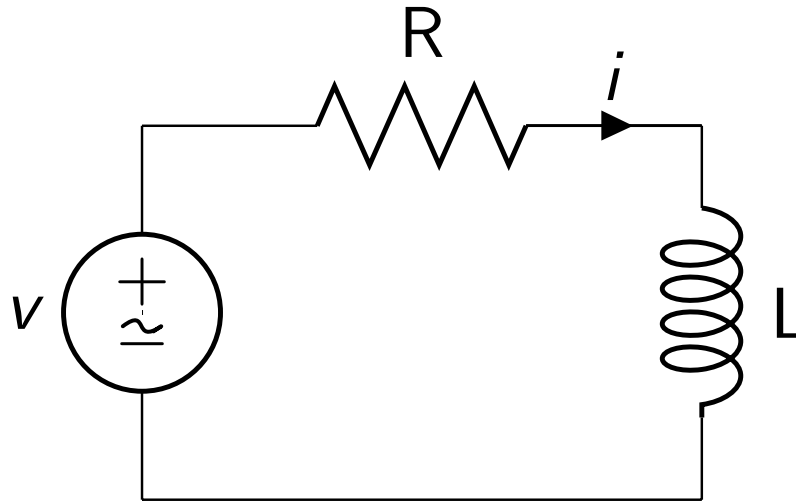

Let $v = V_m \sin(\omega t + \theta)$

Then $i = I_m \sin(\omega t + \phi)$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \text{ and } \theta - \phi = \tan^{-1} \frac{\omega L}{R}$$

Let: $R = 1 \Omega$

$L = 1 \text{ H}$

$v = \sqrt{2} \sin(t) \text{ Volts}$

Then, $\omega = 1 \text{ rad/s}$

$\theta = 0^\circ$

$V_m = \sqrt{2} \text{ V}$

$I_m = 1 \text{ A}$

$\theta - \phi = \tan^{-1}(1) = 45^\circ$

Instantaneous Power

$$p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) - \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$
$$= 0.5 - 0.707 \cos(2t - 45^\circ) \text{ W}$$

Average Power or Real Power (a) $P = \frac{1}{T} \int_0^T p(t) dt = 0.5 \text{ W}$

(b) Also, $P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = 0.5 \times \sqrt{2} \times 1 \times \cos(0 - 45^\circ) = 0.5 \text{ W}$

(c) But, $V_{\text{rms}} = V_m / \sqrt{2}$; $I_{\text{rms}} = I_m / \sqrt{2}$; So, $P = V_{\text{rms}} I_{\text{rms}} \cos(\theta - \phi)$
 $= 1 \times \left(\frac{1}{\sqrt{2}} \right) \times \cos(0 - 45^\circ) = 0.5 \text{ W}$

(d) Also, real power is drawn by the RESISTOR only. Then, average or real power delivered is :

$$(I_{\text{rms}})^2 R = (1/2) \times 1 = 0.5 \text{ W}$$

END