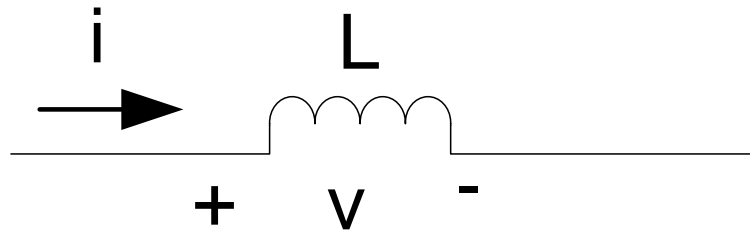


# EE101ME – Electric Circuits

# RL Circuit

## The Inductor




$$v = L \frac{di}{dt}$$

If current  $i$  is constant, voltage  $v$  is 0

So, inductor behaves as a short circuit to dc input current

Again, current through an inductor cannot change instantaneously (immediately)

# The Capacitor

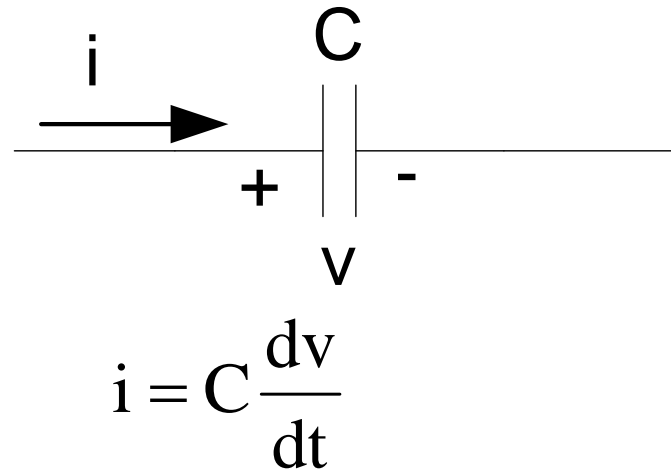

If voltage  $v$  is constant, then  $i$  is 0


So, capacitor behaves as an open circuit to dc input voltage

Again, voltage across a capacitor cannot change instantaneously (immediately)

# Initial Conditions of RLC Circuit
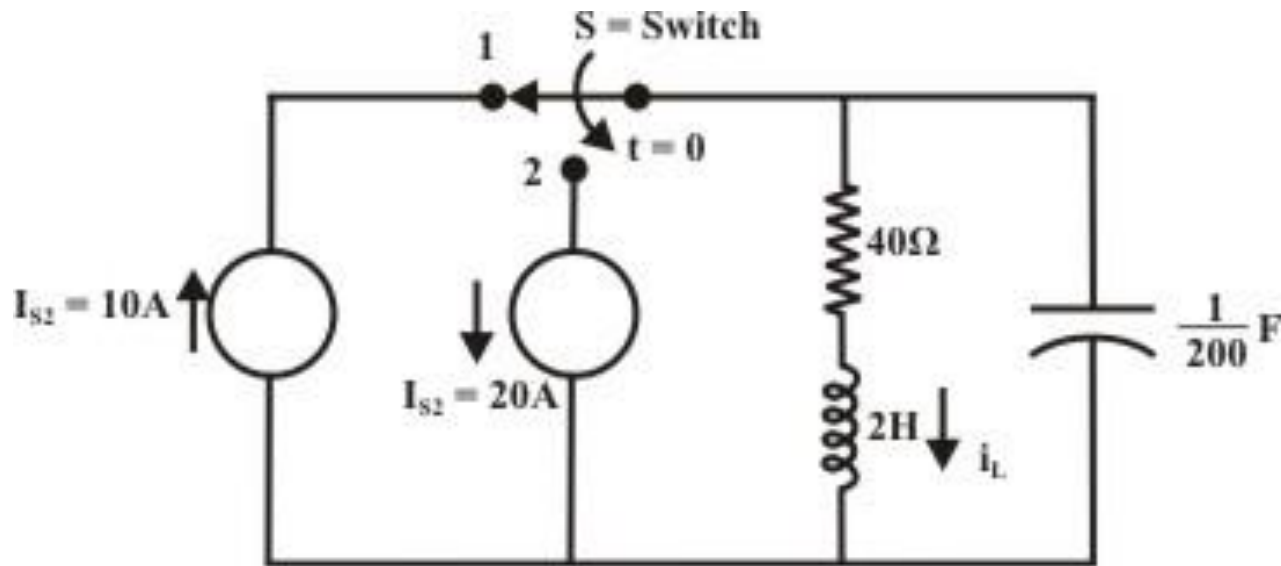
# Initial Conditions

Switch S is connected to Node 1 for a long time before connecting to Node 2 at time  $t = 0$  sec




Values for:

(a)  $i_L(0^-)$ ; (b)  $v_c(0^+)$ ; (c)  $v_R(0^+)$ ; (d)  $i_L(\infty)$

Values are  $10\text{ A}$ ,  $400\text{ V}$ ,  $400\text{ V}$ ,  $-20\text{ A}$

# Response of RL Series Circuit

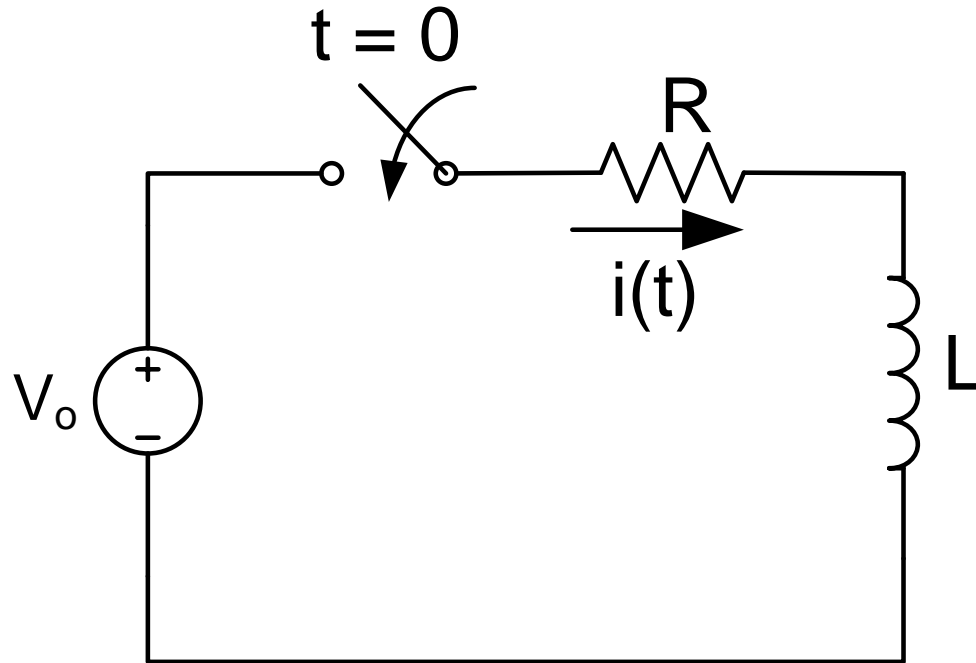

Find  $i(t)$  for  $t > 0$

$$Ri + L \frac{di}{dt} = V_0 \quad \text{for } t > 0$$

*Solution -*

*Complimentary Function*

*+ Particular Integral*



*Solution -*

*Natural Response ( $i_n$ ) from*

$$Ri + L \frac{di}{dt} = 0$$

*Forced Response ( $i_f$ ) from*

$$Ri + L \frac{di}{dt} = V_0$$

*Complete Solution is*

$$i = i_n + i_f$$

*For Natural Response*

$$Ri + L \frac{di}{dt} = 0$$

$$\text{or, } \frac{di}{dt} + \frac{R}{L}i = 0$$

$$\text{or, } i_n = Ae^{-\frac{R}{L}t}$$

*For Forced Response*

$$Ri + L \frac{di}{dt} = V_0$$

$$\text{But } L \frac{di}{dt} = 0$$

$$\text{So, } i_f = \frac{V_0}{R}$$

$$i(t) = Ae^{-\left(\frac{R}{L}\right)t} + \frac{V_0}{R} \quad t > 0$$

*For Finding A :      Apply the condition*

$$i(t = 0) = i(t = 0^-) = i(t = 0^+)$$

$$0 = A + \frac{V_0}{R}$$

$$A = -\frac{V_0}{R}$$

$$i(t) = \left( \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t} \right) \quad t > 0$$

$$\text{or, } i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{t}{\tau}} \right) \quad t > 0 \quad \tau = \frac{L}{R} \quad \text{Time Constant}$$

