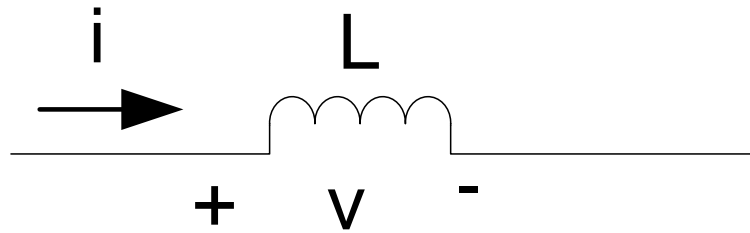


EE101ME – Electric Circuits

RL and RC Circuits

The Inductor




$$v = L \frac{di}{dt}$$

If current i is constant, voltage v is 0

So, inductor behaves as a short circuit to dc input current

Again, current through an inductor cannot change instantaneously (immediately)

The Capacitor

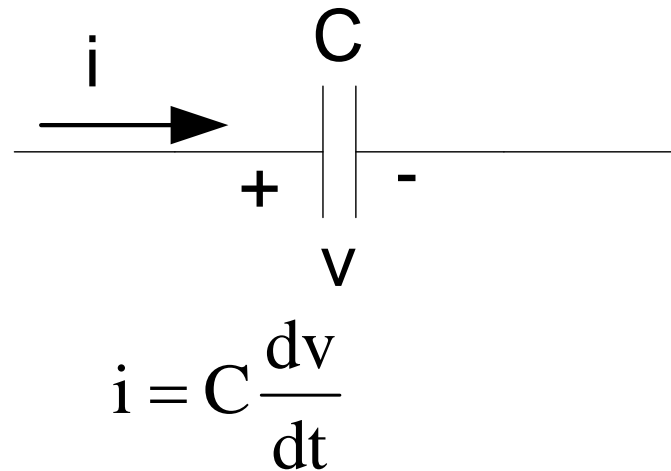

If voltage v is constant, then i is 0


So, capacitor behaves as an open circuit to dc input voltage

Again, voltage across a capacitor cannot change instantaneously (immediately)

Initial Conditions of RLC Circuit

Initial Conditions

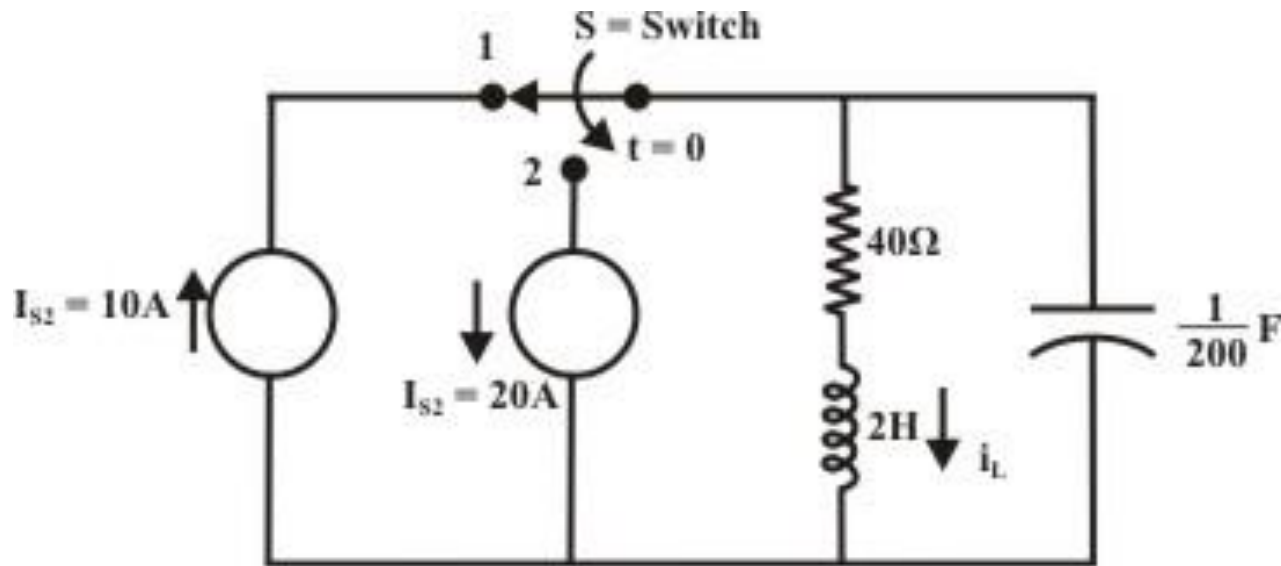Switch S is connected to Node 1 for a long time before connecting to Node 2 at time $t = 0$ sec




Values for:

(a) $i_L(0^-)$; (b) $v_c(0^+)$; (c) $v_R(0^+)$; (d) $i_L(\infty)$

Values are 10 A , 400 V , 400 V , -20 A

Response of RL Series Circuit

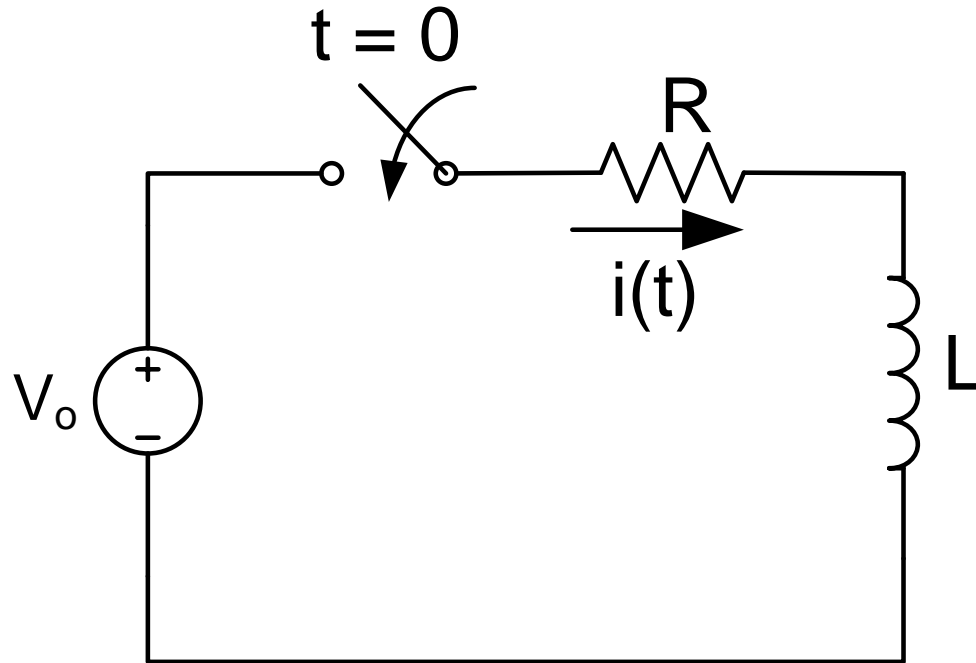

Find $i(t)$ for $t > 0$

After switching:

$$Ri + L \frac{di}{dt} = V_0 \quad \text{for } t > 0$$

Solution -

Complimentary Function

+ Particular Integral

Solution -

Natural Response (i_n) from

$$Ri + L \frac{di}{dt} = 0$$

Forced Response (i_f) from

$$Ri + L \frac{di}{dt} = V_0$$

Complete Solution is

$$i = i_n + i_f$$

For Natural Response

$$Ri + L \frac{di}{dt} = 0$$

$$\text{or, } \frac{di}{dt} + \frac{R}{L}i = 0$$

$$\text{or, } i_n = Ae^{-\frac{R}{L}t}$$

For Forced Response

$$Ri + L \frac{di}{dt} = V_0$$

$$\text{But } L \frac{di}{dt} = 0$$

$$\text{So, } i_f = \frac{V_0}{R}$$

Overall Response

$$i(t) = Ae^{-\left(\frac{R}{L}\right)t} + \frac{V_0}{R} \quad t > 0$$

For Finding A : Apply the condition

$$i(t = 0) = i(t = 0^-) = i(t = 0^+)$$


$$0 = A + \frac{V_0}{R}$$

$$A = -\frac{V_0}{R}$$


$$i(t) = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t} \right) \quad t > 0$$

$$\text{or, } i(t) = \frac{V_0}{R} \left(1 - e^{-\frac{t}{\tau}} \right) \quad t > 0 \quad \tau = \frac{L}{R} \quad \text{Time Constant}$$

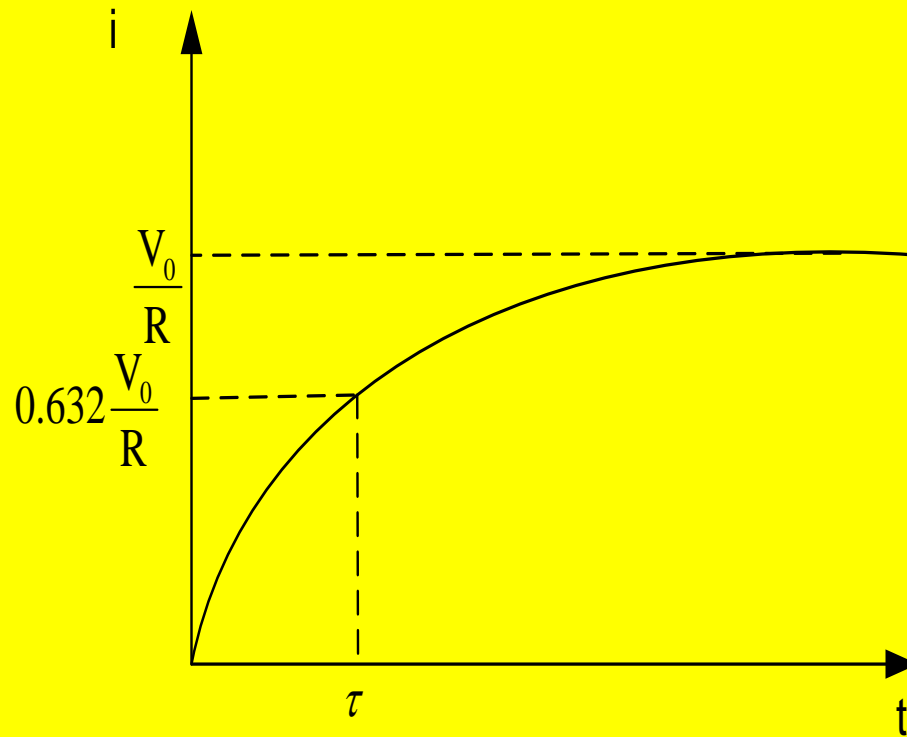Response of R-L Circuit or plot of the inductor current:



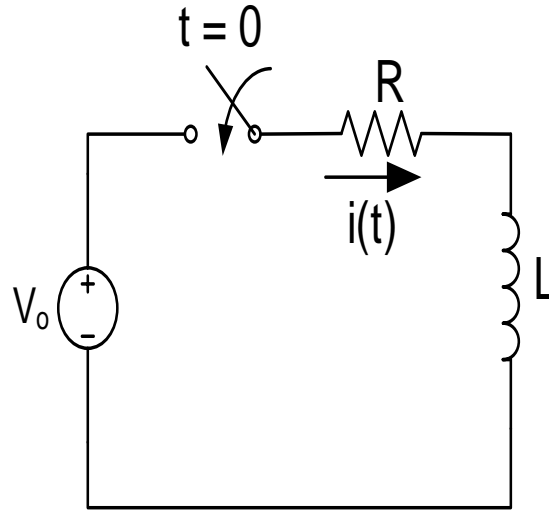
Find expression for the inductor current after switching and then plot $i_L(t)$ for $t \leq 0.1$ sec.




$$V_0 = 100 \text{ V}, R = 8\Omega, L = 0.2 \text{ H}$$

$$i_L(t) = [0 - 12.5] e^{-40t} + 12.5 = 12.5(1 - e^{-40t})$$

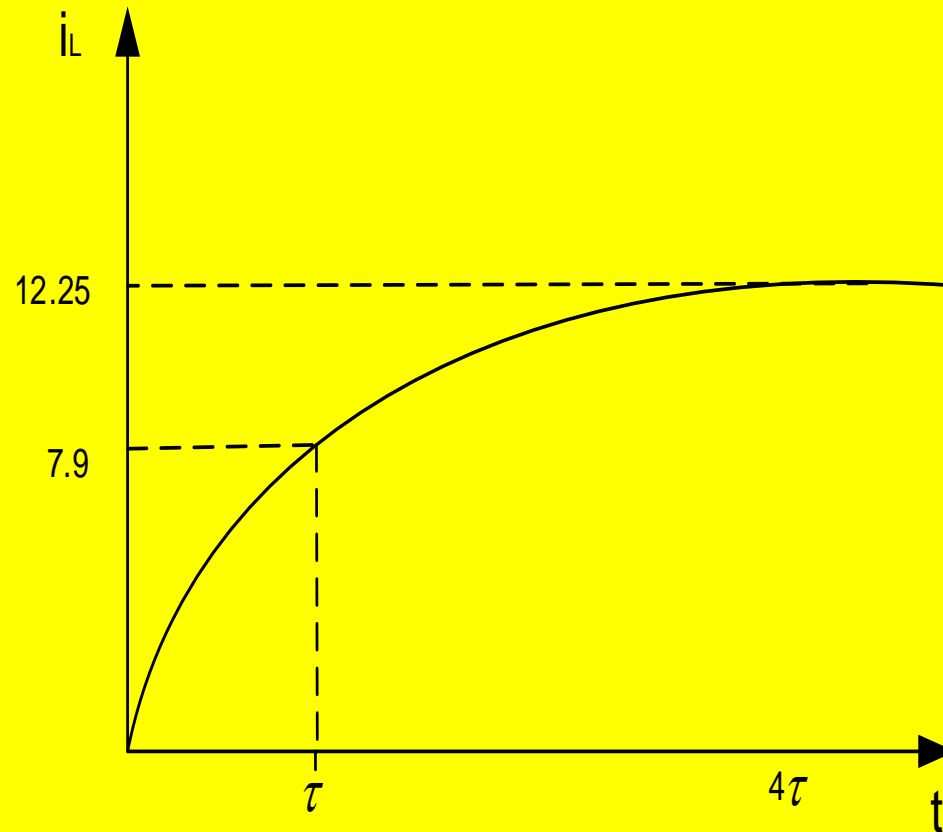Response of R-L Circuit or plot of the inductor current:



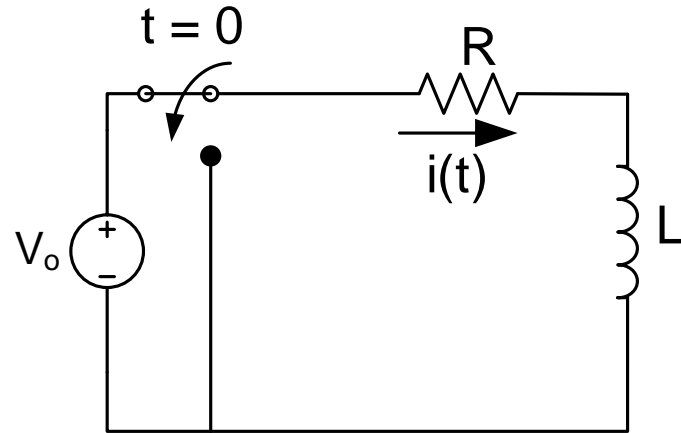- (i) Find expression for the inductor current after switching.
- (ii) At which time the inductor current becomes 50% of its initial value.




$$V_0 = 100 \text{ V}, R = 8\Omega, L = 0.2 \text{ H}$$

$$(i) \quad i_L(t) = 12.5 e^{-40t}$$

$$(ii) \quad t = 0.01733 \text{ sec}$$

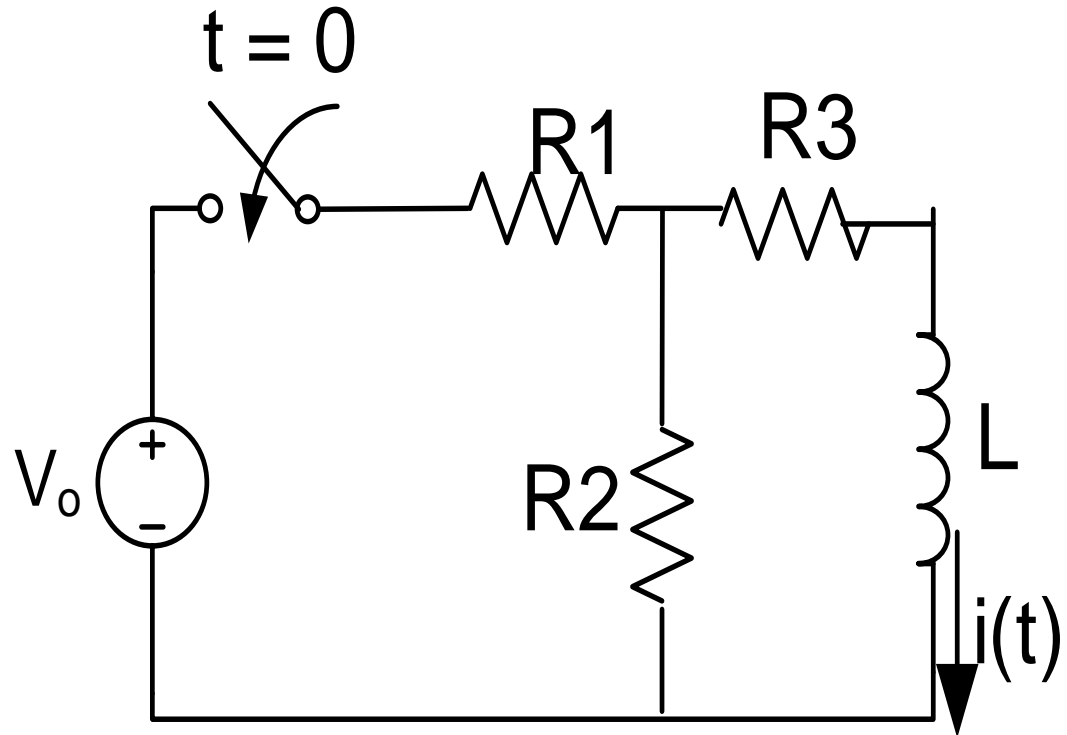Find expression for the inductor current after closing the switch at time $t = 0$.




$$i_L(t) = 0.333(1 - e^{-1.5t})$$

$$V_0 = 1 \text{ V}, R_1 = R_2 = R_3 = 1 \Omega, L = 1 \text{ H}$$

RL Circuit

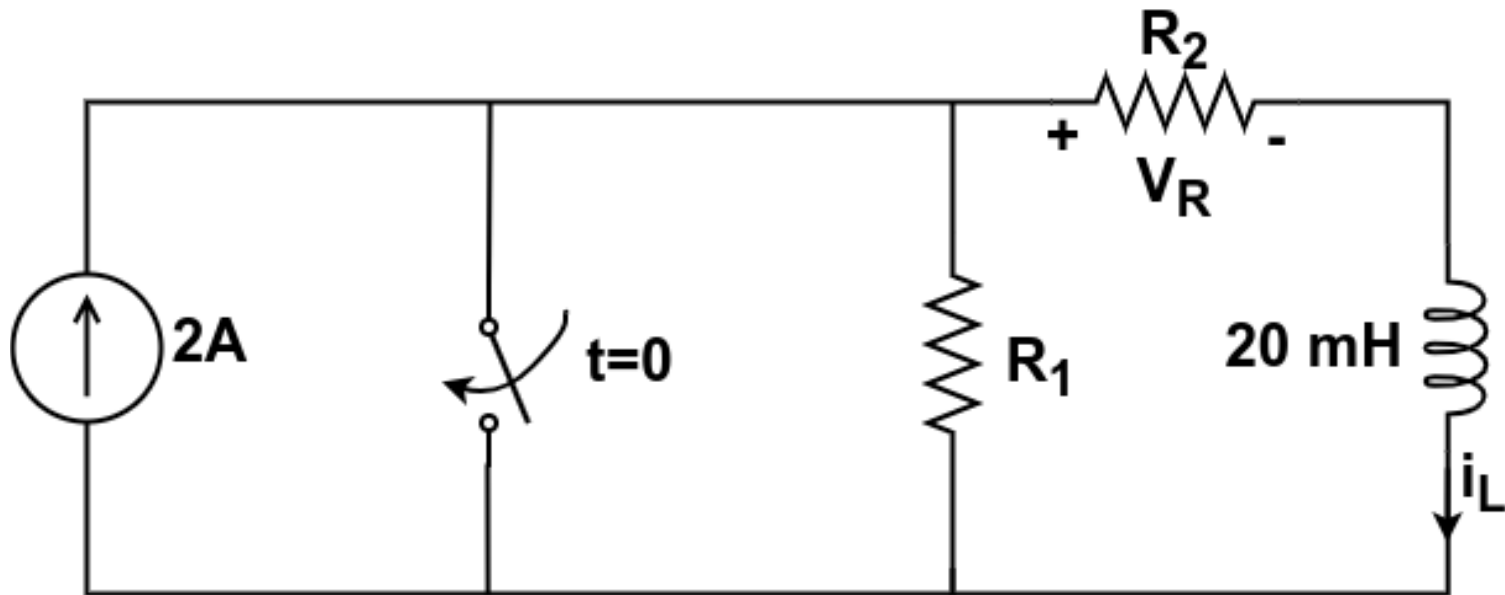
Given $R_1 = 7.8204 \text{ Ohm}$ and $R_2 = 13.8629 \text{ ohm}$,
find $v_R(0^+)$ and $v_R(1 \text{ ms})$. The switch closes at time $t = 0$.



$$v_R(0^+) = 10 \text{ V and } v_R(1 \text{ ms}) = 5 \text{ V}$$

Before closing the switch, the energy storage elements did not have any stored energy in them. If switch is closed at $t=0$, find

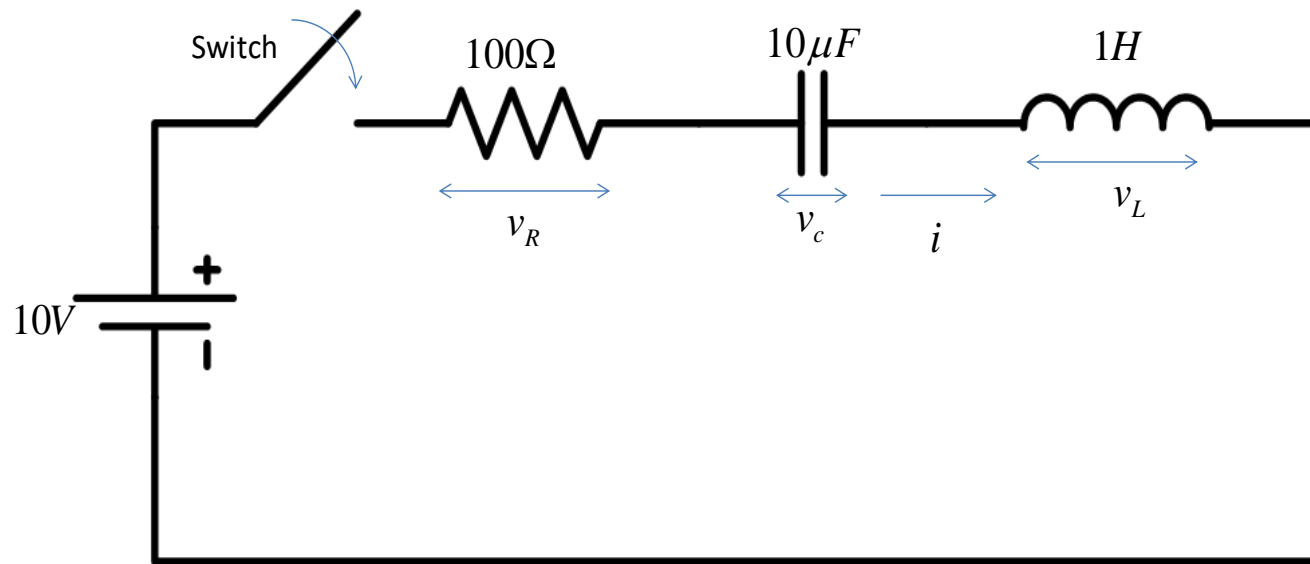a) $i(0^+)$ b) $\frac{di}{dt}(0^+)$ c) $\frac{d^2i}{dt^2}(0^+)$ d) $V_L(0^+)$ and e) $V_c(0^+)$.



a) 0 A b) 10 A/s c) -1000 A/s² d) 10 V e) 0 V

END