

EE 101ME – Electric Circuits

First order Differential Equation: $dx(t)/dt + ax(t) = b$

Can also be written as: $dx(p)/dp + ax(p) = b$

Multiplying both sides by e^{ap} gives:

$$e^{ap} dx(p)/dp + e^{ap} ax(p) = e^{ap} b$$

$$\Rightarrow d(e^{ap} x(p))/dp = e^{ap} b$$

$$\Rightarrow d(e^{ap} x(p)) = e^{ap} b dp$$

$$\Rightarrow \int_0^t d(e^{ap} x(p)) = \int_0^t e^{ap} b dp$$

$$\Rightarrow e^{ap} x(p) \big|_o^t = (b/a) e^{ap} \big|_o^t$$

Substitution of limits of integral $\Rightarrow e^{at} x(t) - x(0) = (b/a) (e^{at} - 1)$

$$\Rightarrow e^{at} x(t) = x(0) + (b/a) (e^{at} - 1)$$

Multiplying both sides of above equation by e^{-at}


$$\Rightarrow x(t) = e^{-at} x(0) + (b/a) (1 - e^{-at})$$

$$= (x(0) - b/a) e^{-at} + b/a$$

So, for a 1st order Differential Equation: $\frac{dx(t)}{dt} + a x(t) = b$

Its solution can be written as: $x(t) = (x(0) - b/a) e^{-at} + b/a$

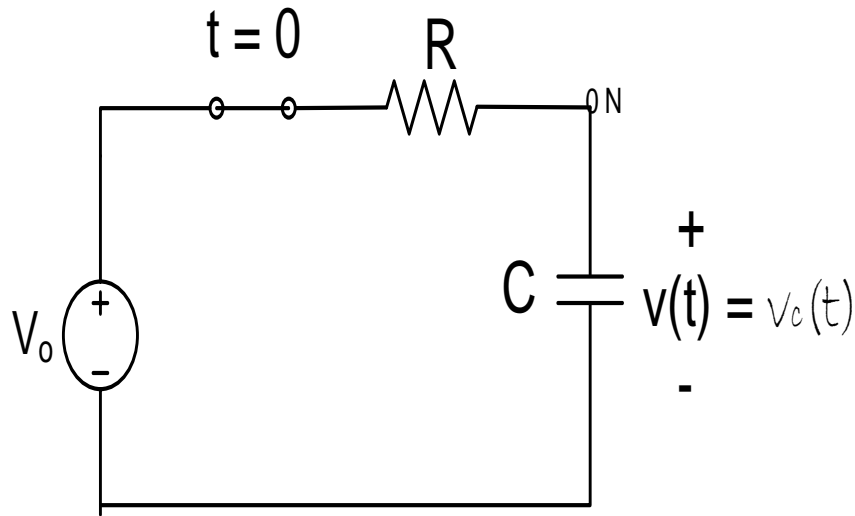RC Series Circuit: Switch is closed at time $t = 0$



Find expression for
the capacitor voltage
 $v(t)$ for $t > 0$

Solution:

Voltage at the Node N is v .

Applying KCL at a Node N: (current through the capacitor is equal to current entering the Node N)

$$\Rightarrow C \, dv(t)/dt = (V_0 - v)/R$$

Applying KCL at a Node N:

$$C \, dv(t)/dt = (V_o - v)/R$$

$$\Rightarrow dv/dt + (1/RC) \, v = (V_o/RC)$$

We know, given $dx(t)/dt + a \, x(t) = b$


its solution is $x(t) = [x(0) - (b/a)] e^{-at} + (b/a)$

For series RC circuit : After closing the switch $v(0)=v(0^-)=0$

Again, $x(t) = v(t)$, $a = 1/(RC)$ and $b = V_o/(RC)$


Then, $v(t) = v_c(t) = V_o (1 - e^{-t/(RC)})$

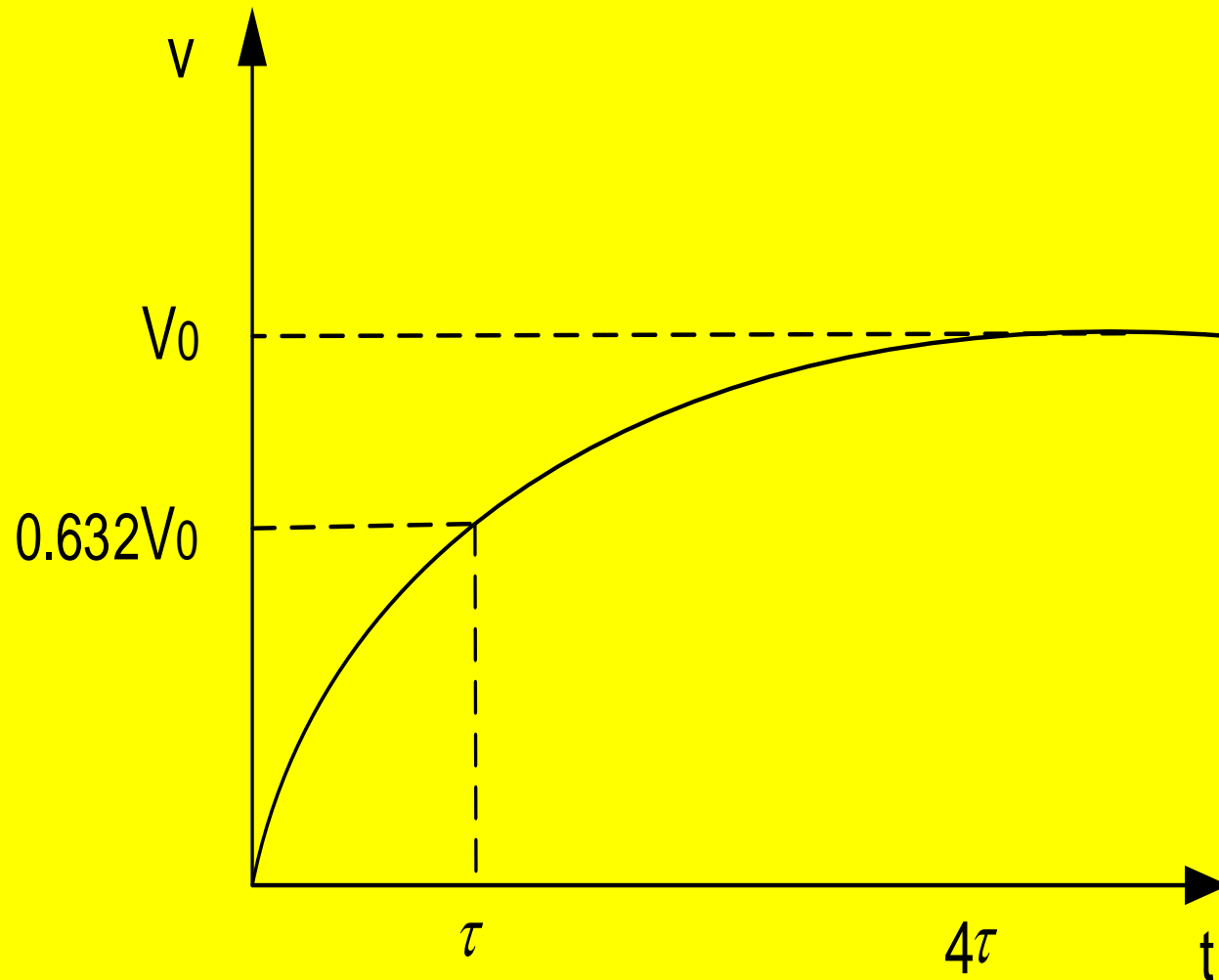Plot for the capacitor voltage after closing the switch:




Initial Conditions and RC Circuit

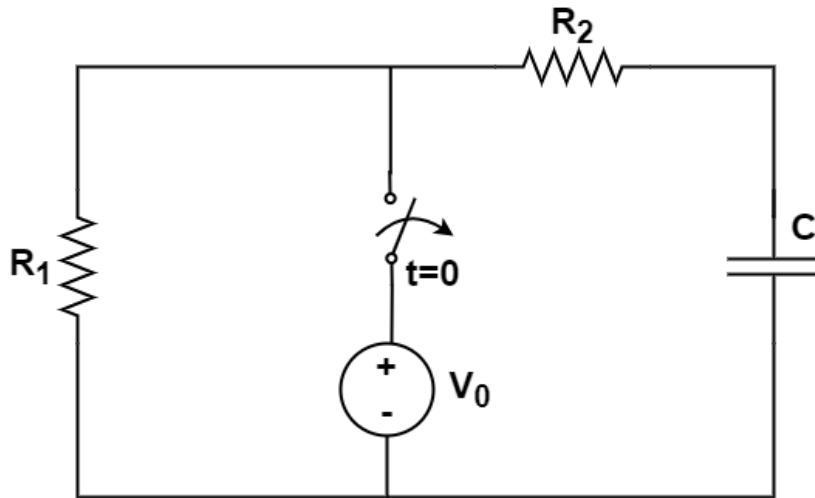The switch is connected for a long time before opening at time $t = 0$ sec



Given: $R_1 = 4$ Ohm, $R_2 = 8$ Ohm, $C = 20$ microFarad and $V_0 = 18$ V.

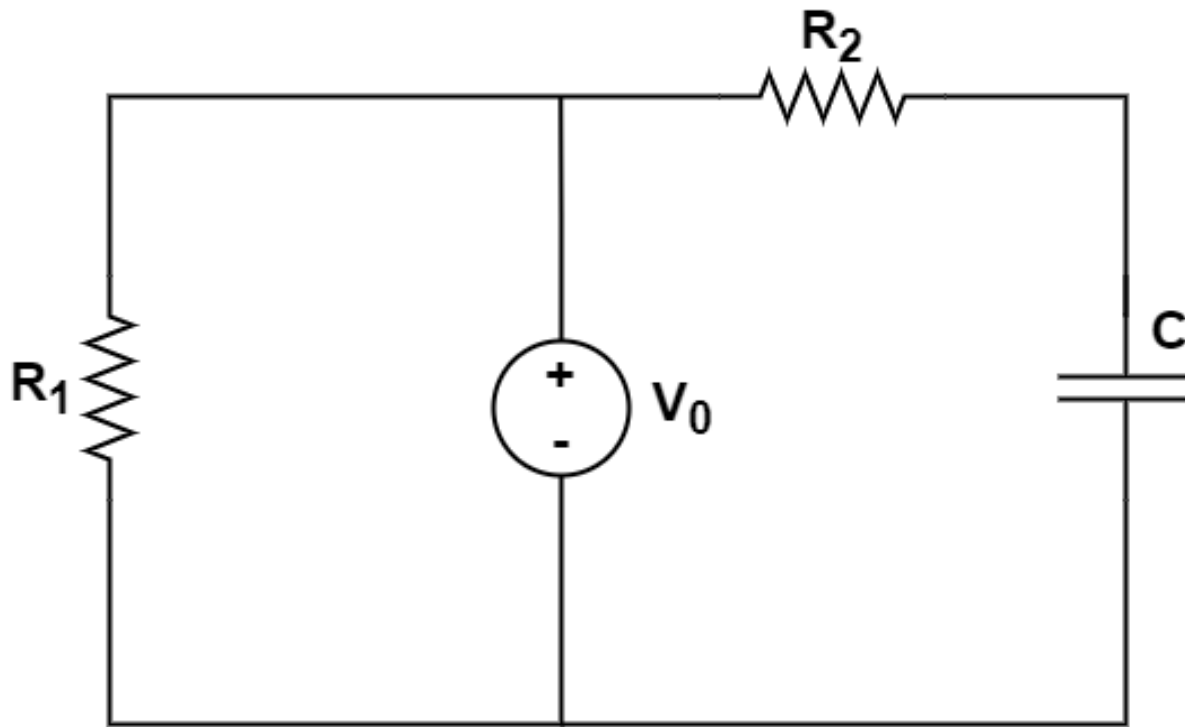Write the expression for $v_c(t)$ across the capacitor C for $t > 0$.




The circuit at $t = 0^-$ before the switch is opened

The capacitor is fully charged to $v_c(0^-) = V_0 = 18V$

since the capacitor current $i_c = C \, dv/dt = 0$ for DC V_0

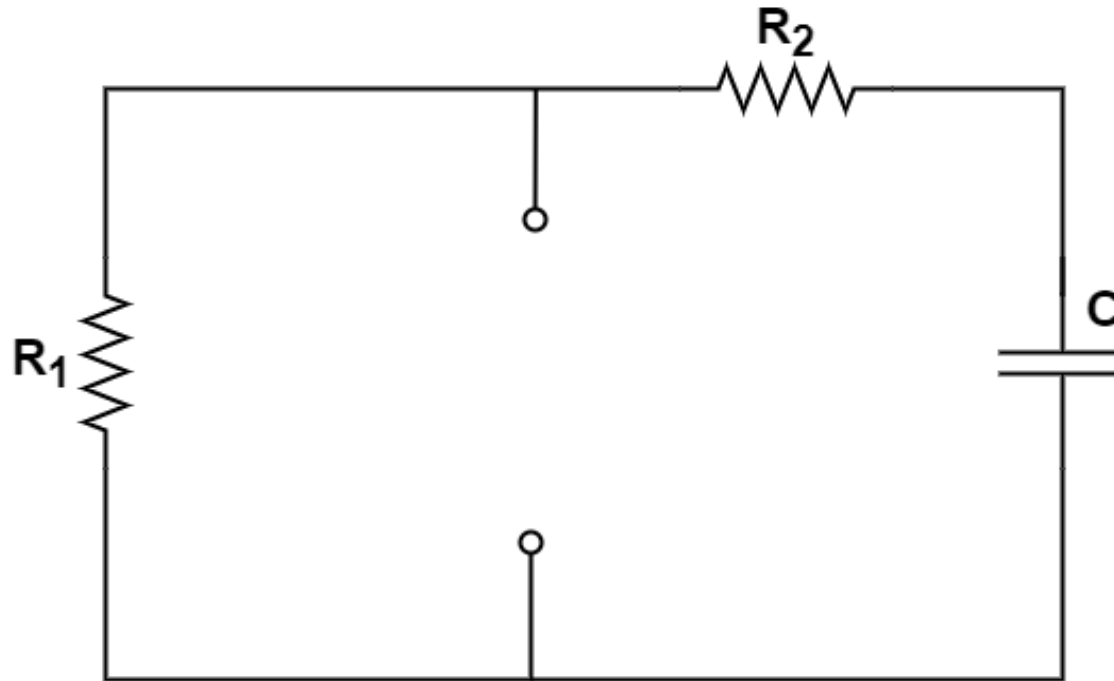The switch opens at $t = 0$. The circuit is shown for $t > 0^+$.



For series RC circuit : After opening the switch $v_c(0)=v(0^-)=18\text{ V}$

Note that there is no DC source in the above circuit, so $V_0 = 0\text{ V}$

Again, $x(t) = v_c(t)$, $a = 1/(RC)$, $R = R_1 + R_2$ and $b = V_0/(RC) = 0$

We know: $x(t) = (x(0) - b/a) e^{-at} + b/a$

Then, $v_c(t) = v_c(0) e^{-t/(RC)} = 18 e^{-4166.67 t} \text{ V}$

END