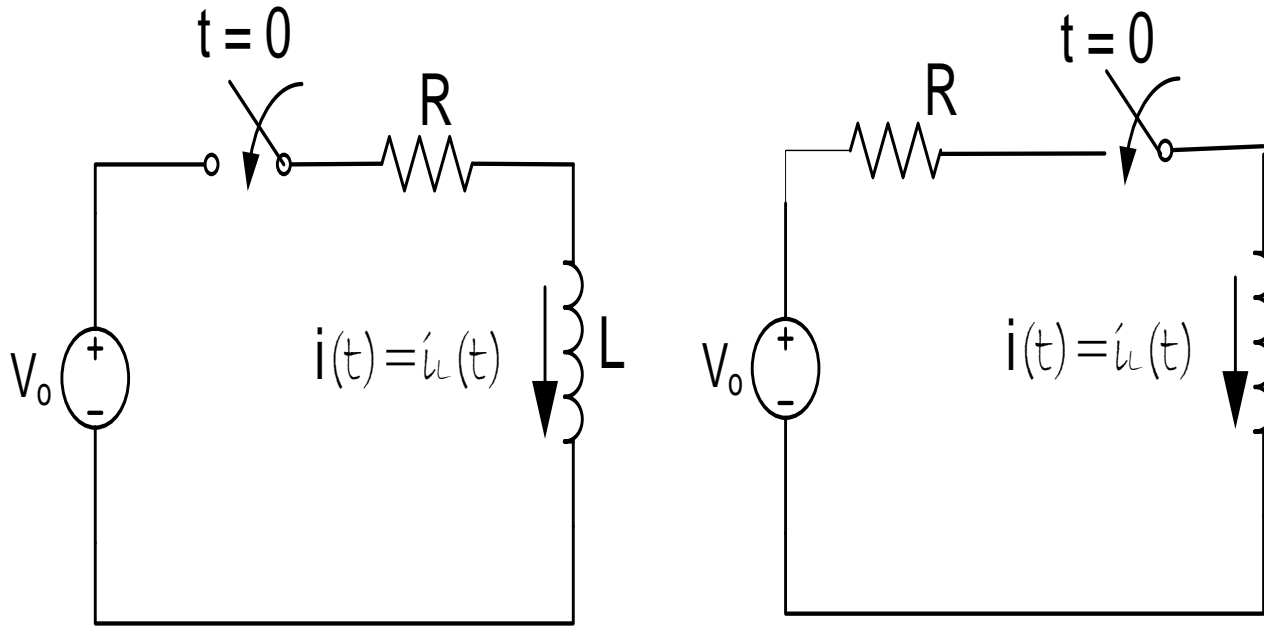


EE 101ME – Electric Circuits

Revision of RL/RC Circuits

RLC Circuits


Response of RL Series Circuit



Using Source Transform DC voltage source V_0 and series R can be replaced by


DC current source (V_0/R) and parallel R

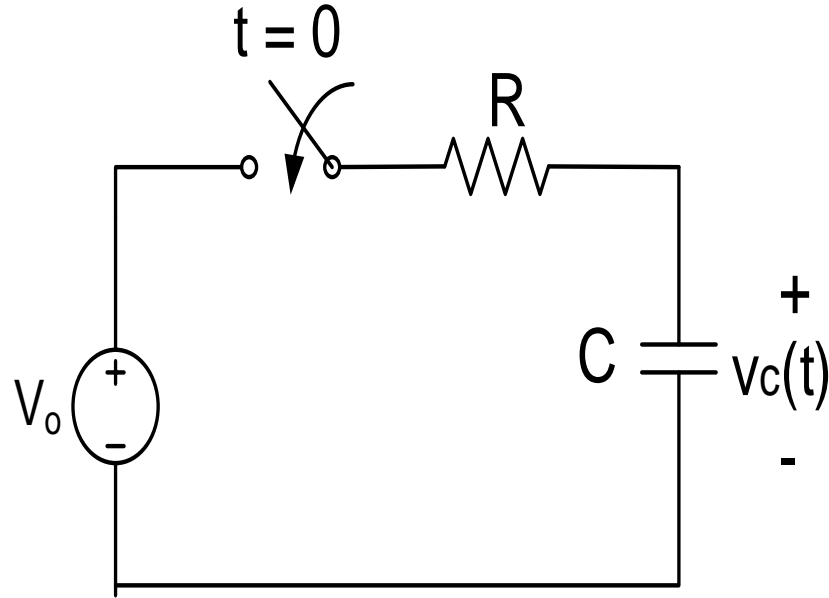Draw an equivalent circuit of the given circuit using a DC current source I_0 and rewrite the expression for $v_c(t)$.



$$v_c(t) = [v_c(0) - I_0 R] e^{-t/(RC)} + I_0 R$$

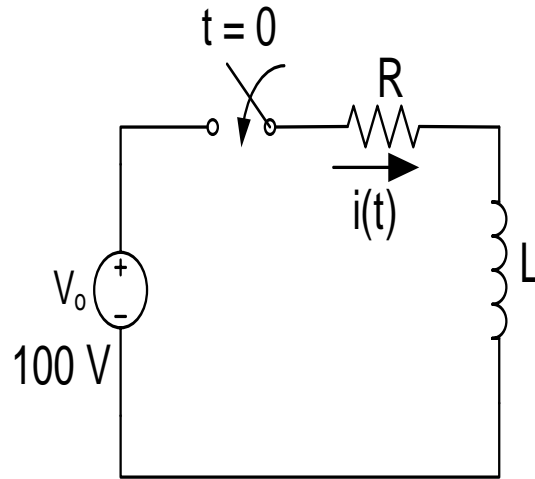
Determine R and L of the following circuit




when $i(t)=i_L(t) = 12.5(1- e^{-40t})$ A and $v_L(t) = 100 e^{-40t}$ V

$R = 8$ Ohm and $L = 0.2$ H

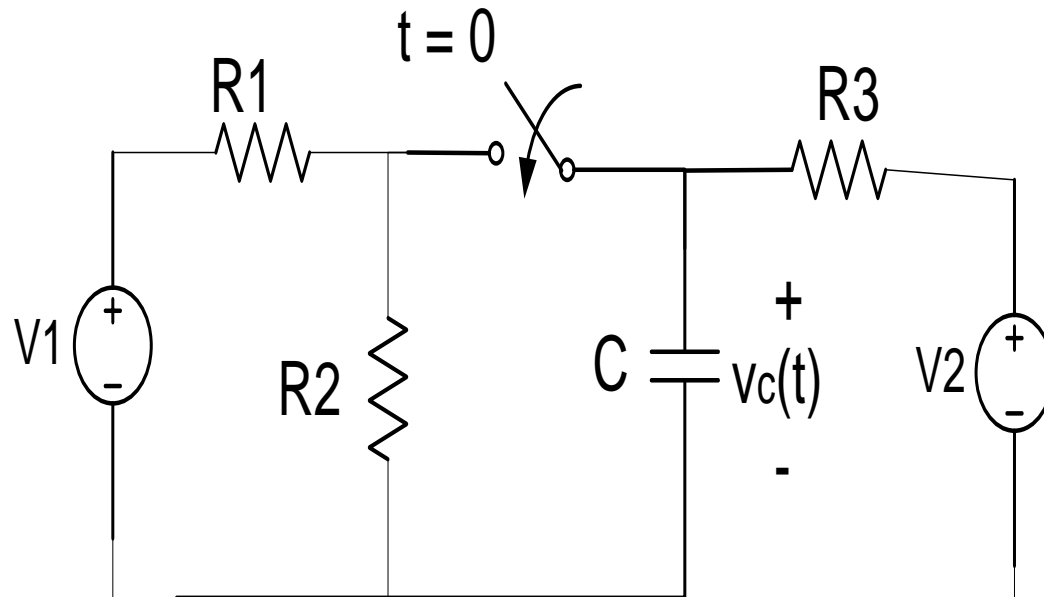The switch in the following circuit is closed at time $t = 0$ sec.
Find expression for $V_c(t)$ for $t > 0$.



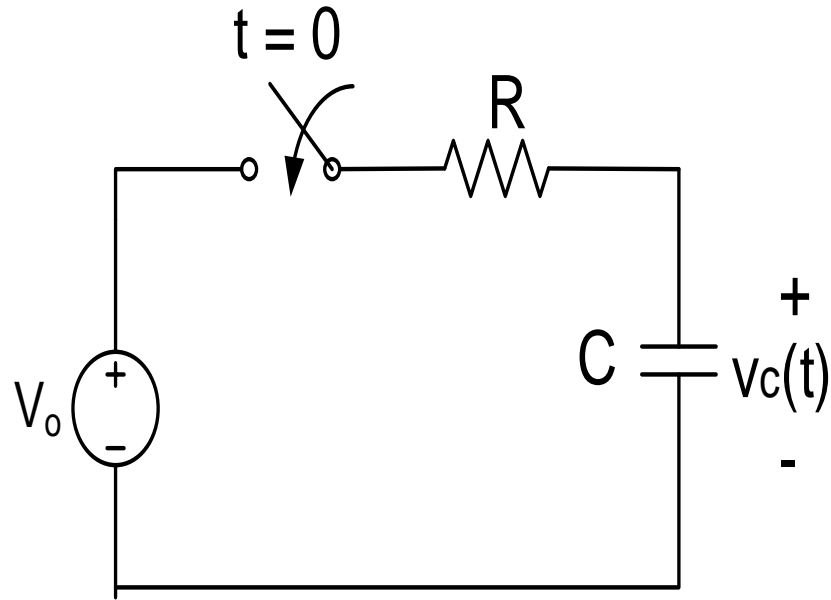


$$v_c(t) = [v_c(0) - V_0] e^{-t/(RC)} + V_0$$

$$V_c(0) = V_2, R=R_{th}= R_1||R_2||R_3, V_0=V_{th}=R(V_1/R_1 + V_2/R_3)$$

Initial Conditions and RLC Circuits

Initial Conditions

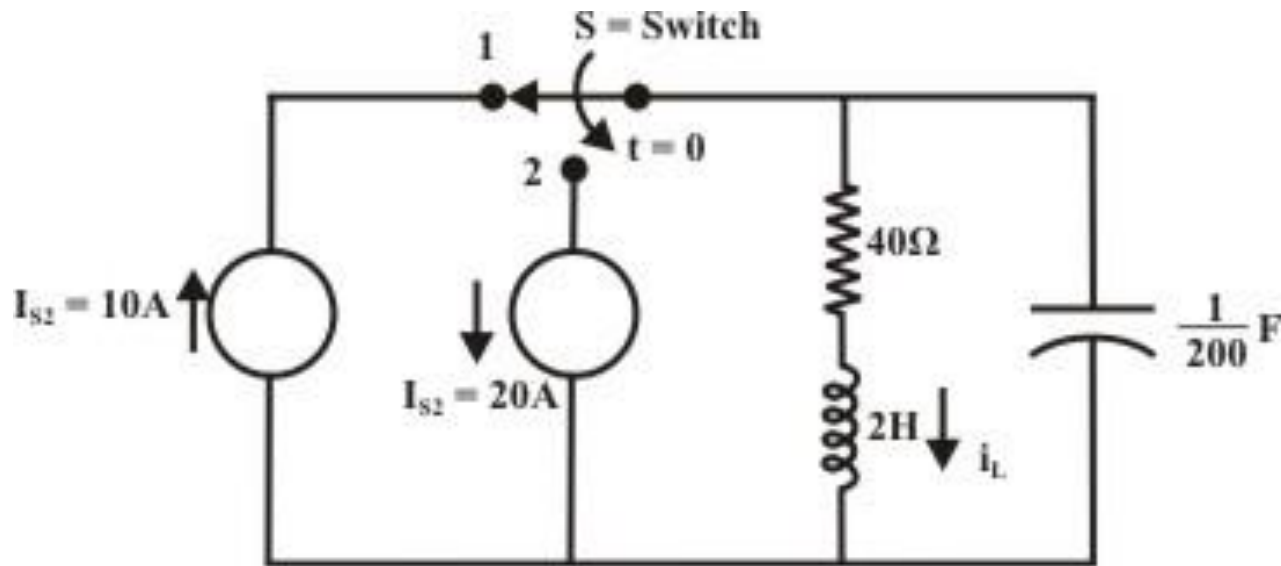Switch S is connected to Node 1 for a long time before connecting to Node 2 at time $t = 0$ sec




Values for:

(a) $i_L(0^-)$; (b) $v_c(0^+)$; (c) $v_R(0^+)$; (d) $i_L(\infty)$

Values are 10 A, 400 V, 400 V, -20 A

Before closing the switch, the energy storage elements did not have any stored energy in them. If switch is closed at $t=0$, find

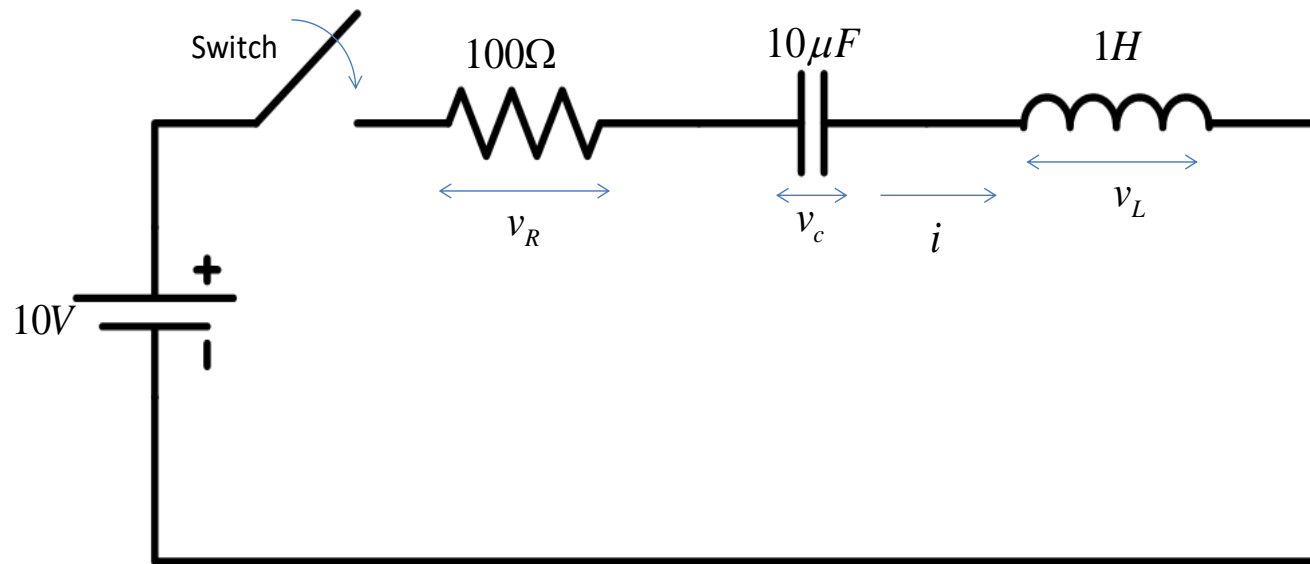
a) $i(0^+)$ b) $\frac{di}{dt}(0^+)$ c) $\frac{d^2i}{dt^2}(0^+)$ d) $V_L(0^+)$ and e) $V_c(0^+)$.



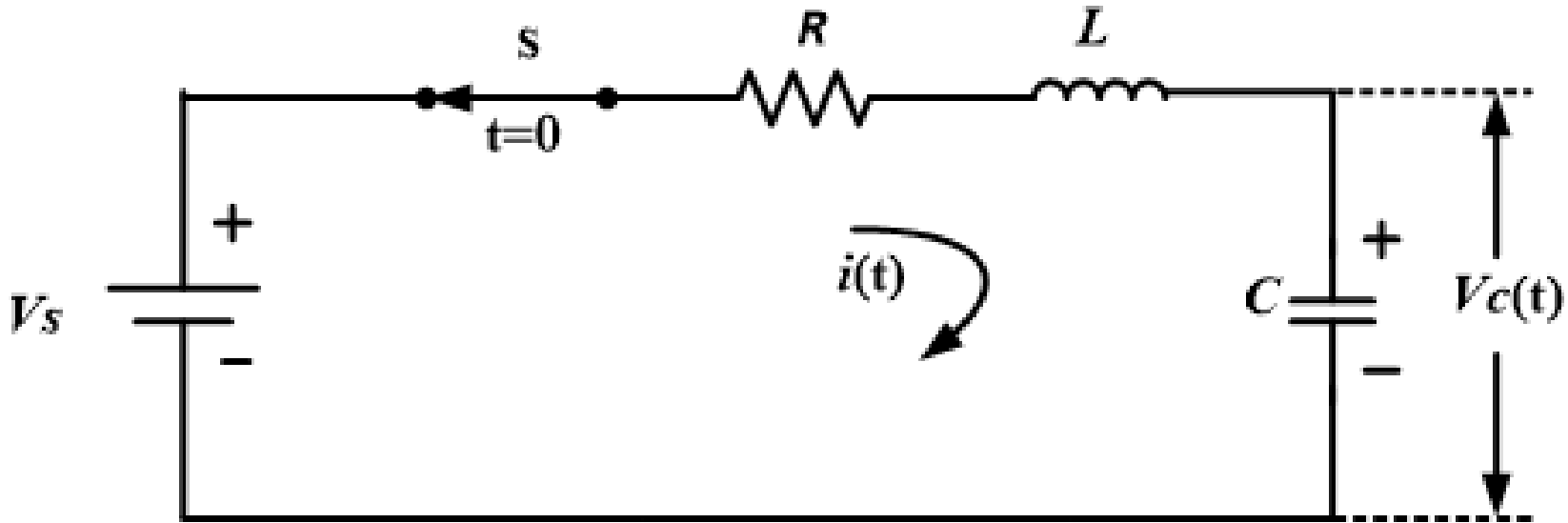a) 0 A b) 10 A/s c) -1000 A/s² d) 10 V e) 0 V

RLC Circuits

Derive an expression for $V_c(t)$ for $t > 0$.



$$\text{KVL} \Rightarrow L \frac{di(t)}{dt} + R i(t) + v_c(t) = V_s \quad \text{and} \quad i(t) = C \frac{dv_c(t)}{dt}$$

Substitution yields

$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$


Complete solution

$$v_c(t) = \left(A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} \right) + A$$

Three types of Responses

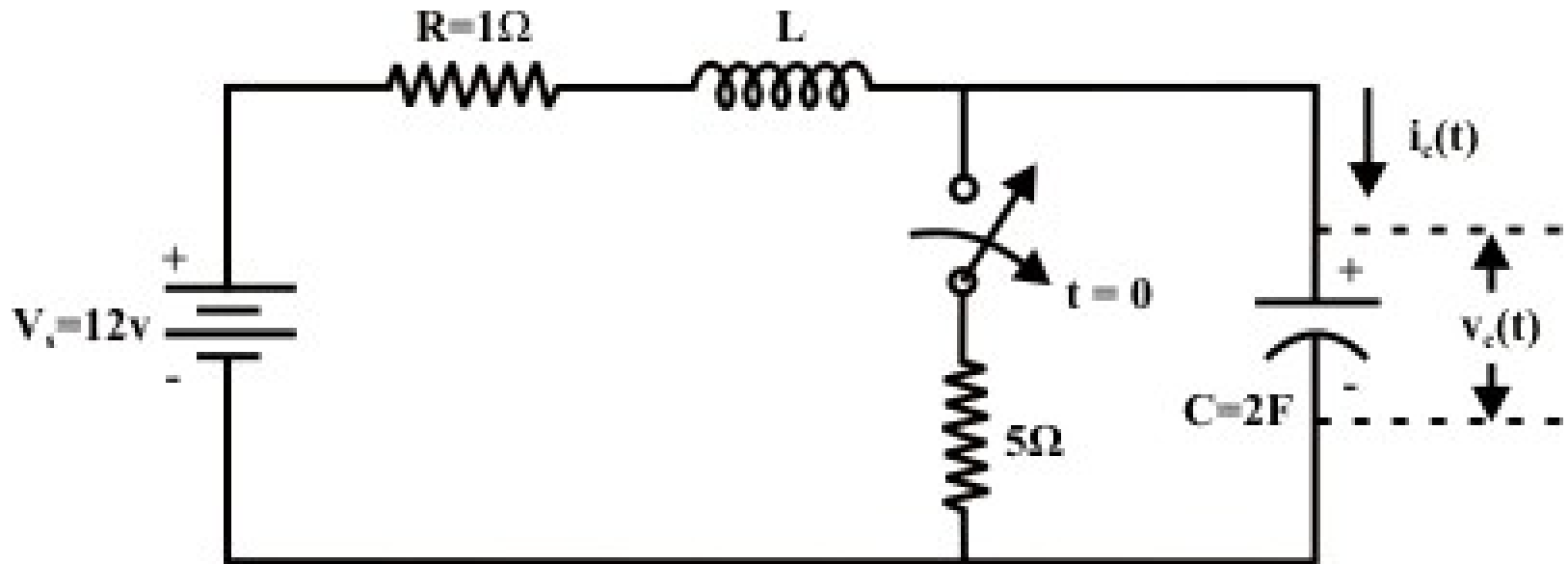Example

Switch is closed for a sufficiently long time before opening at $t=0$. Find the expression for $v_c(t)$ and $i_c(t)$. Take $L = 0.2$ H.



Solution

Initial conditions for the capacitor voltage and inductor current:

$$v_c(0^+) = v_c(0^-) = 10 \text{ V}$$

$$i_L(0^+) = i_L(0^-) = \frac{12}{1+5} = 2 \text{ A}$$

Roots are:

$$\alpha_1 = -0.563; \quad \alpha_2 = -4.436$$

General expression for the capacitor voltage for $t > 0$ is

$$v_c(t) = A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} + A = A_1 e^{-0.563t} + A_2 e^{-4.436t} + A$$

and

$$\frac{dv_c(t)}{dt} = \alpha_1 A_1 e^{\alpha_1 t} + \alpha_2 A_2 e^{\alpha_2 t} = -0.563 A_1 e^{\alpha_1 t} - 4.436 A_2 e^{\alpha_2 t}$$


Using initial conditions

$$A_1 = -2.032, A_2 = 0.032 \text{ and } A = 12$$

$$v_c(t) = -2.032 e^{-0.563t} + 0.032 e^{-4.436t} + 12, \text{V}$$

$$i_c(t) = C \frac{dv_c(t)}{dt} = 2(1.144e^{-0.563t} - 0.144e^{-4.436t}), \text{A}$$

Draw the plots for capacitor voltage for 20 sec

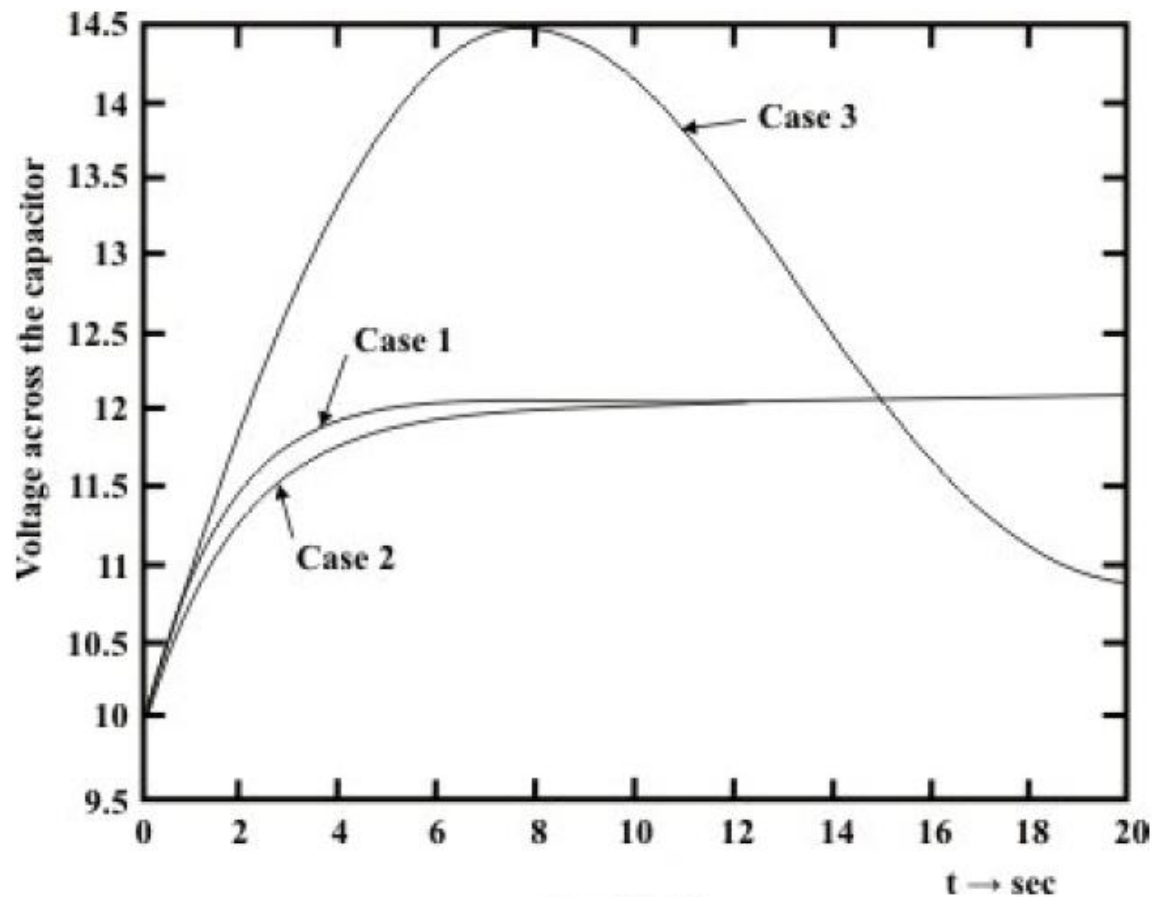

Case 1:
 $L = 0.5 \text{ H}$

Case 2:
 $L = 0.2 \text{ H}$

Case 3:
 $L = 0.8 \text{ H}$

END