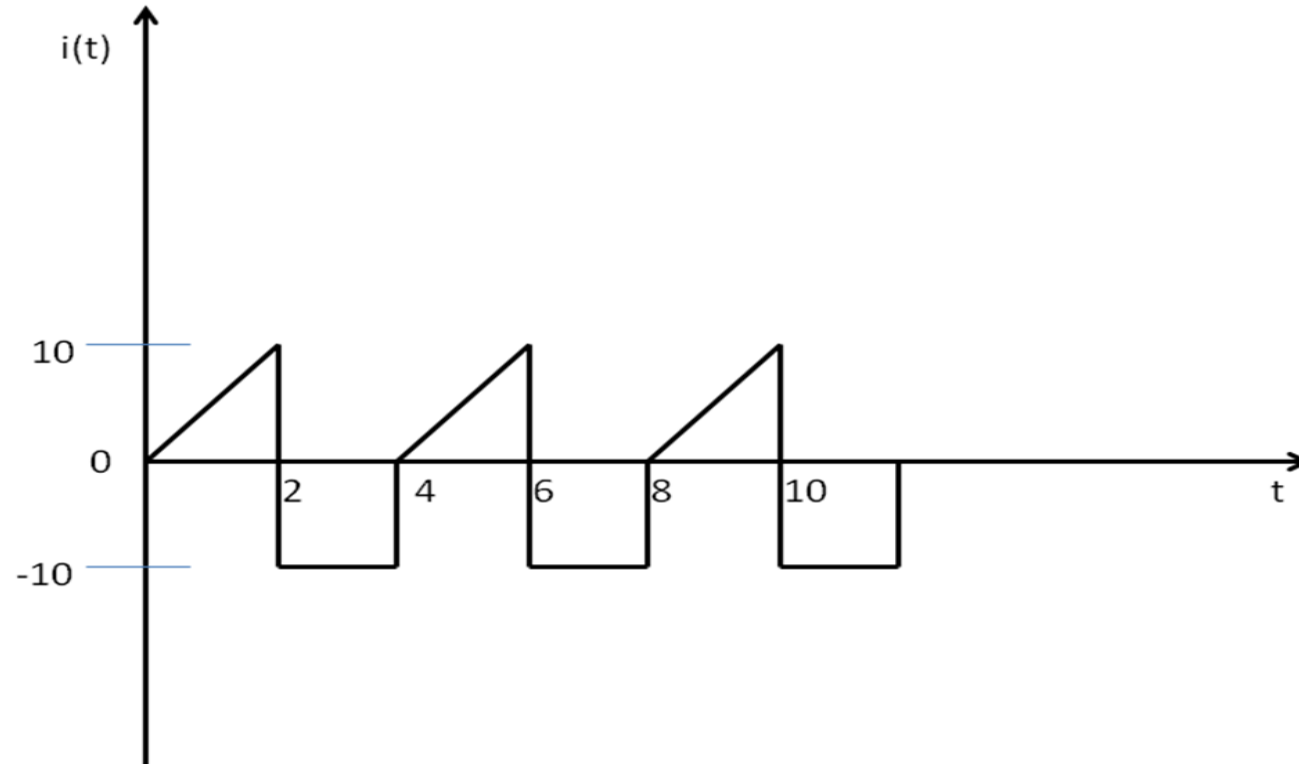


EE 1102H – Electric Circuits

AC Circuits

Practice Problems

Q1. Determine the rms value of the current waveform in the following **Figure**.



If the current is passed through a 2 Ohm resistor, find the average power absorbed by the resistor.

Solution: The period of the waveform is $T=4$.

Over a period, the current waveform can be written as

$$i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$$

The rms value is

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]} \\ &= \sqrt{\frac{1}{4} \left[25 \frac{t^3}{3} \right]_0^2 + [100t]_2^4} = 8.165 A \end{aligned}$$

The power absorbed by 2 Ohm resistor is

$$P = I_{rms}^2 R = (8.165)^2 (2) = 133.3 W$$

Also, let $p(t)$ be the instantaneous power.

Power absorbed by the resistor

= Real power

= Average power


$$= \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T i(t)^2 R dt$$

Substituting T , $i(t)$ and R of the previous page in the above formula and simplifying, we get

$$\text{Average power} = \frac{400}{3} W$$

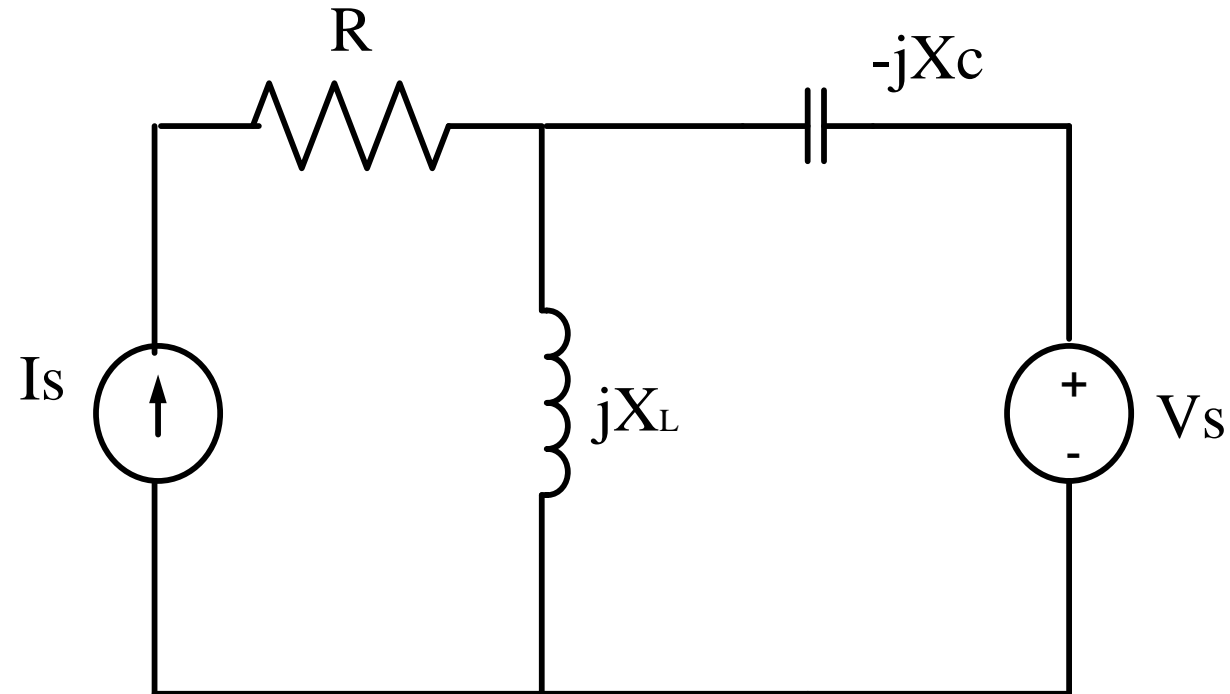
Q2. Find voltage across the current source and current through the inductor in the following circuit.



Given $I_s = 5 \sin \omega t$ A and $V_s = 55 \sin (\omega t + 30^\circ)$ V

$R = 5 \text{ Ohm}$ $X_L = 10 \text{ Ohm}$ and $X_C = 5 \text{ Ohm}$

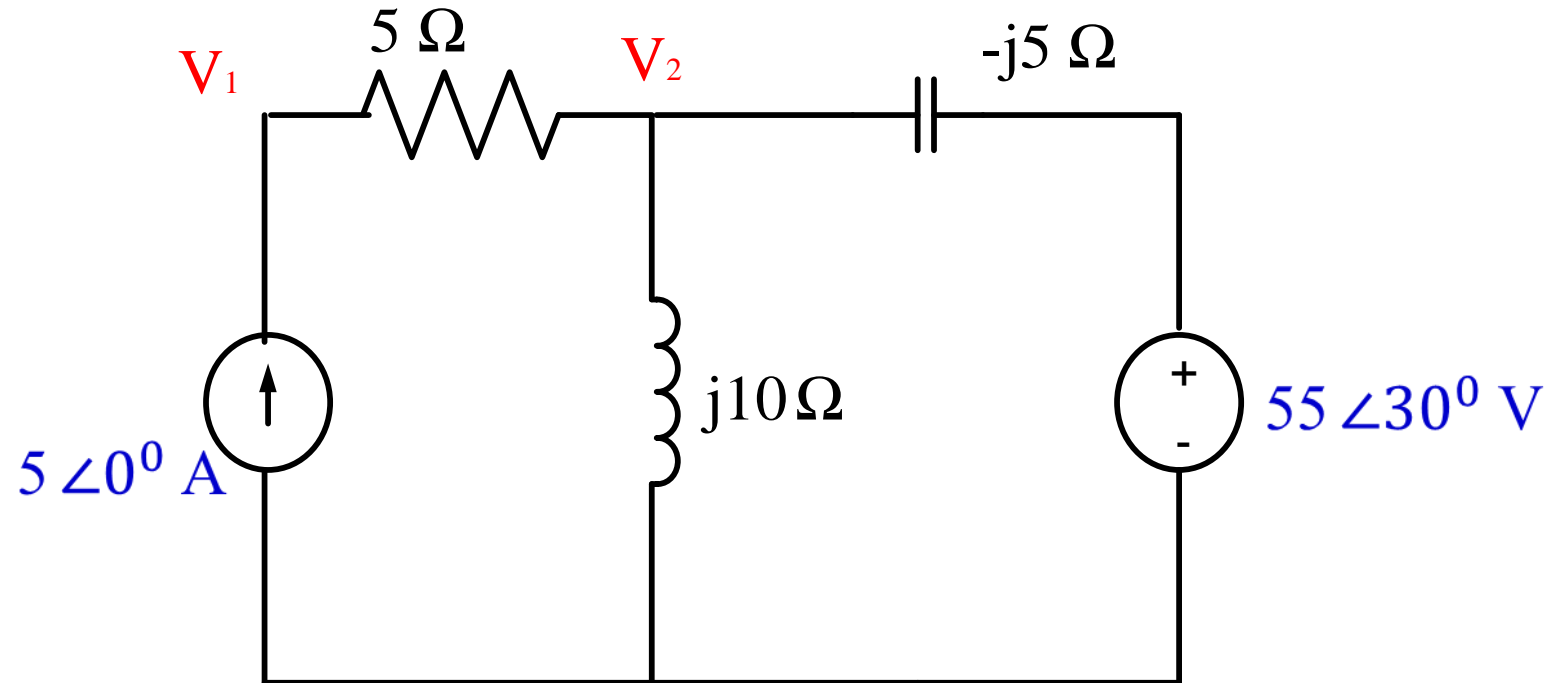Solution : Redraw the circuit using phasors



Hints : $A \angle \theta = A (\cos \theta + j \sin \theta) = A e^{j\theta}$; polar to rectangular form conversion

$$5\angle 0^\circ + \frac{55\angle 30^\circ - V_2}{-j5} = \frac{V_2}{j10}$$

$$\Rightarrow j50 - 2(55\angle 30^\circ - V_2) = V_2$$

$$\Rightarrow V_2 = 95.263 + j5$$

$$I_L = V_2 / (j10) = 0.5 - j9.5263 = 9.5394 \angle -87^\circ$$

$$i_L(t) = 9.5394 \sin(\omega t - 87^\circ) \text{ A}$$

Voltage across the current source:

$$\begin{aligned} V_1 &= 5X5 + V_2 = 120.263 + j5 \\ &= 120.367 \angle 2.381^\circ \end{aligned}$$

$$v_1(t) = 120.367 \sin(\omega t + 2.381^\circ) \text{ V}$$

Verify your answers using some other circuit analysis techniques

END