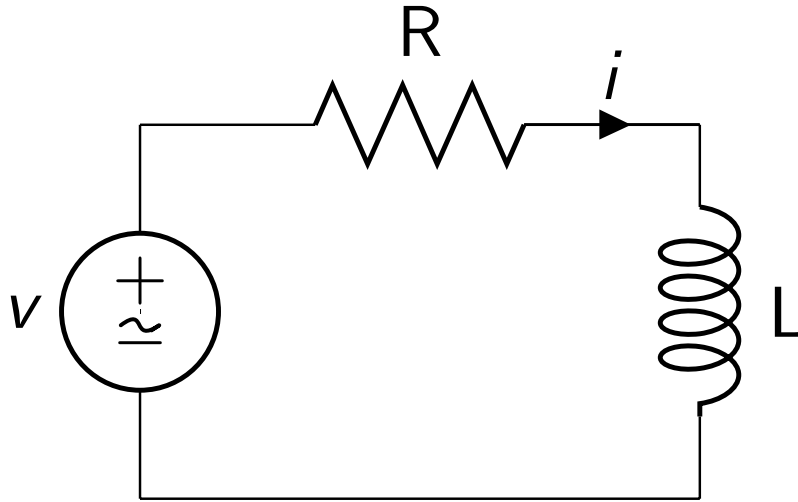


# EE 1102H – Electric Circuits

# Instantaneous Power, Average Power Complex Power, Apparent Power and Power Factor

# Instantaneous Power



Let  $v = V_m \sin(\omega t + \theta)$

Then  $i = I_m \sin(\omega t + \phi)$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \text{ and } \phi = -\tan^{-1} \frac{\omega L}{R} + \theta$$

$$p(t) = v(t)i(t)$$

$$p(t) = V_m \sin(\omega t + \theta) I_m \sin(\omega t + \phi)$$




$$p(t) = \frac{V_m I_m}{2} (\cos(\theta - \phi) - \cos(2\omega t + \theta + \phi))$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) - \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

$$\text{Average Power} = \frac{1}{T} \int_0^T p(t) dt = P$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

# SERIES R-L CIRCUIT

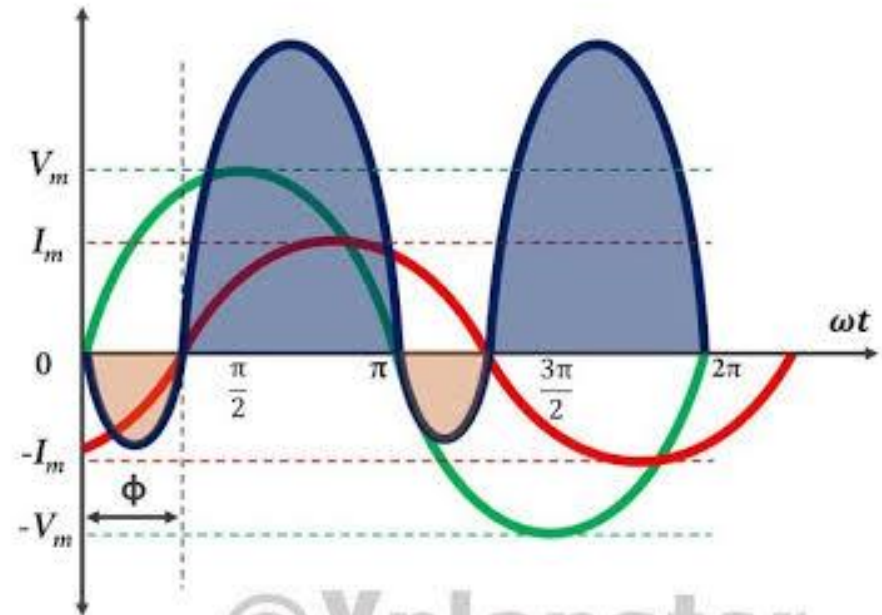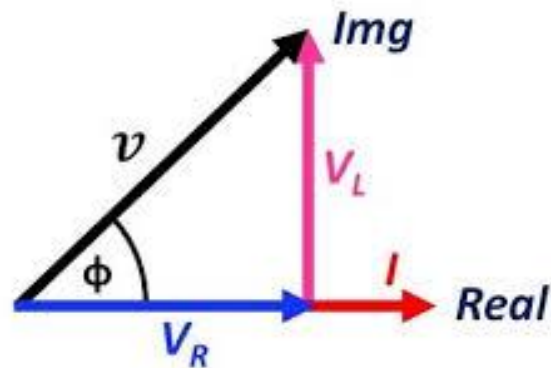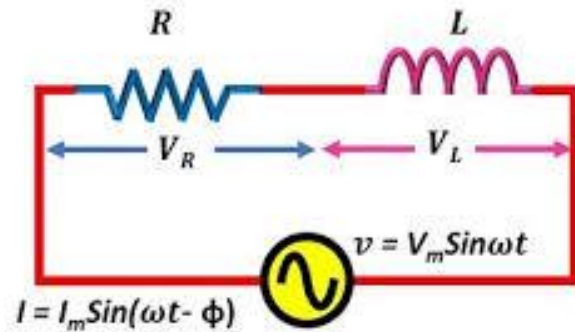


$$v = V_R + jV_L$$



$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

# Power in Pure Inductor

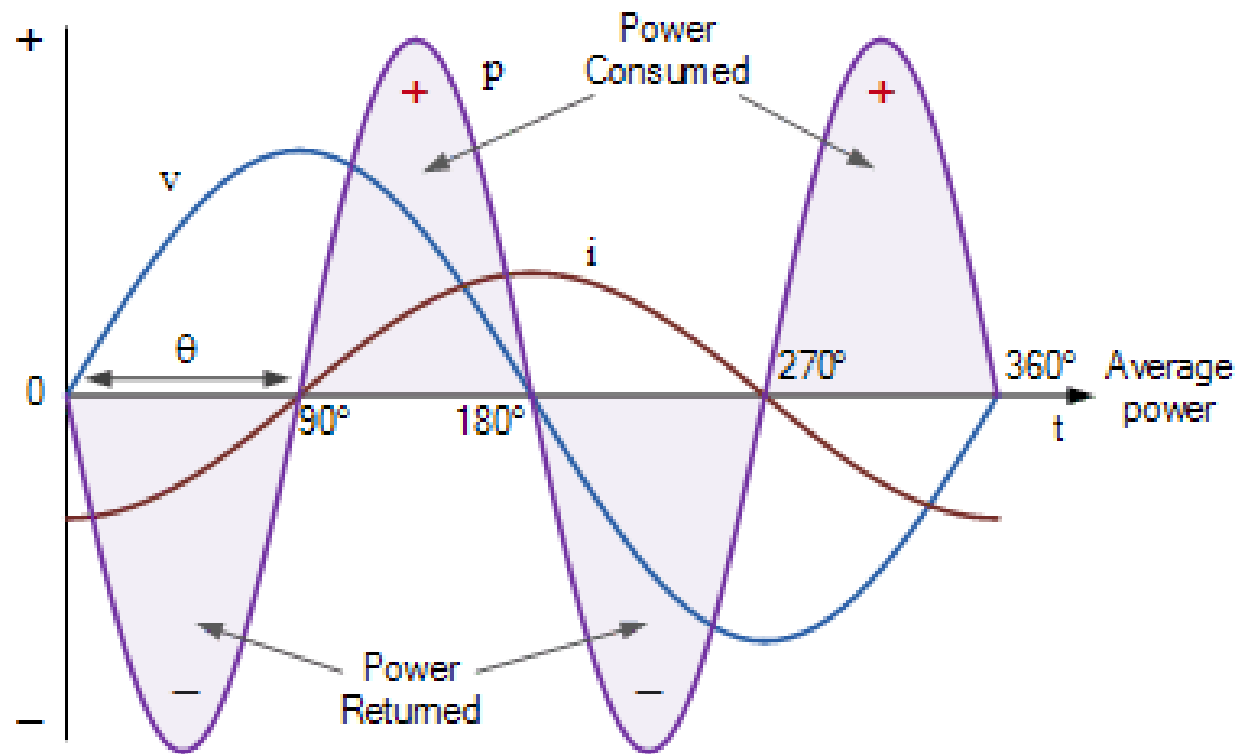

# Average Power


Resistor:  $V_m$  and  $I_m$  are in phase.

$$P = \frac{1}{2} V_m I_m \cos(0) = \frac{1}{2} V_m I_m$$

Ideal Inductor :  $V_m$  leads  $I_m$  by  $90^\circ$ .

$$P = \frac{1}{2} V_m I_m \cos(90^\circ) = 0$$

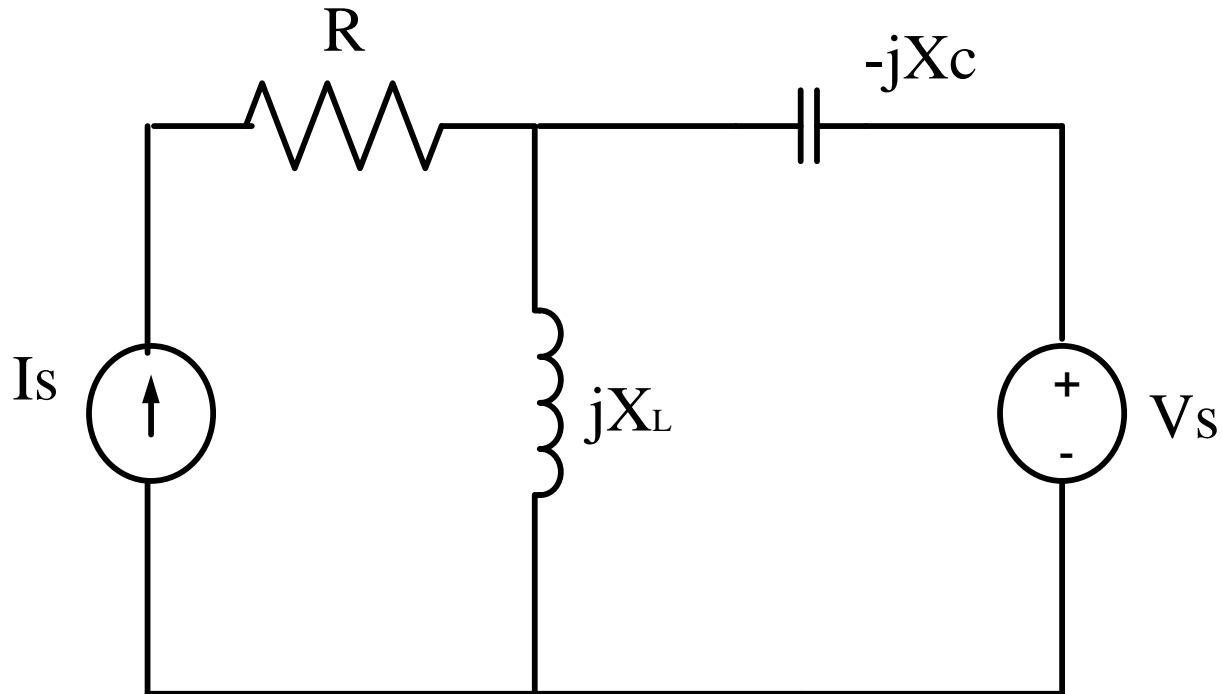Find power delivered by the current source




Given  $I_S = 5 \angle 0^\circ$  A;  $V_S = 55 \angle 30^\circ$  V;  $R = 5$  Ohm

$X_L = 10$  Ohm and  $X_C = 5$  Ohm



## Solution

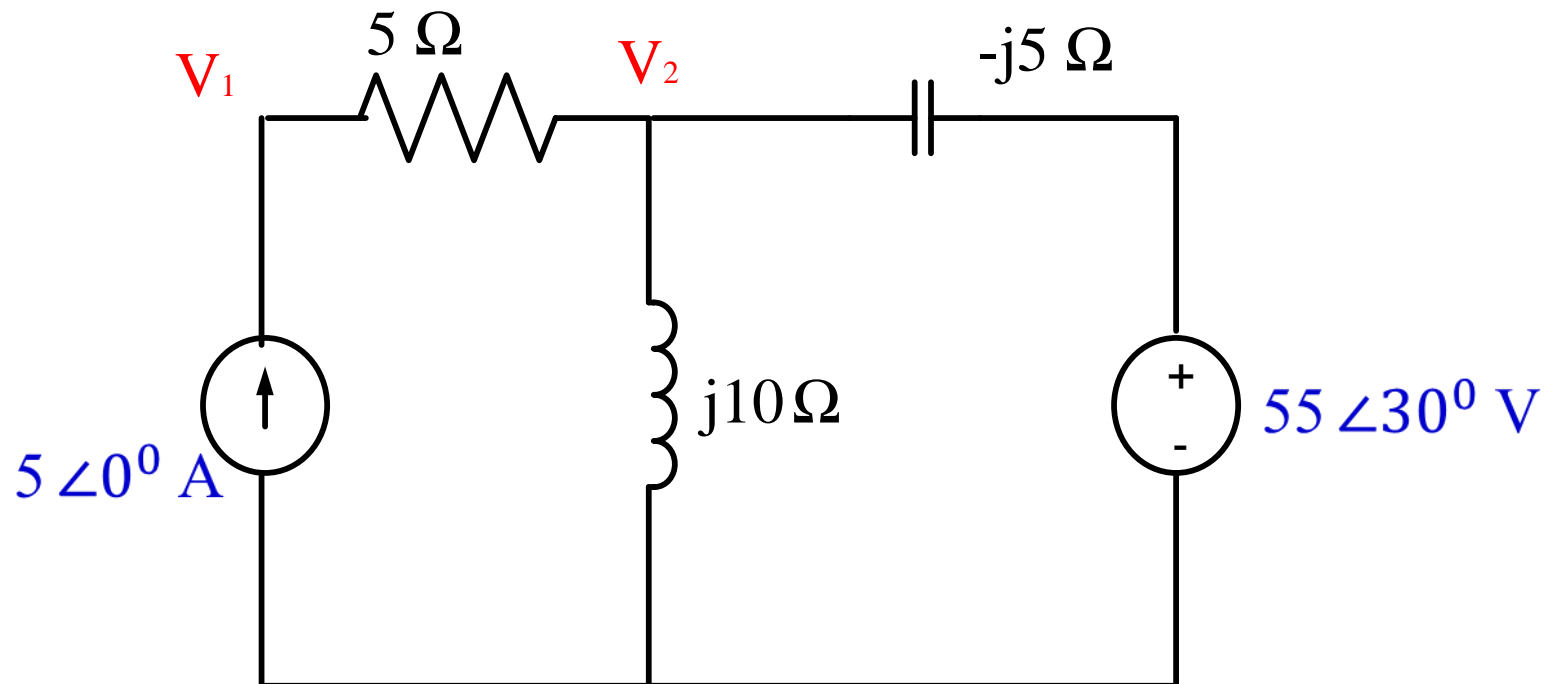

$$5\angle 0^0 + \frac{55\angle 30^0 - V_2}{-j5} = \frac{V_2}{j10}$$

$$\Rightarrow j50 - 2(55\angle 30^0 - V_2) = V_2$$

$$\Rightarrow V_2 = 95.263 + j5$$

But,

$$\begin{aligned} V_1 &= 5X5 + V_2 = 120.263 + j5 \\ &= 120.367 \angle 2.381^\circ \end{aligned}$$

Therefore, power delivered by the Current source =

$$V_1 I_s \cos(\angle V_1 - \angle I_s)$$

$$= \frac{1}{2} V_m I_m \cos(2.381^\circ - 0)$$

$$= (\frac{1}{2}) \times 120.367 \times 5 \times \cos(2.381^\circ) = 300.66 \text{ W}$$


# Average or Real Power

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = VI \cos(\theta - \phi)$$


where

$$V = \frac{V_m}{\sqrt{2}}, \quad I = \frac{I_m}{\sqrt{2}}$$

# Impedance and Power Triangle

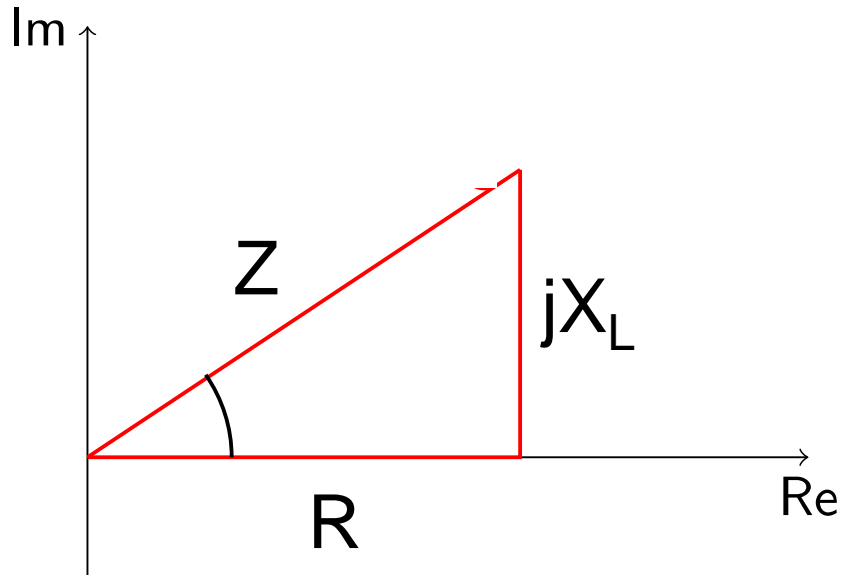


$$\text{Impedance } Z = R + j X_L$$

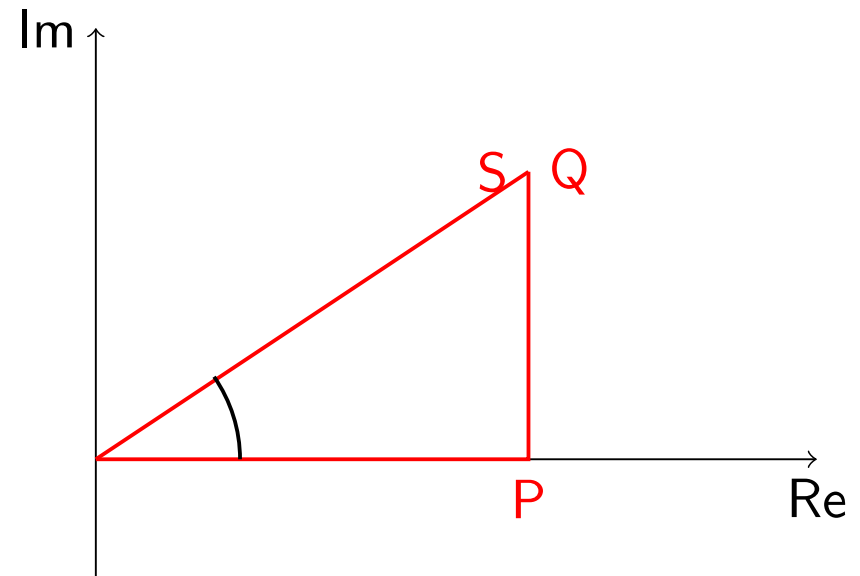

$$\begin{aligned} P &= I^2 R \text{ in W,} \\ Q &= I^2 X_L \text{ in VAR} \\ S &= VI \text{ in VA} \end{aligned}$$

# Power Triangle

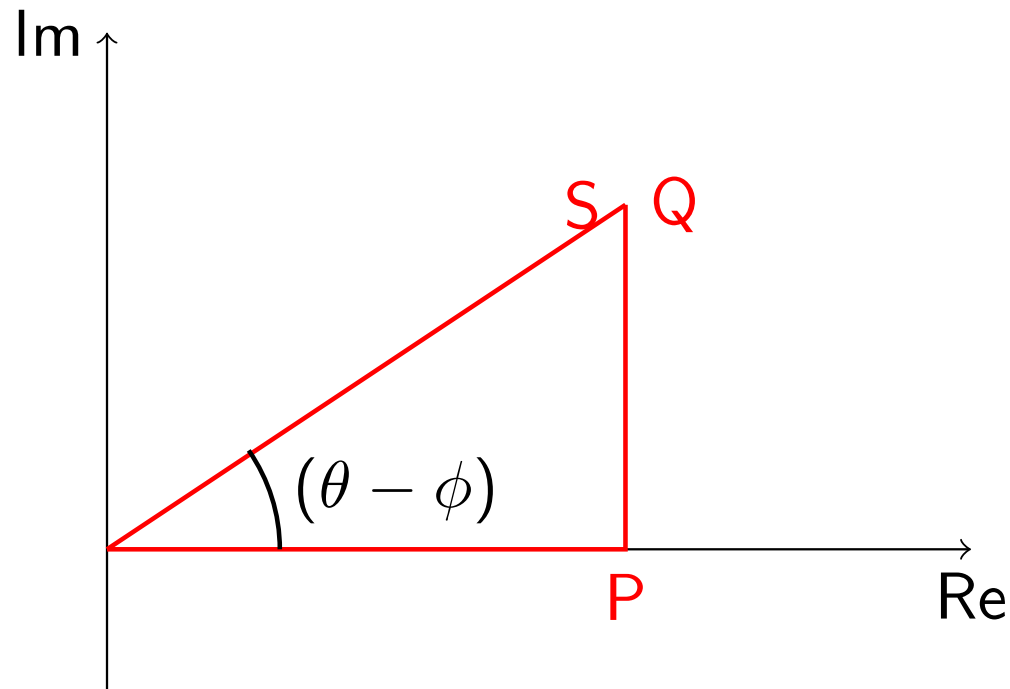

$$\mathbf{S} = VI \cos(\theta - \phi) + jVI \sin(\theta - \phi)$$

P = Real power in W, Q = Reactive power in VAR

# Complex Power

$$\begin{aligned}\mathbf{S} &= VI \cos(\theta - \phi) + jVI \sin(\theta - \phi) \\ &= VI \angle(\theta - \phi) = V \angle \theta \ I \angle -\phi\end{aligned}$$

Phasor voltage and current in RMS are

$$\mathbf{V} = V \angle \theta, \quad \mathbf{I} = I \angle \phi$$

Then the complex power is

$$\mathbf{S} = \mathbf{V} \mathbf{I}^*$$

# Apparent Power


Magnitude of complex power is called the apparent power

$$|S| = VI$$


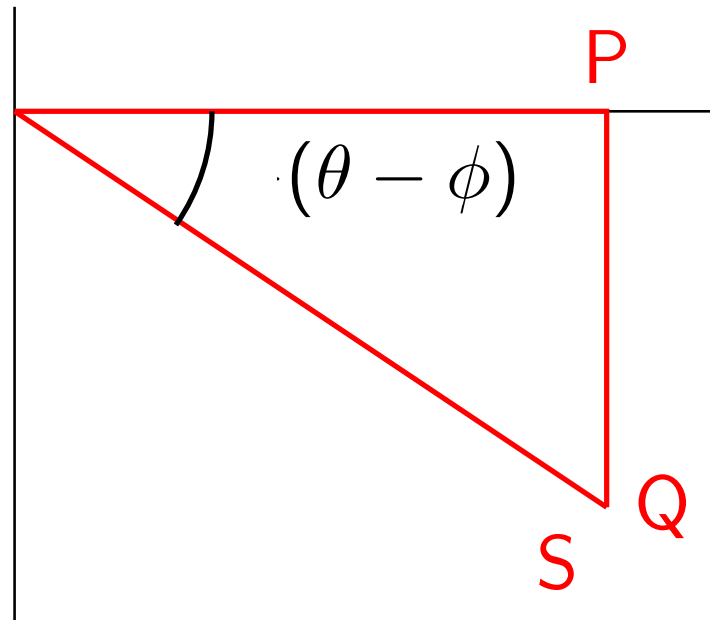
# Test

- Draw the power triangle of a RC load connected to a sinusoidal source



END