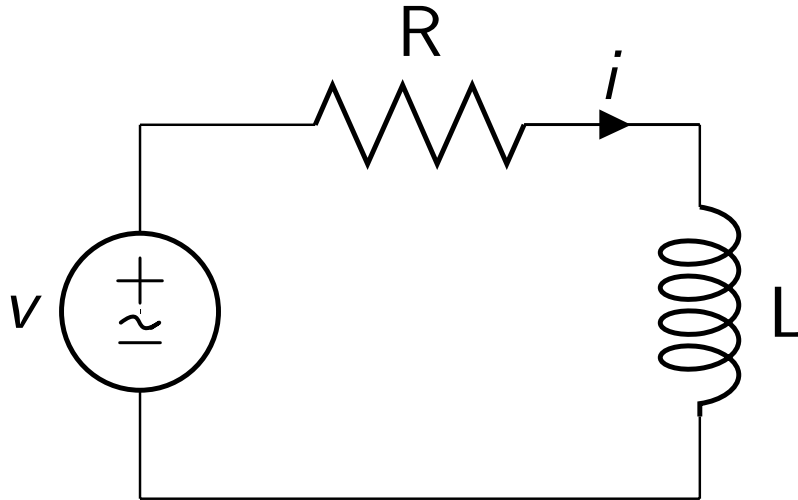


EE 1102H – Electric Circuits

Reviews of Instantaneous Power,
Average Power
Apparent Power

Power Factor (PF)
PF improvement

Instantaneous Power



Let $v = V_m \sin(\omega t + \theta)$

Then $i = I_m \sin(\omega t + \phi)$

$$I_m = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \text{ and } \phi = -\tan^{-1} \frac{\omega L}{R} + \theta$$

$$\Rightarrow \theta - \phi = \tan^{-1} \frac{\omega L}{R}$$

$$p(t) = v(t)i(t)$$

$$p(t) = V_m \sin(\omega t + \theta) I_m \sin(\omega t + \phi)$$




$$p(t) = \frac{V_m I_m}{2} (\cos(\theta - \phi) - \cos(2\omega t + \theta + \phi))$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) - \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

$$\text{Average Power} = \frac{1}{T} \int_0^T p(t) dt = P$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

SERIES R-L CIRCUIT

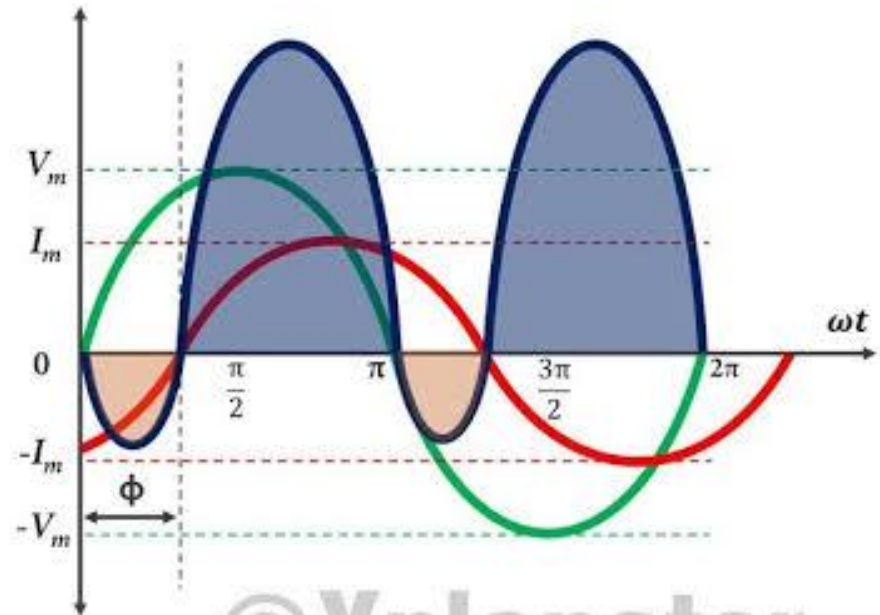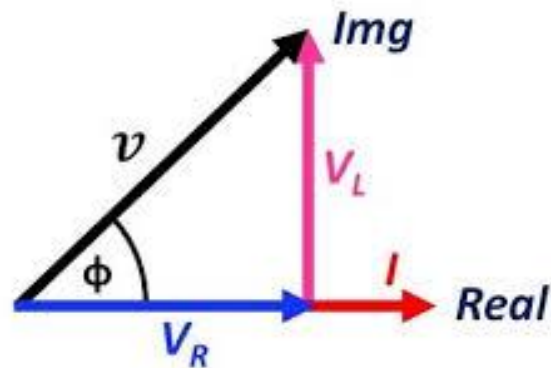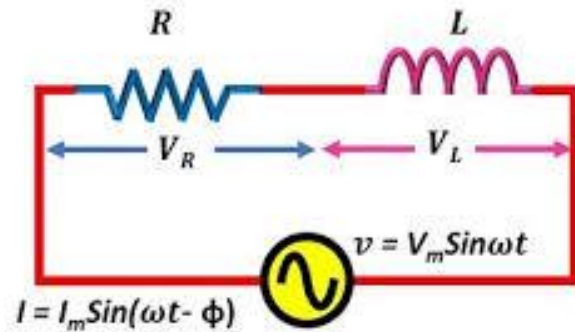


$$v = V_R + jV_L$$



$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

Power in Pure Inductor

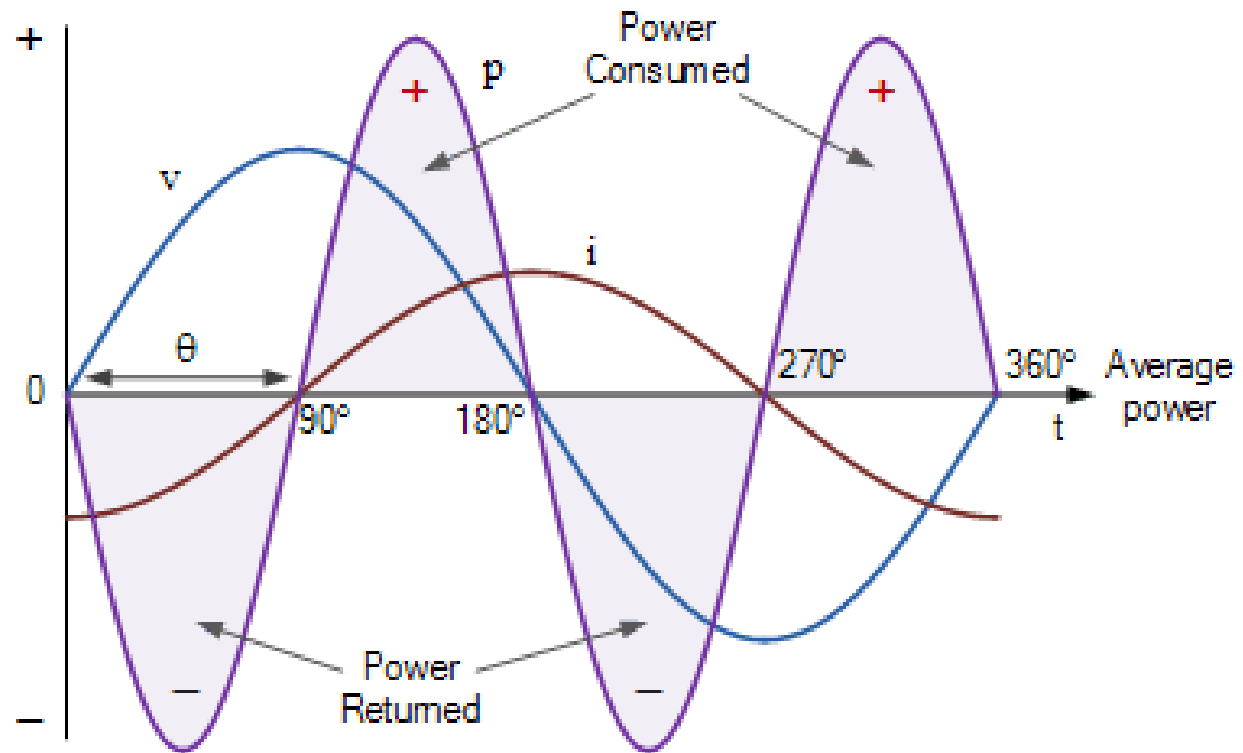

Average Power


Resistor: V_m and I_m are in phase.

$$P = \frac{1}{2} V_m I_m \cos(0) = \frac{1}{2} V_m I_m$$

Ideal Inductor : V_m leads I_m by 90° .

$$P = \frac{1}{2} V_m I_m \cos(90^\circ) = 0$$

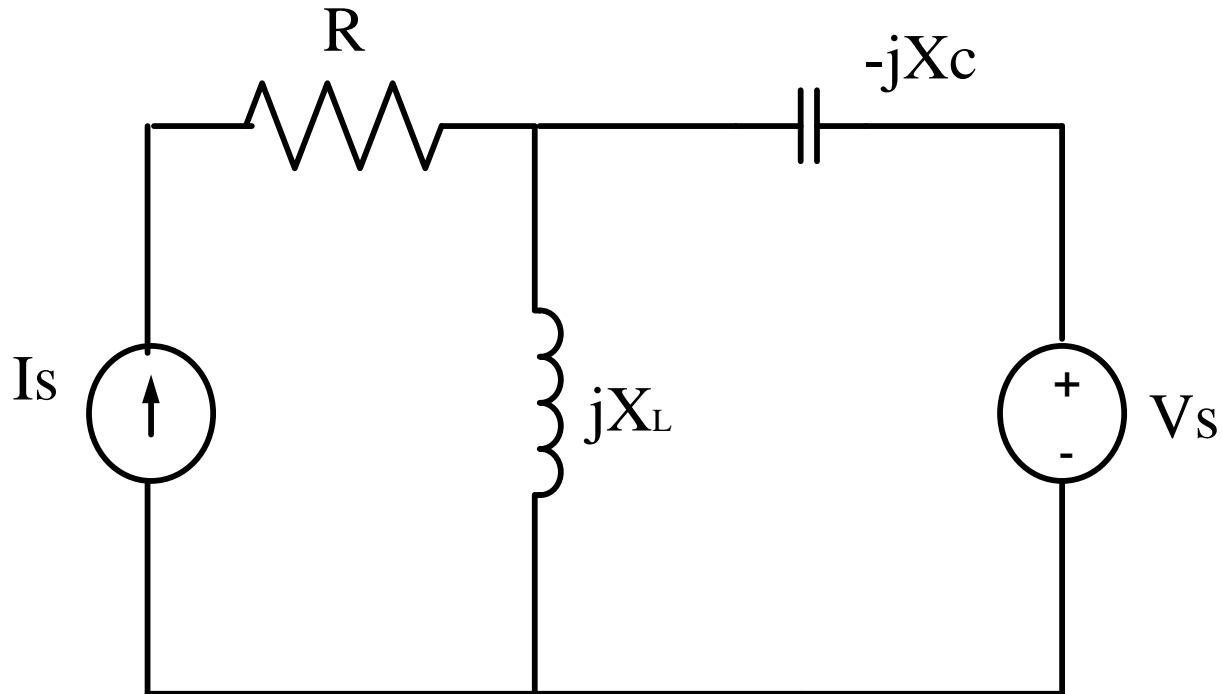
Find power delivered by the current source



Given $I_S = 5 \angle 0^\circ$ A; $V_S = 55 \angle 30^\circ$ V; $R = 5$ Ohm

$X_L = 10$ Ohm and $X_C = 5$ Ohm

Solution

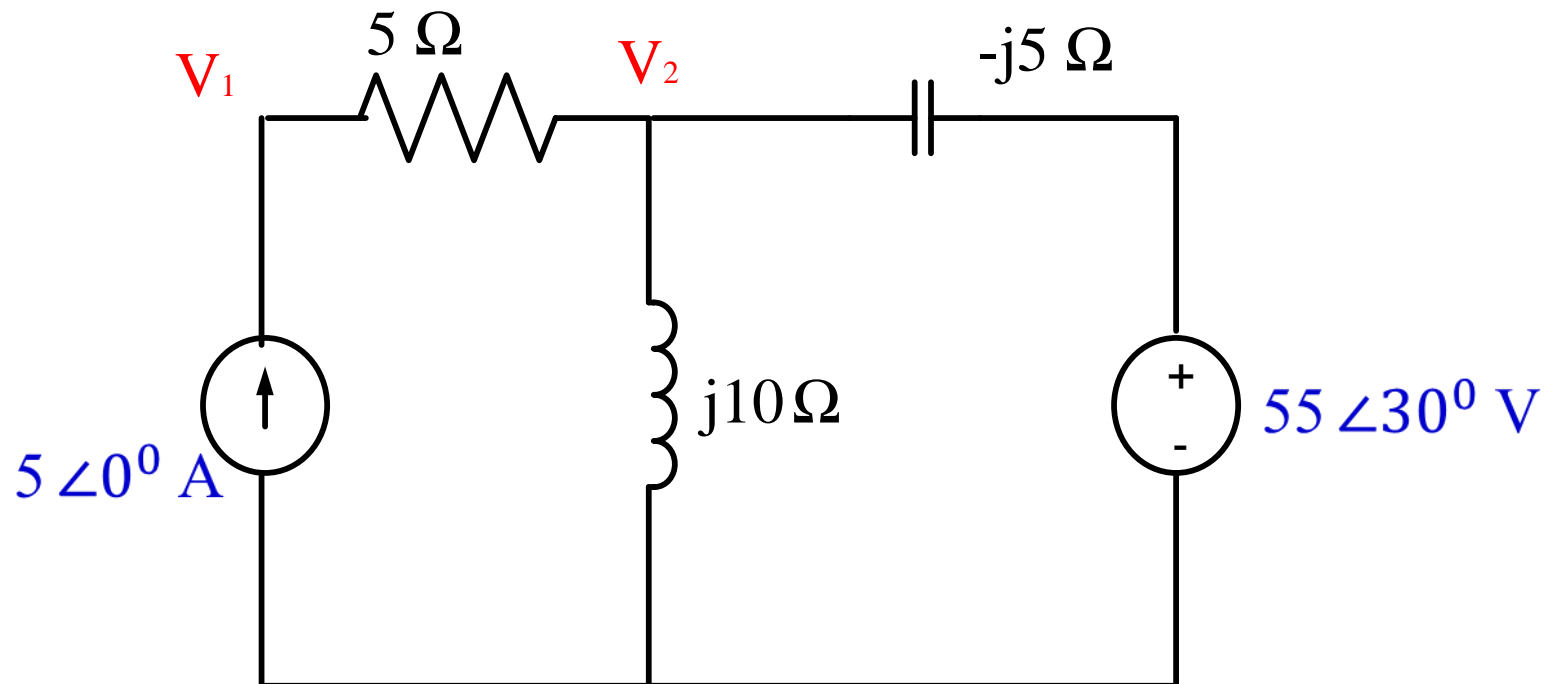

$$5\angle 0^0 + \frac{55\angle 30^0 - V_2}{-j5} = \frac{V_2}{j10}$$

$$\Rightarrow j50 - 2(55\angle 30^0 - V_2) = V_2$$

$$\Rightarrow V_2 = 95.263 + j5$$

But,

$$\begin{aligned} V_1 &= 5X5 + V_2 = 120.263 + j5 \\ &= 120.367 \angle 2.381^\circ \end{aligned}$$

Therefore, power delivered by the Current source =

$$V_1 I_s \cos(\angle V_1 - \angle I_s)$$

$$= \frac{1}{2} V_m I_m \cos(2.381^\circ - 0)$$

$$= (\frac{1}{2}) \times 120.367 \times 5 \times \cos(2.381^\circ) = 300.66 \text{ W}$$


Average or Real Power

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = VI \cos(\theta - \phi)$$


where

$$V = \frac{V_m}{\sqrt{2}}, \quad I = \frac{I_m}{\sqrt{2}}$$

Impedance and Power Triangle

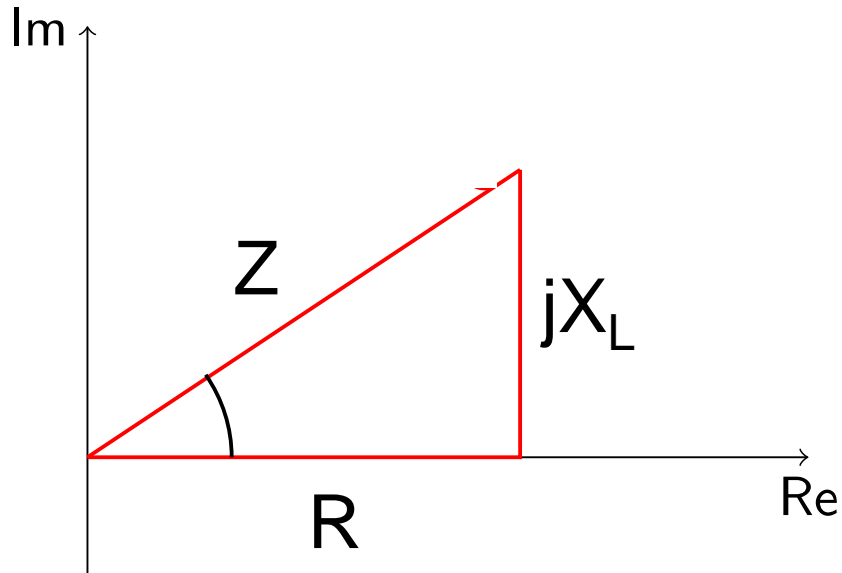


$$\text{Impedance } Z = R + j X_L$$

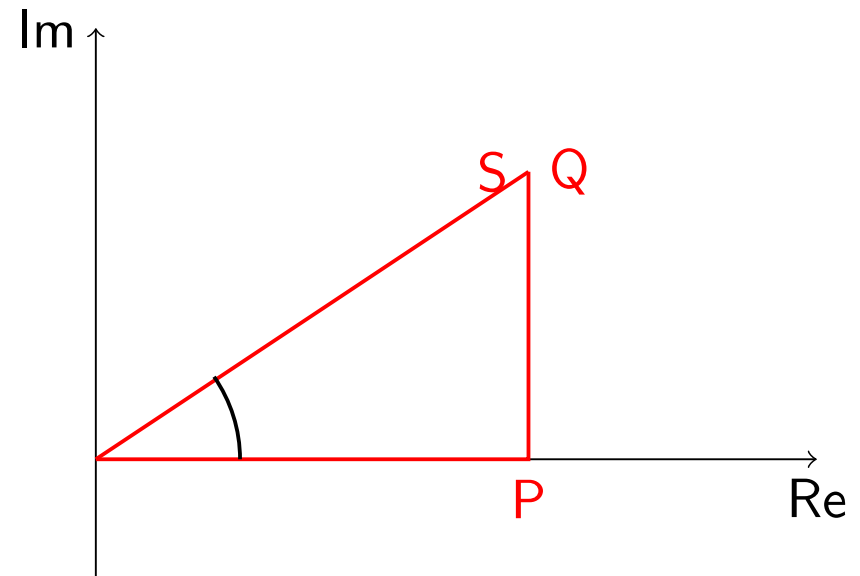

$$\begin{aligned} P &= I^2 R \text{ in W,} \\ Q &= I^2 X_L \text{ in VAR} \\ S &= VI \text{ in VA} \end{aligned}$$

Power Triangle

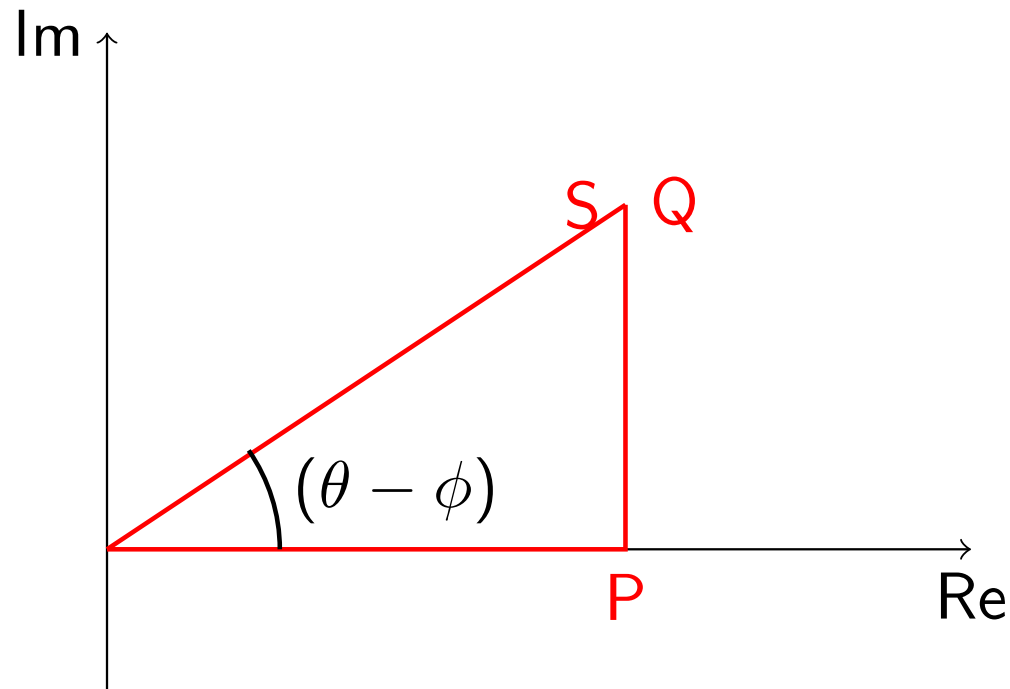

$$\mathbf{S} = VI \cos(\theta - \phi) + jVI \sin(\theta - \phi)$$

P = Real power in W, Q = Reactive power in VAR

Complex Power

$$\begin{aligned}\mathbf{S} &= VI \cos(\theta - \phi) + jVI \sin(\theta - \phi) \\ &= VI \angle(\theta - \phi) = V \angle \theta \ I \angle -\phi\end{aligned}$$

Phasor voltage and current in RMS are

$$\mathbf{V} = V \angle \theta, \quad \mathbf{I} = I \angle \phi$$

Then the complex power is

$$\mathbf{S} = \mathbf{V} \mathbf{I}^*$$


Apparent Power

Magnitude of complex power is called the apparent power

$$|S| = VI$$

Test

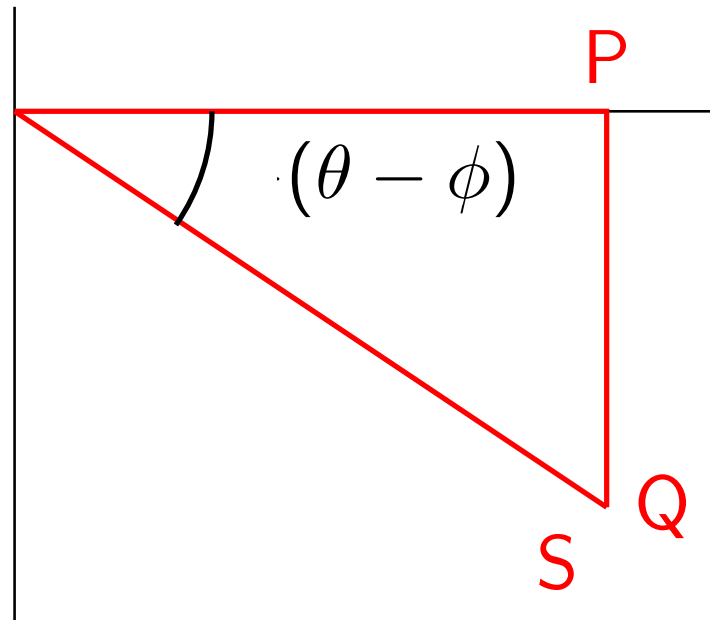- Draw the power triangle of a RC load connected to a sinusoidal source



Power factor

pf is the ratio of real power to the apparent power


$$\text{pf} = \frac{VI \cos(\theta - \phi)}{VI} = \cos(\theta - \phi)$$

Maximum value of pf is 1

$$(\theta - \phi) < 0 \quad \text{pf is leading}$$

Example 1

Estimate average, reactive powers and pf

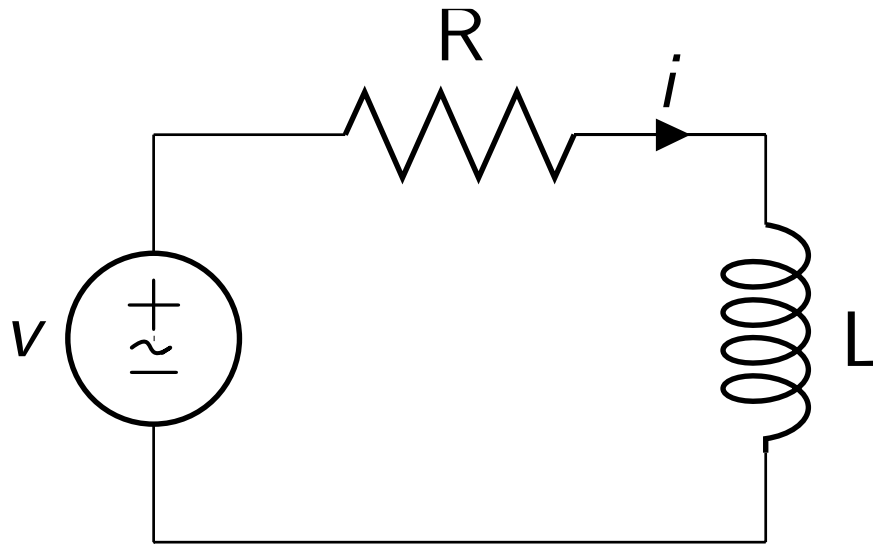

Given, $v(t) = 240\sqrt{2}\sin(1000t)$ V, $R = 4\Omega$ and $L = 3\text{mH}$

Answers:


Real/Active Power : 9216 W,

Reactive Power: 6912 VAR,

Power Factor: 0.8 (lagging)

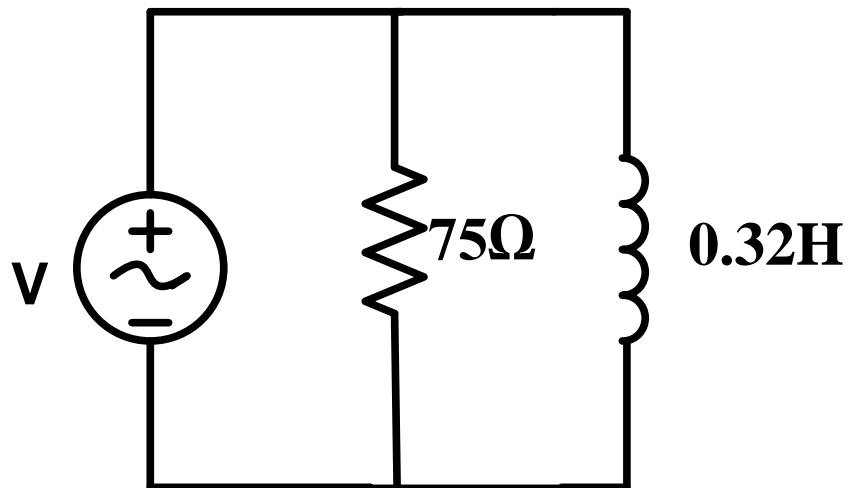Example 2:

Consider the following circuit which has a voltage source of $v = 240\sqrt{2} \cos(100\pi t)$ V.



Find its real power, reactive power and power factor.

Given, $\mathbf{V} = 240\sqrt{2} \angle 0^\circ = V_m \angle \theta$ and $\mathbf{Z} = (75 \parallel j32\pi) = 48 + j 36 = 60 \angle 36.87^\circ$ (approx.)

Then, $\mathbf{I} = \mathbf{V}/\mathbf{Z} = 4\sqrt{2} \angle -36.87^\circ = I_m \angle \phi$ and $(\theta - \phi) = 36.87^\circ$.

The power factor is $\cos(\theta - \phi) = \cos(36.87^\circ) = \mathbf{0.8 \text{ lagging}}$
(as the pf angle is +ve)

(1) Real power = $P = (1/2) V_m I_m \cos(\theta - \phi) = (1/2) 240\sqrt{2} \times 4\sqrt{2} \times \cos(36.87^\circ) = 768 \text{ W}$

Also, using RMS values of voltage and current, $P = V_{\text{rms}} \times I_{\text{rms}} \times \cos(36.87^\circ) = 240 \times 4 \times 0.8 = 768 \text{ W}$

Also, $P = V_{\text{rms}}^2 / R = 240^2 / 75 = 768 \text{ W}$

$$\begin{aligned} (2) \text{ Reactive power} &= Q \\ &= V_{\text{rms}}^2 / X_L \\ &= V_{\text{rms}} \times I_{\text{rms}} \times \sin(36.87^\circ) = 576 \text{ VAR} \end{aligned}$$


(Note: $X_L = 100 \, \Omega$)

Also, reactive power = $P \tan(\theta - \phi) = 576 \text{ VAR}$

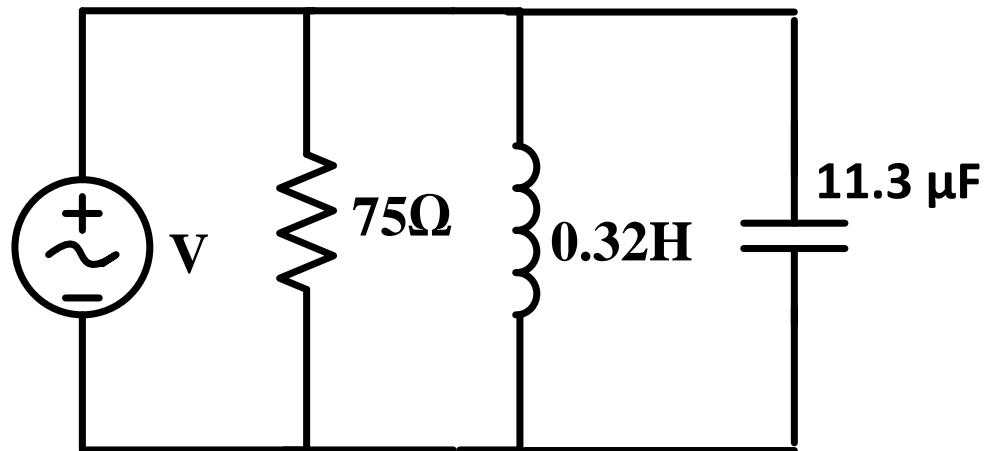Example 3:

Consider the circuit of Example 2, which has a voltage source of $240\sqrt{2} \cos(100\pi t)$ V.

Find its power factor if a capacitor of $C = 11.3 \mu\text{F}$ is connected in parallel with the voltage source.



Reactive power of the capacitor, $Q_c = - V_{\text{rms}}^2 / X_c = - 204.04 \text{ VAR}$

Net reactive power experienced by the source
 $= 576 - 204.04 = 371.96 \text{ VAR}$

Net real power experienced by the source $= 768 \text{ W}$


Using the power triangle,

$$\tan (\theta - \phi) = 371.96 / 768$$

$$\Rightarrow (\theta - \phi) = 25.842^\circ \quad (\text{pf angle is positive})$$

Therefore, power factor $= \cos(25.842^\circ) = 0.9$ lagging

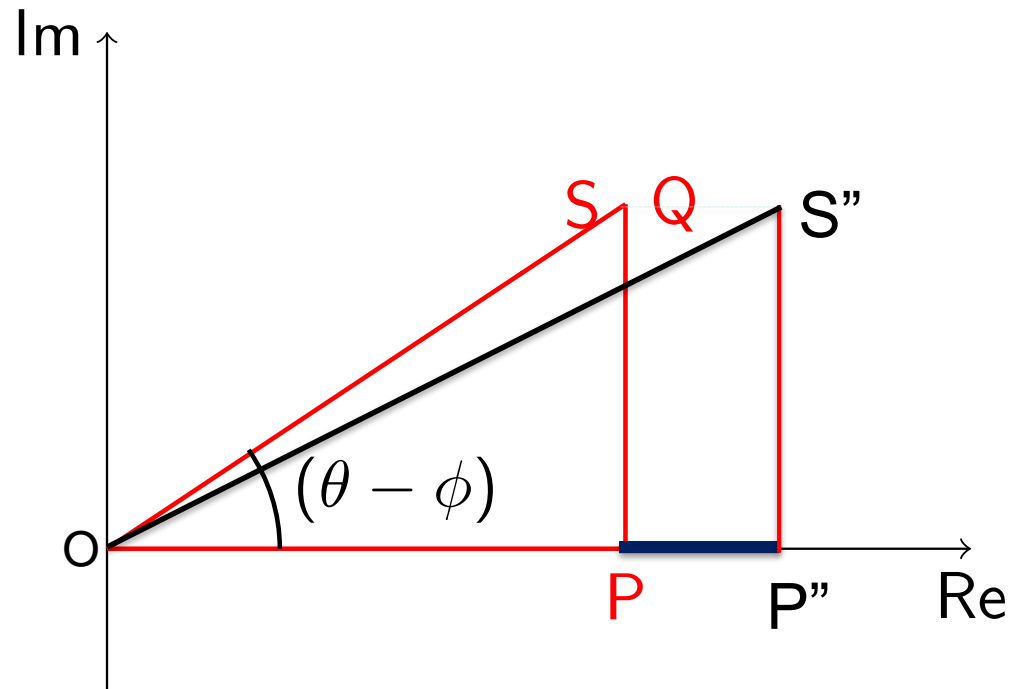Power Factor Improvement by adding Real power load (R_L)



$P + P'' =$ Real power in W, $Q =$ Reactive power in VAR

$S'' =$ Apparent power in VA

Improved Power factor

pf is the ratio of real power to the apparent power

$$= \frac{P+P''}{|S''|}$$

Previous power triangle angle is $(\theta - \phi)$.

New power triangle has angle $(\theta'' - \phi'')$ which is lesser than the previous one

=> improvement in the power factor

END