


EE 101H – Electric Circuits

Source Transformation


And

Superposition Theorem

Source Transformation

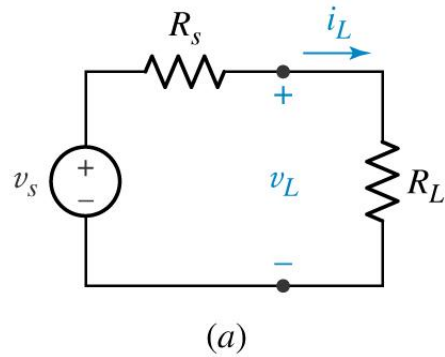


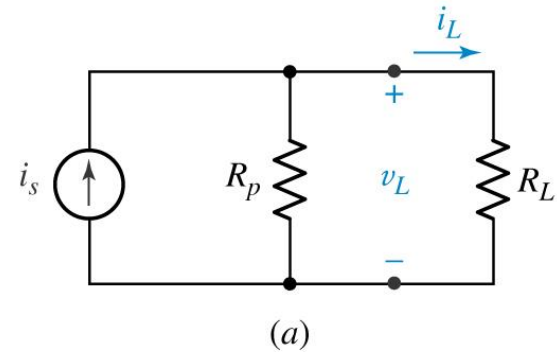(a) A general practical voltage source connected to a load resistor R_L .



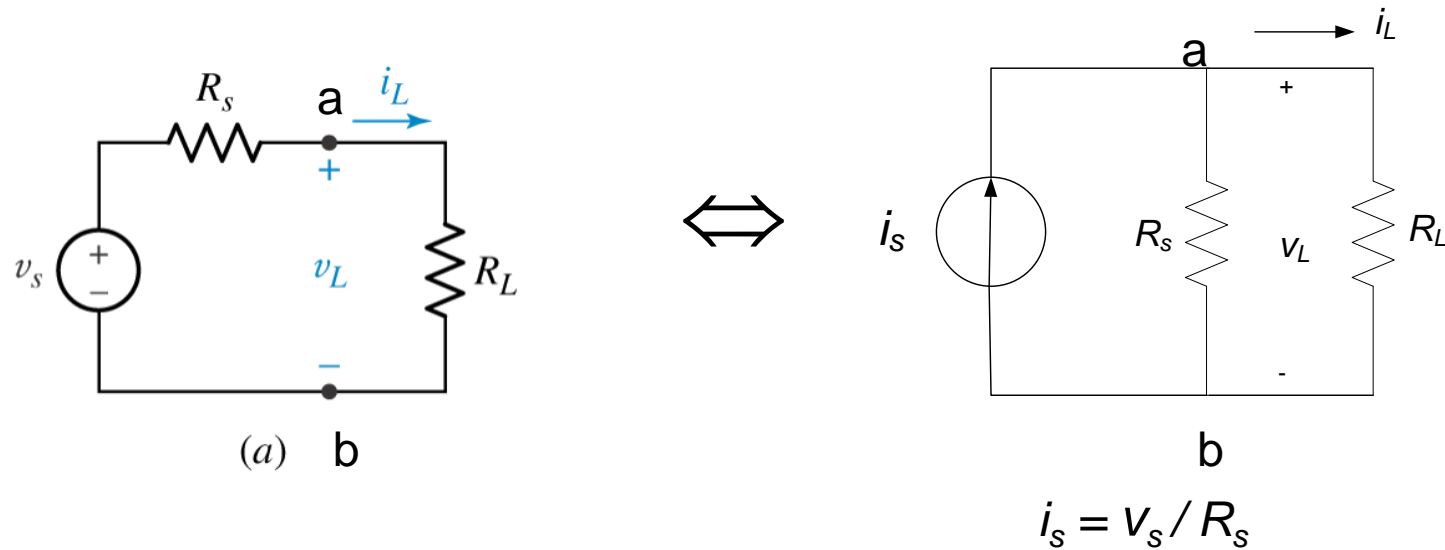(b) A general practical current source connected to a load resistor R_L .


A source transformation allows a voltage source in series with a resistor to be replaced by a current source in parallel with the same resistor or vice versa



Suppose R_L is connected between a & b
 In order the two circuits be equivalent, resistor current i_L must be same in both cases


$$\frac{v_s}{R_s + R_L} = i_s \frac{R_s}{R_s + R_L} \Rightarrow i_s = \frac{v_s}{R_s}$$

Ex

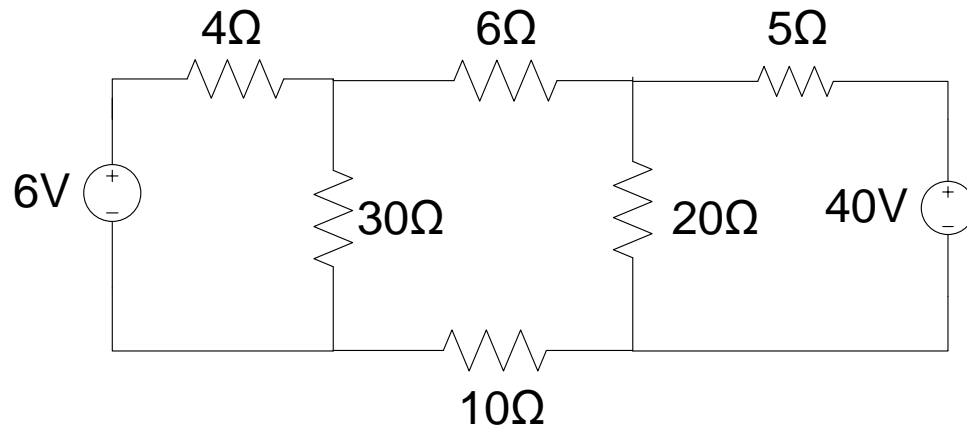


Find the power associated with the 6V source using source transformation.

Solution


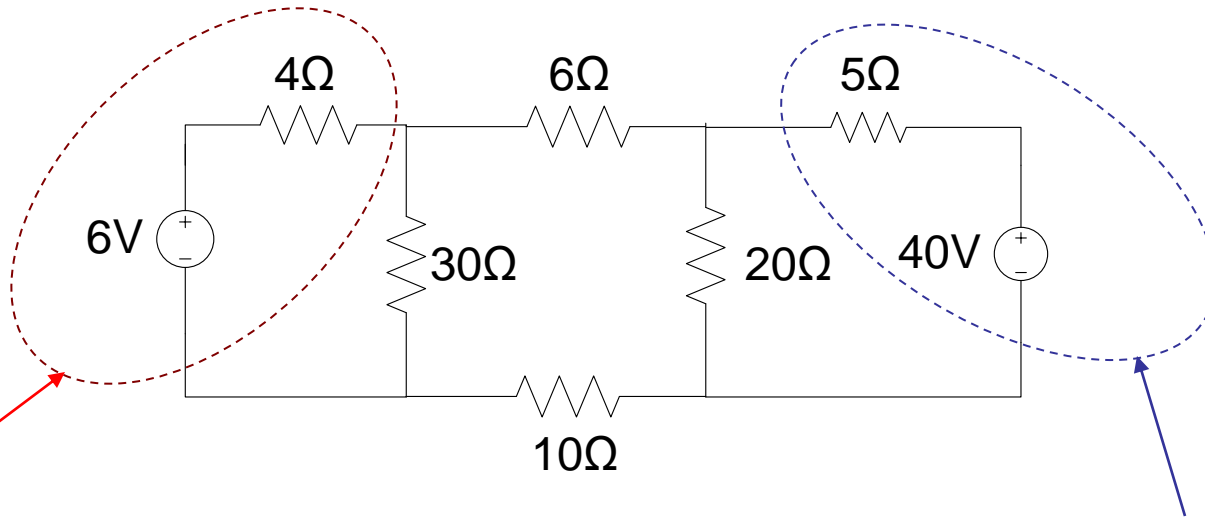



Do not disturb this part

Use source transformation

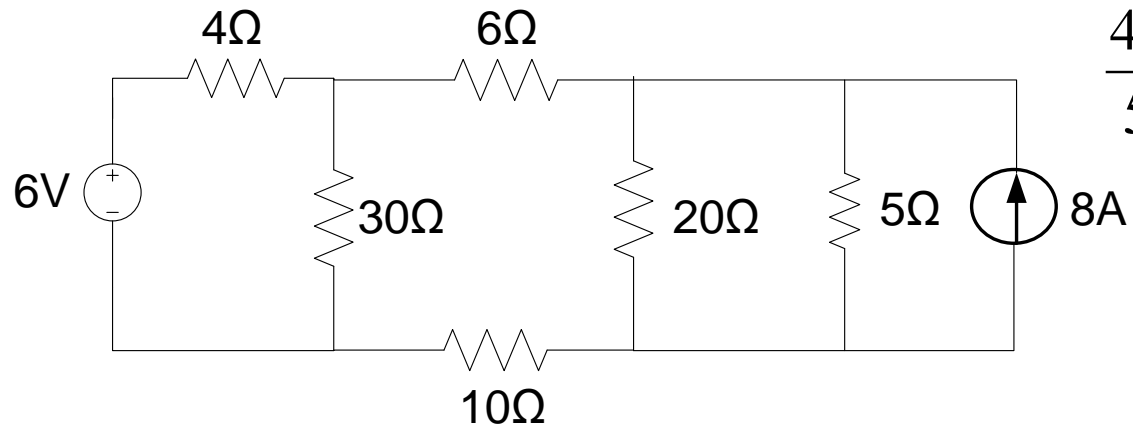




$$\frac{40V}{5\Omega} = 8A$$

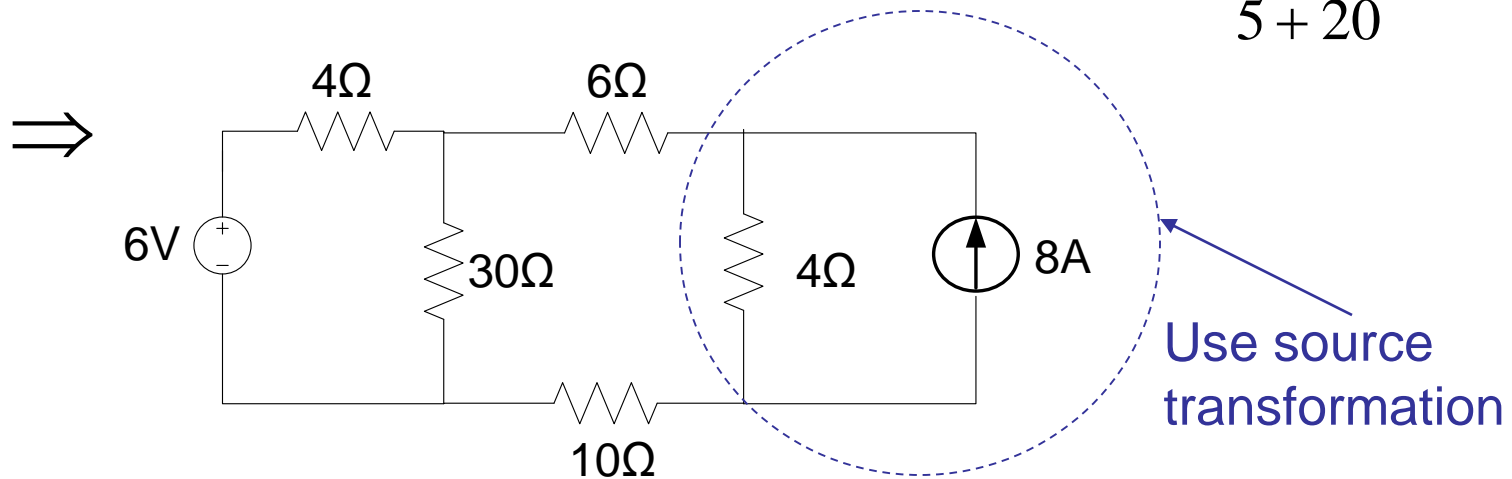
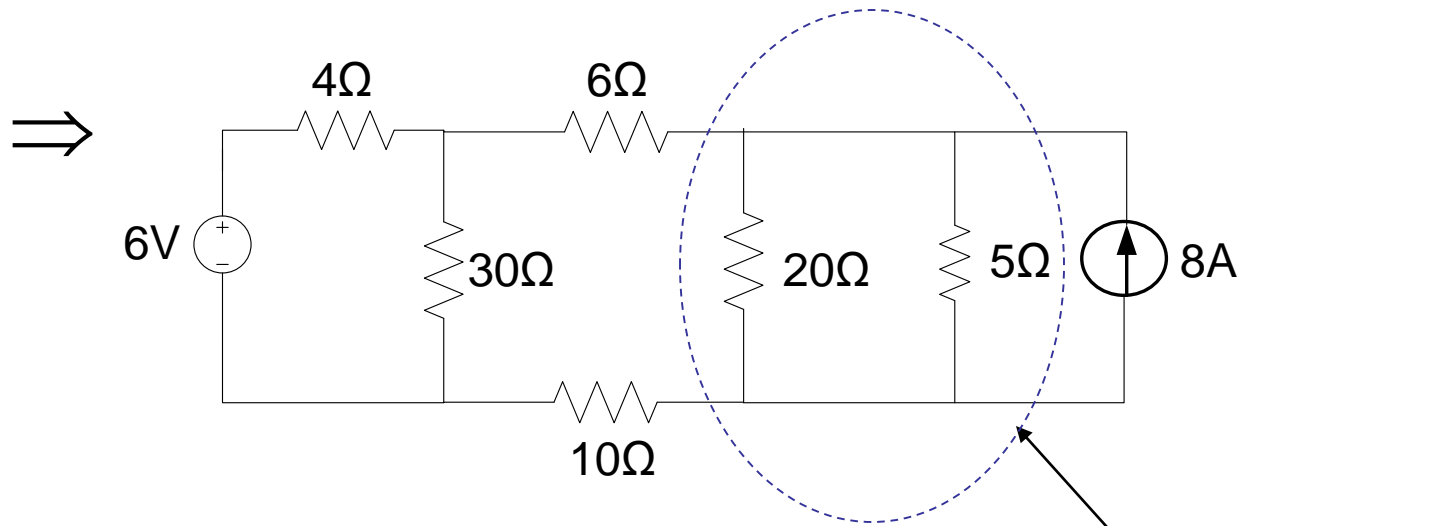



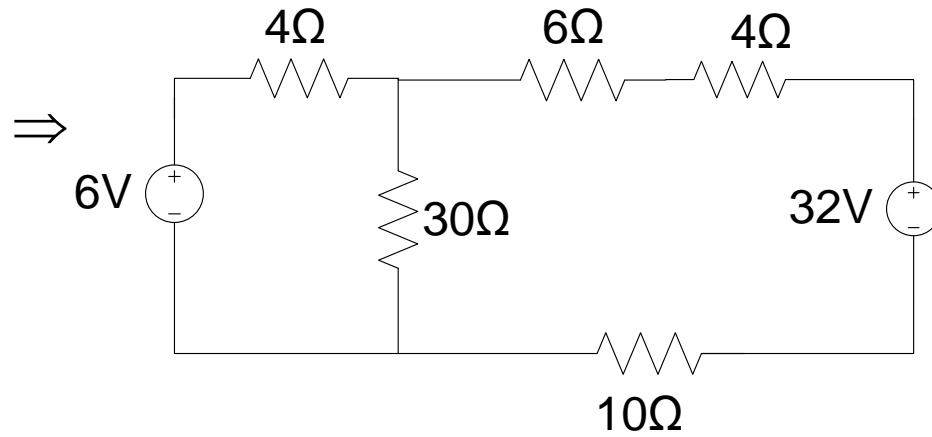

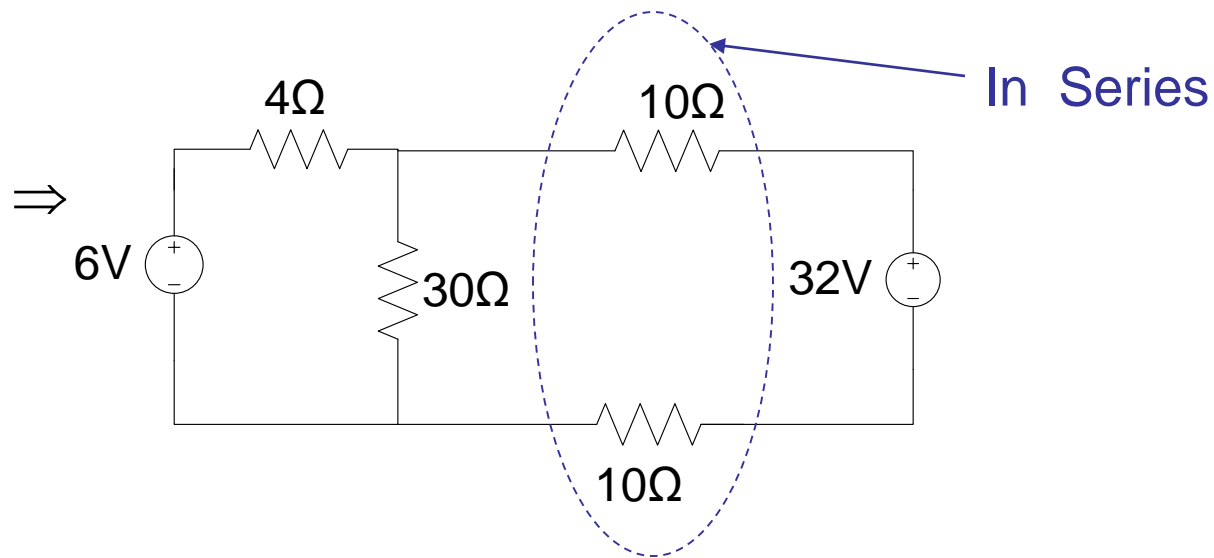
$$8\text{A} \times 4\Omega = 32\text{V}$$



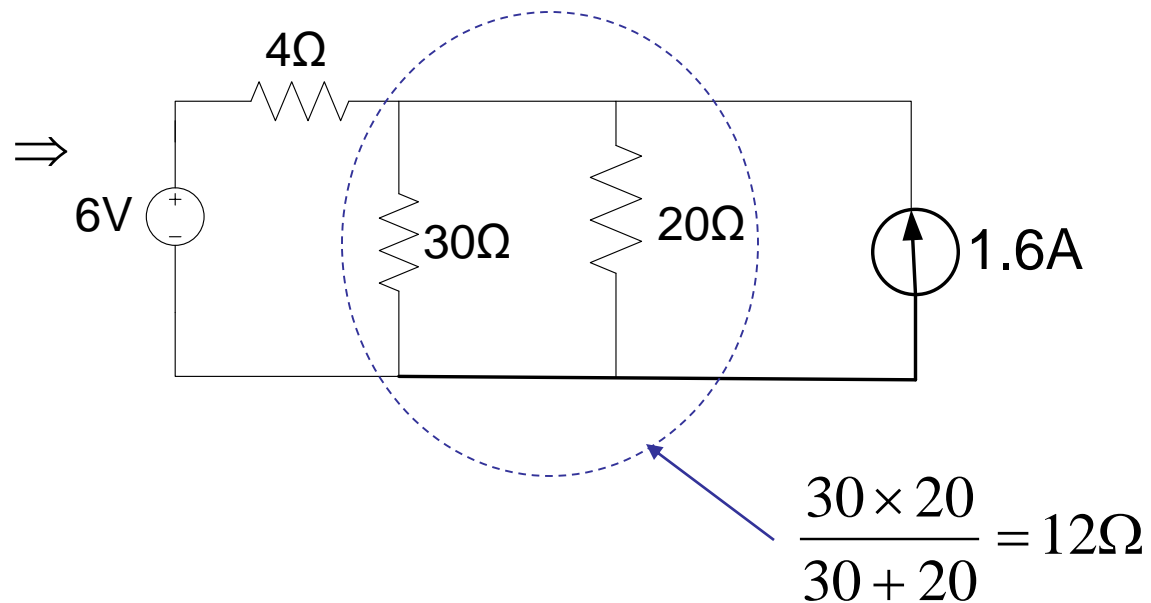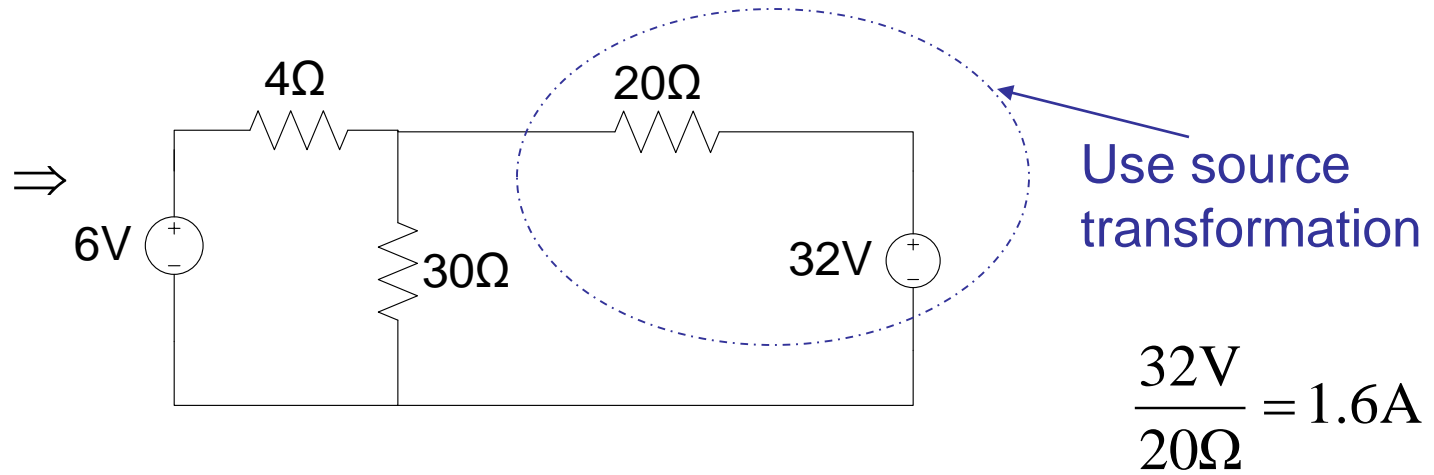

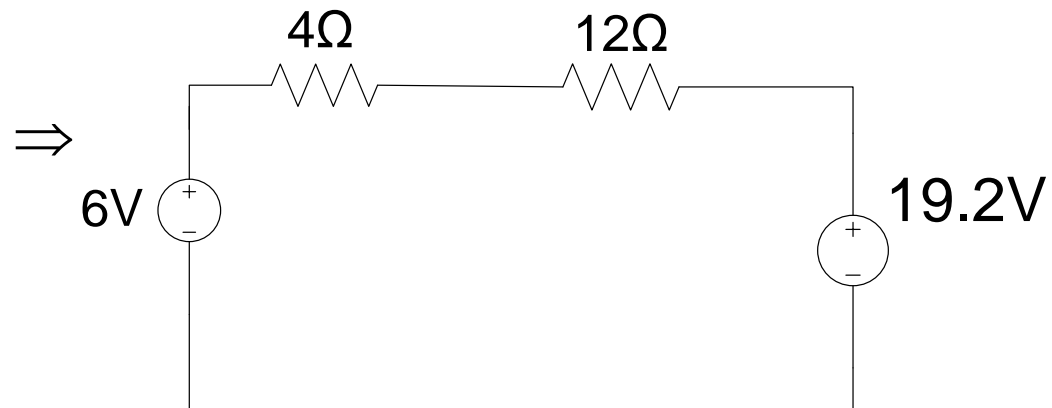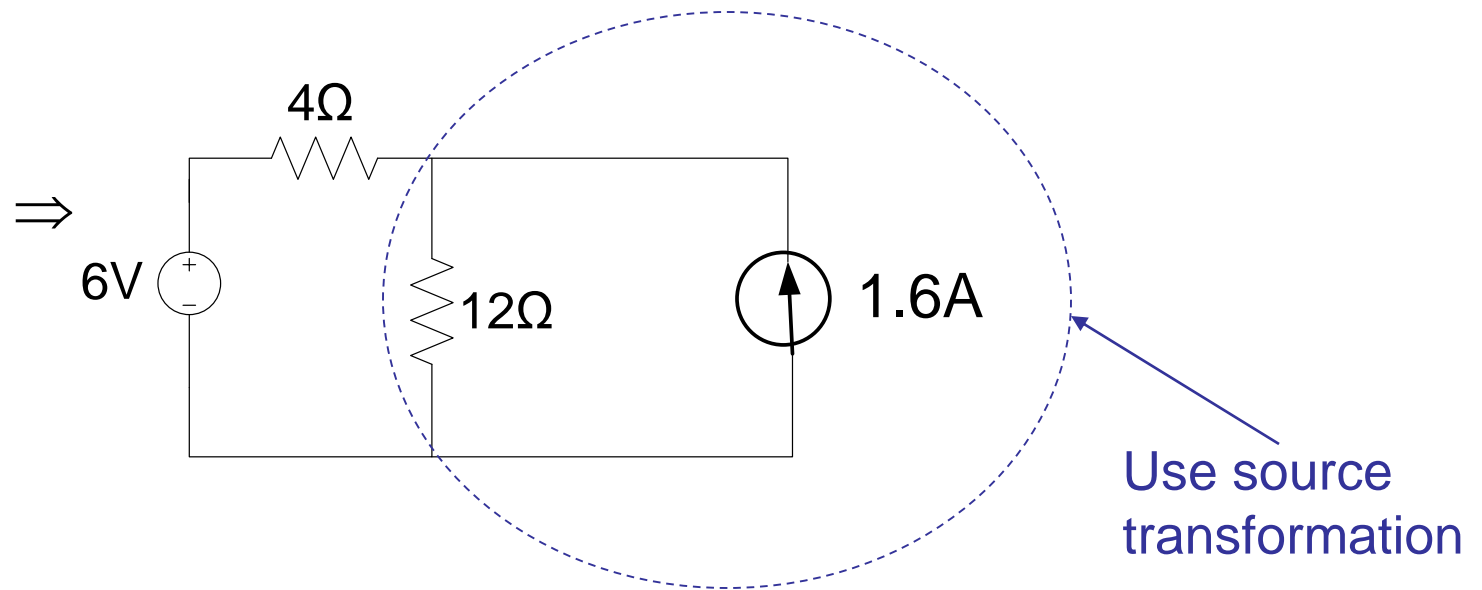

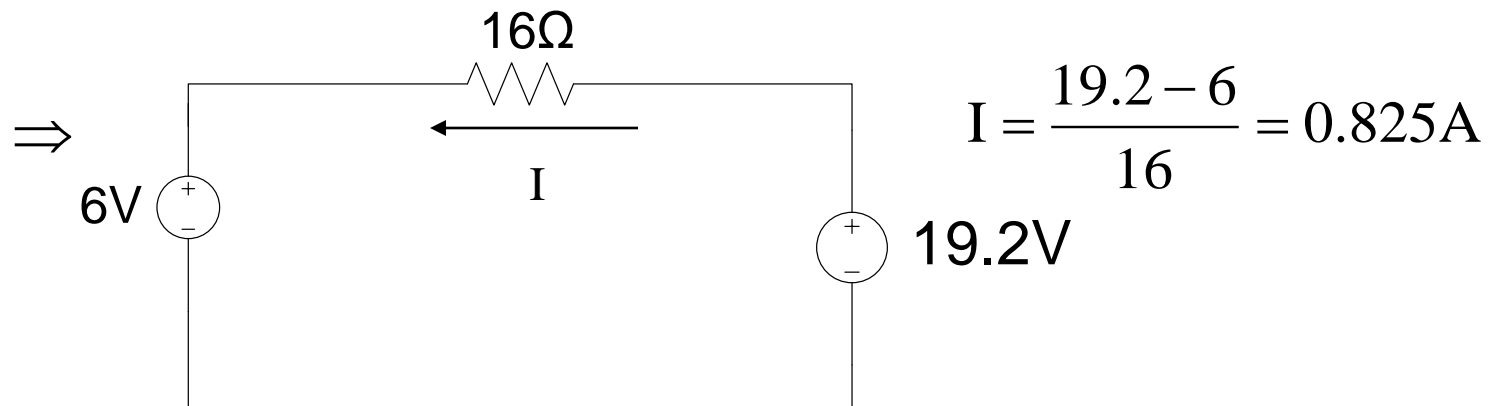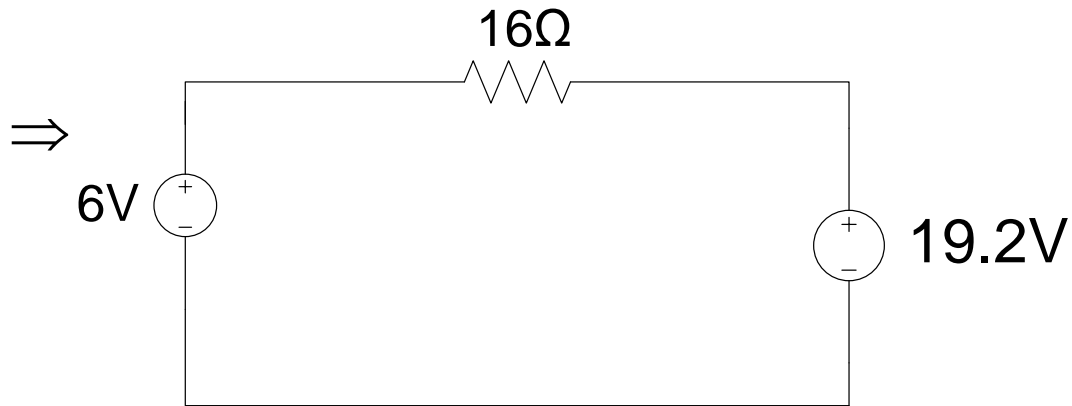


The power associated with the 6V source
 $= 6\text{V} \times 0.825\text{A} = 4.95\text{W}$
 Power is +ve, absorbed

Superposition Theorem


A linear system obeys the principle of superposition

It states that whenever a linear system is excited by more than one independent source of energy, the total response is the sum of the individual responses

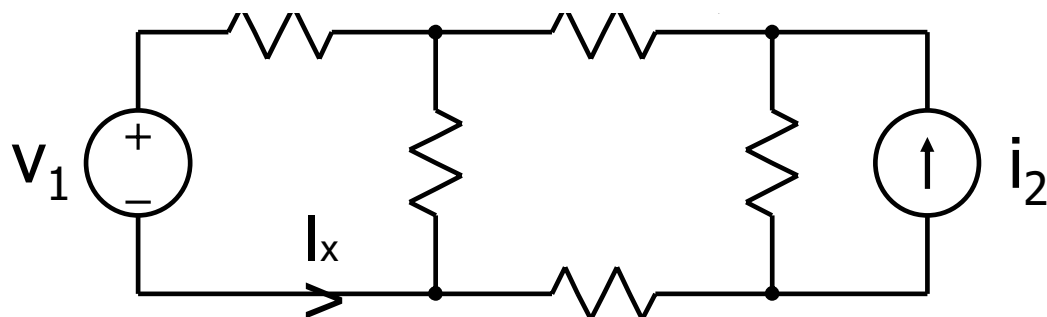with all other **independent sources made zero.**




Setting $i_2 = 0$

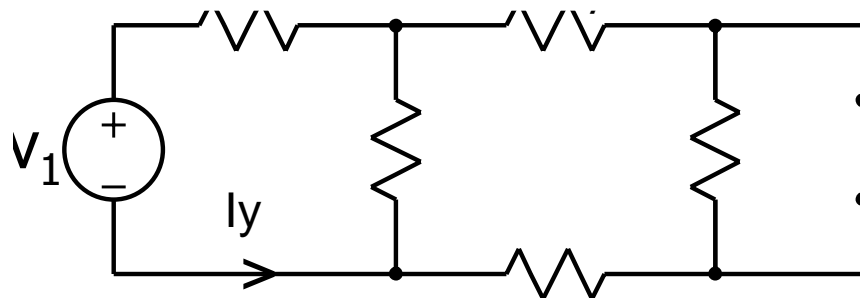


$$I_x = I_y + I_z$$

Setting $V_1 = 0$

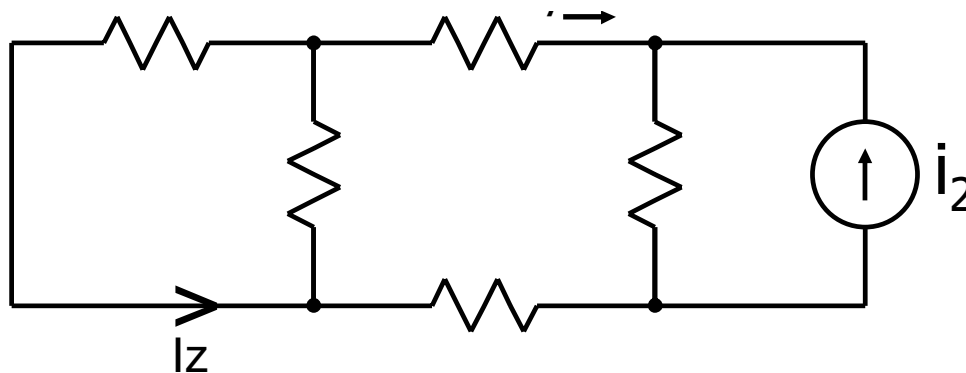


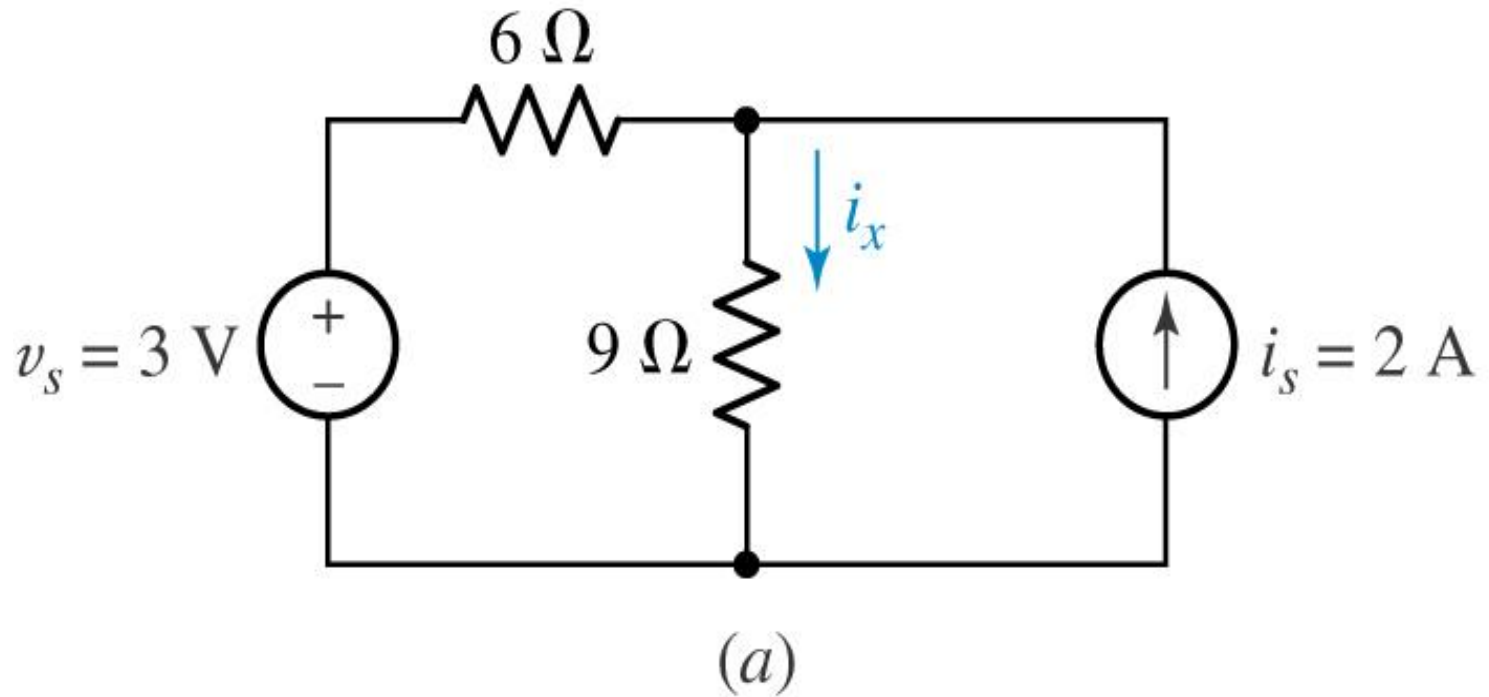Example : Use superposition to find the current i_x



Solution

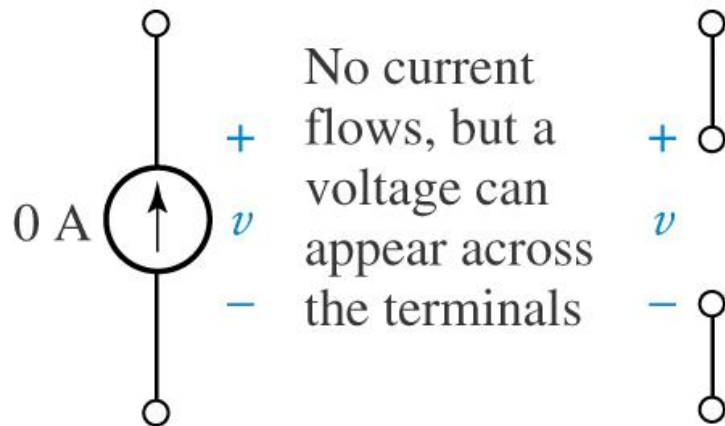1. Find branch currents due to voltage source alone
Replace the ideal current source by an open circuit




No current flows, but a voltage can appear across the terminals

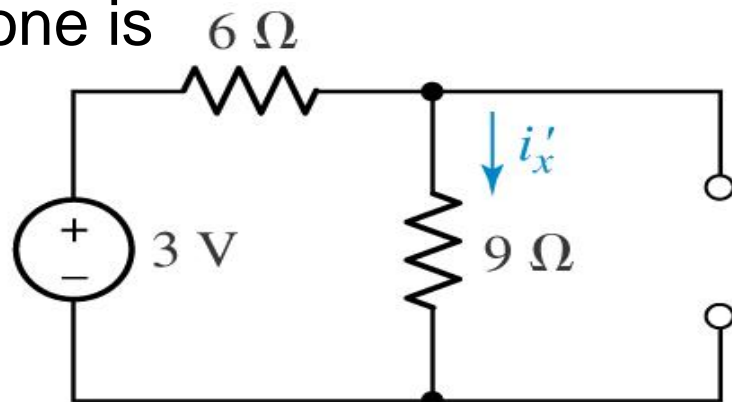(a) A current source set to zero acts like an open circuit.

Current due to 3V source alone is
Denoted by i'_x


$$i'_x = 3\text{V} / (6+9)\Omega = 0.2\text{A}$$




(b)

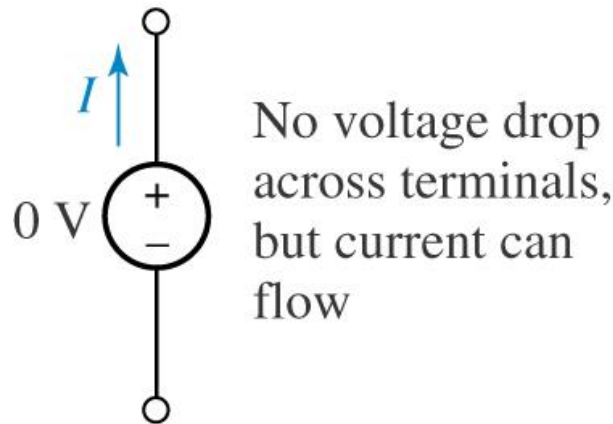2. Branch currents due to current source alone

Replace the ideal voltage source by a short circuit



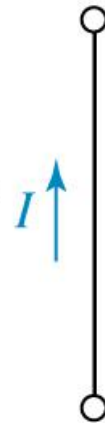
No voltage drop across terminals, but current can flow




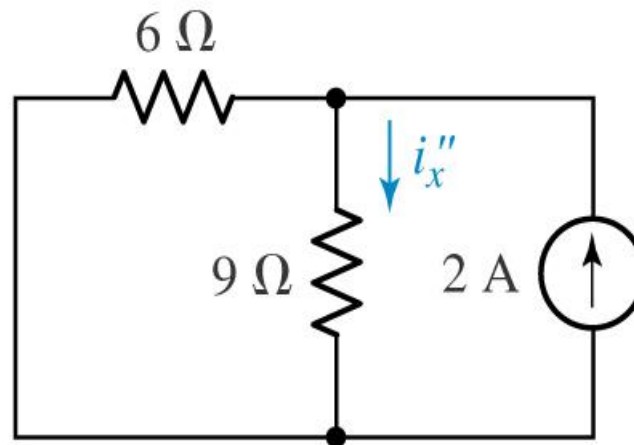(b) A voltage source set to zero acts like a short circuit.


Current due to 2A current source alone is
Denoted by i_x''

$$i_x'' = 2 \times \frac{6}{6+9} = 0.8\text{ A}$$




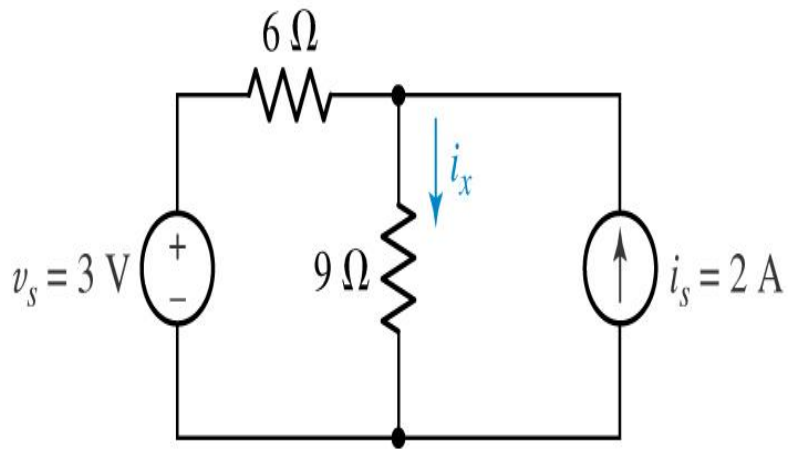

(a)

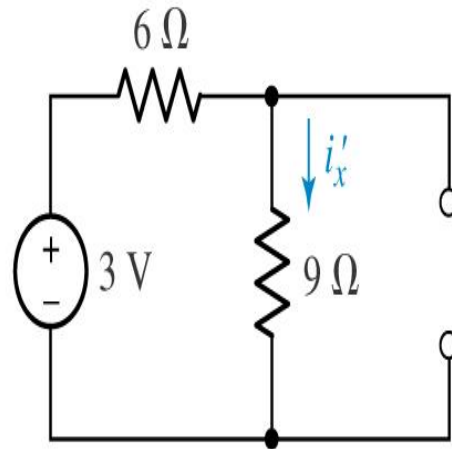

(b)

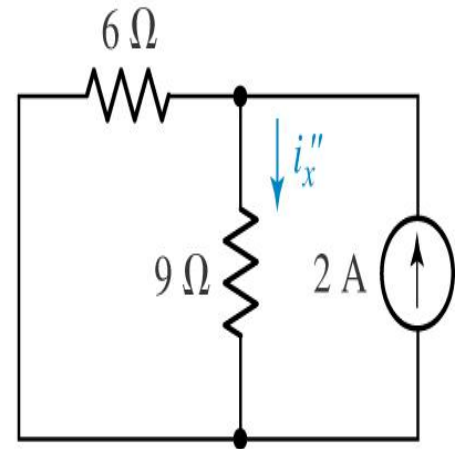




(c)

$$\begin{aligned}
 i_x &= i'_x + i''_x \\
 &= 0.2 + 0.8 \\
 &= 1\text{ A}
 \end{aligned}$$

Use superposition to find the current i_x

While using superposition in linear circuits containing both independent and dependent sources, dependent sources are never deactivated

Example

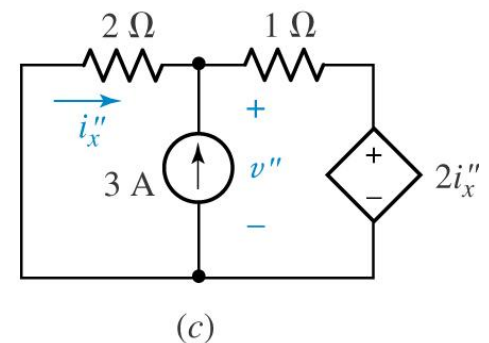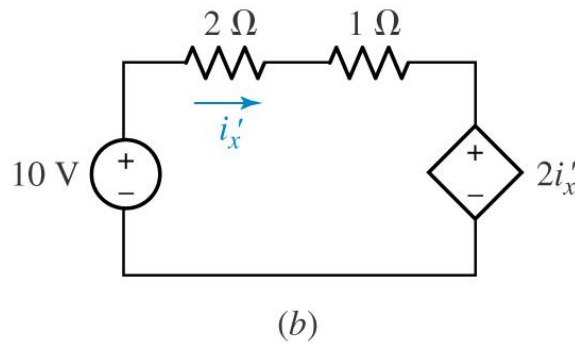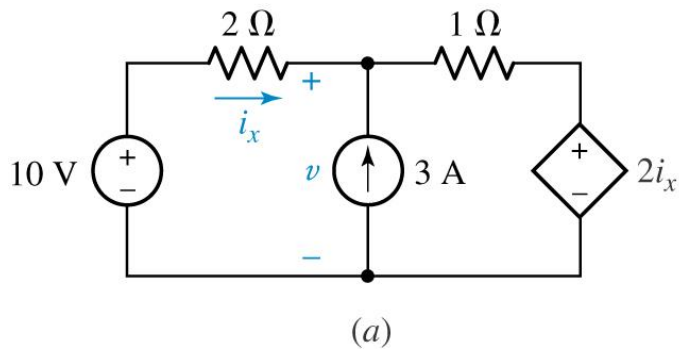

Using KVL in (b),

$$10 - (2+1) i_x' - 2 i_x' = 0$$
$$\text{Or, } 10 - 5 i_x' = 0$$
$$i_x' = 2\text{A}$$

Using KCL in (c),

$$i_x'' + 3 = (v'' - 2i_x'') / 1$$
$$\text{Or, } 3i_x'' + 3 = v''$$
$$\text{Again, } v''/2 = -i_x''$$
$$\text{So, } 3i_x'' + 3 = -2i_x''$$
$$\text{Or, } 5i_x'' = -3$$
$$\text{Or, } i_x'' = -0.6\text{A}$$

$$i_x = i_x' + i_x'' = 2 + (-0.6) = 1.4\text{A}$$

Feedback

- Go slow
- Move faster
- Any other?