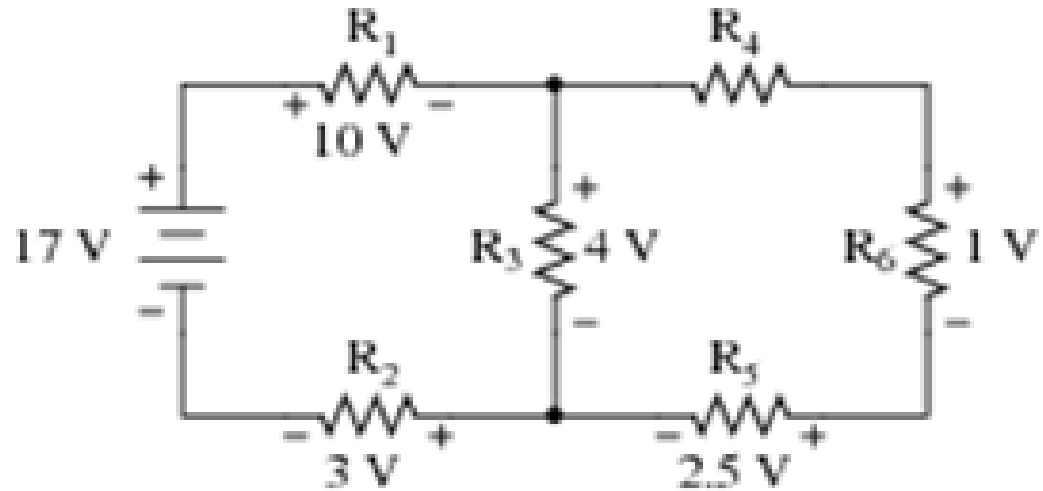



EE 101H – Electric Circuits



Practice Problems




Q1. Use Kirchhoff's Voltage Law to determine magnitude and polarity of the voltage across the resistor R_4 in this resistor network:

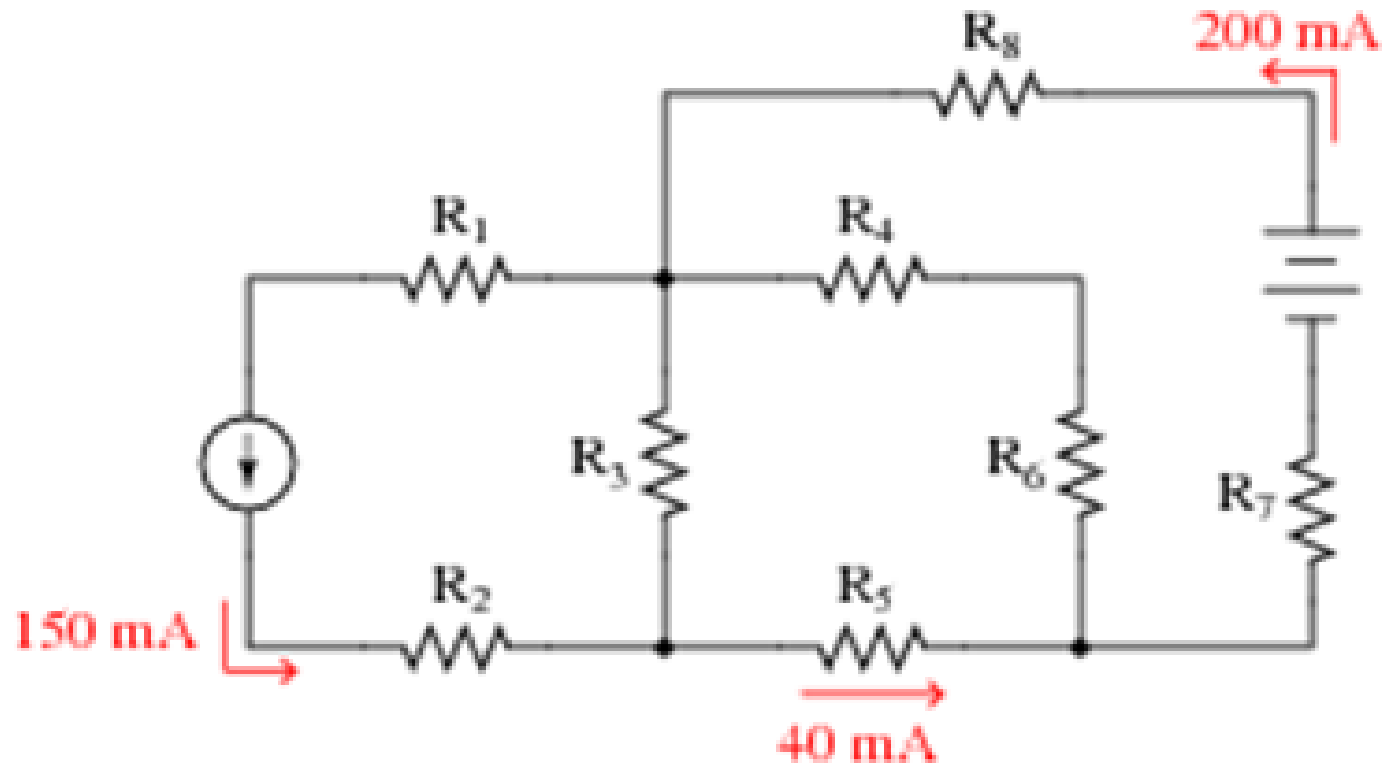
Q2. Use Kirchhoff's Current Law to find magnitudes and directions of currents through all the resistors in this circuit:



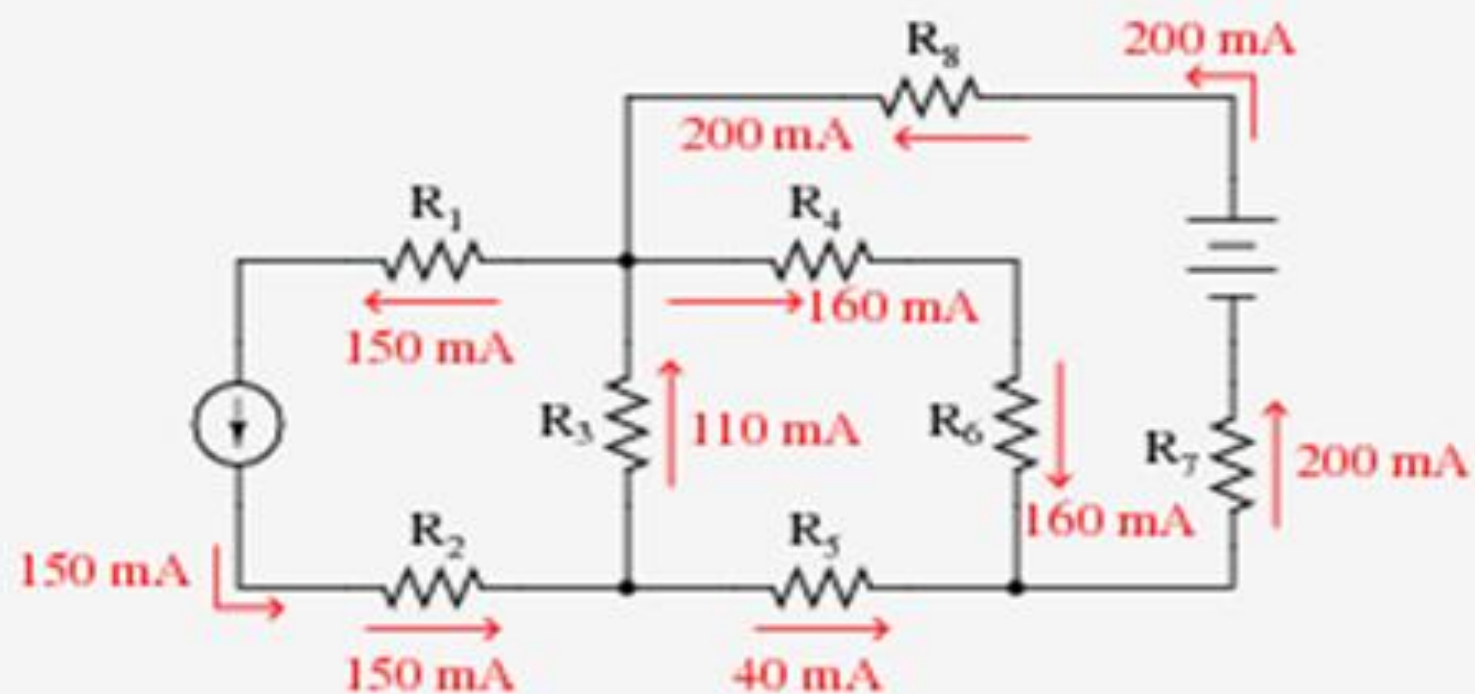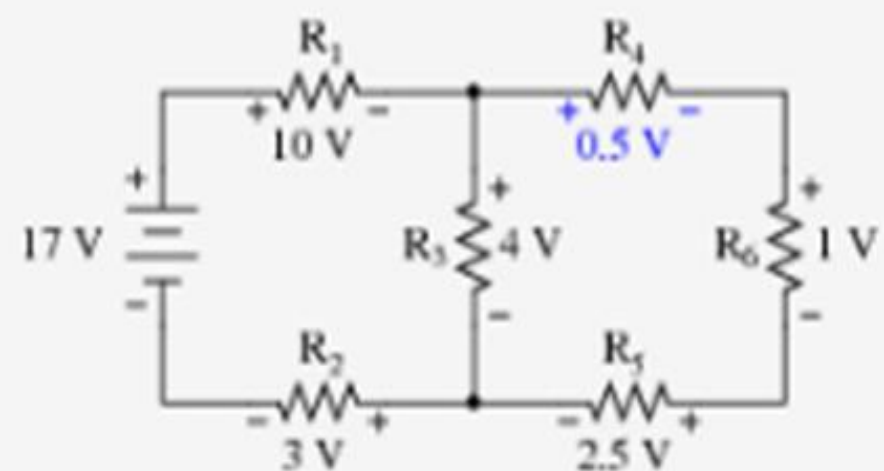

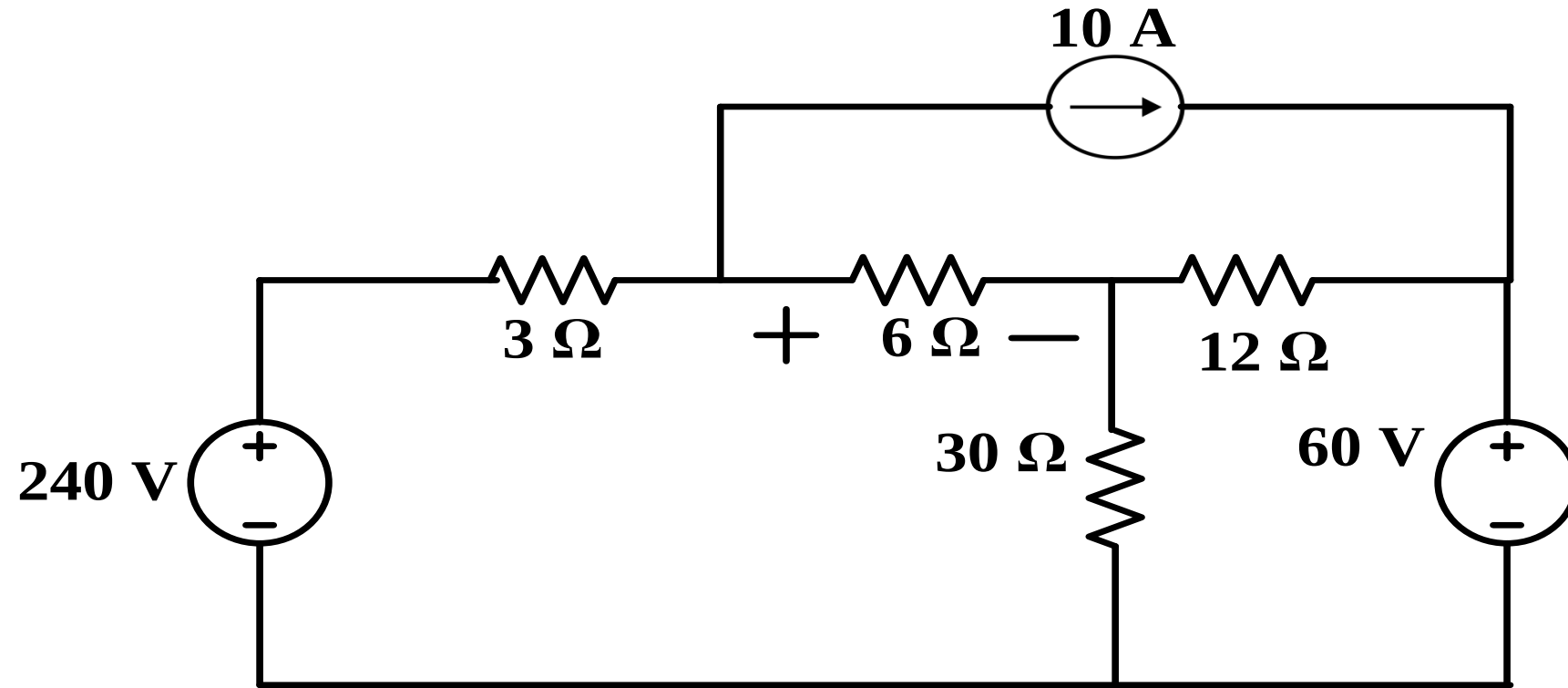

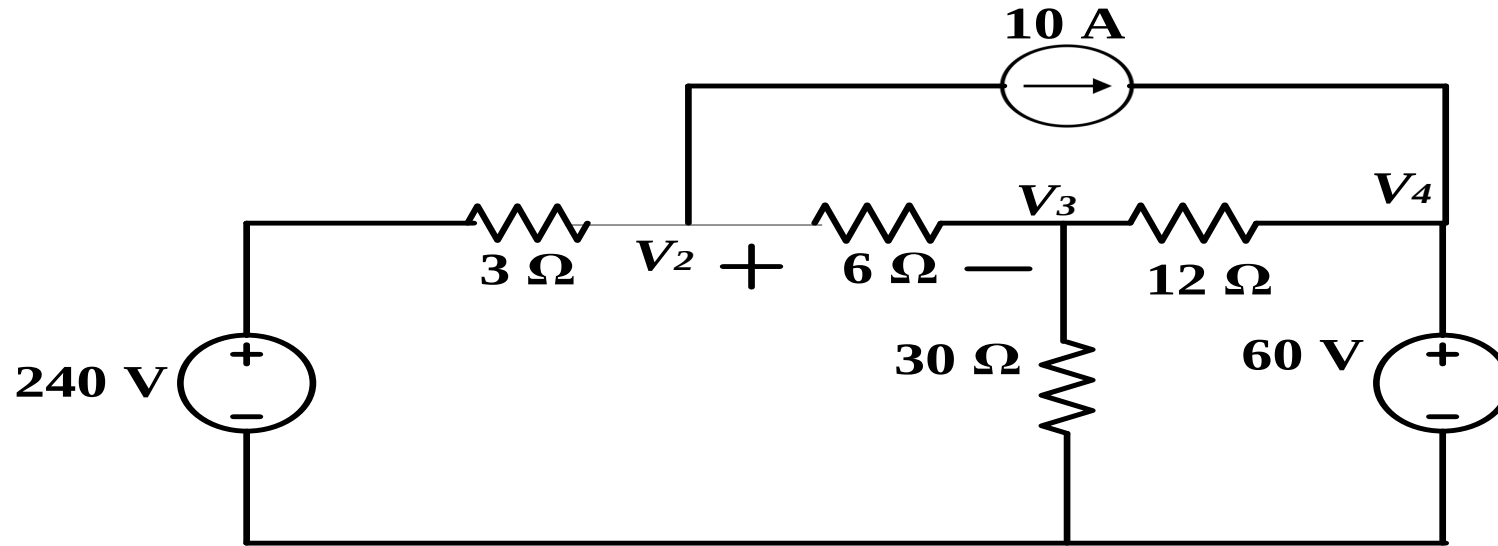Q3. Using nodal analysis, compute voltage across the 6Ω resistor.



Using Kirchoff's current law (KCL) at the node V_2 :

$$\frac{V_2 - 240}{3} + \frac{V_2 - V_3}{6} + 10 = 0 \text{ or } 2(v_2 - 240) + v_2 - v_3 + 60 = 0 \text{ giving}$$

$$3v_2 - v_3 - 420 = 0 \quad \dots\dots\dots(1)$$

Using KCL at the node V_3 :

$$\frac{V_3 - V_2}{6} + \frac{V_3}{30} + \frac{V_3 - 60}{12} = 0 \quad \text{or} \quad 10(v_3 - v_2) + 2v_3 + 5(v_3 - 60) = 0 \quad \text{giving}$$

$$17v_3 - 10v_2 - 300 = 0 \quad \dots\dots\dots(2)$$

Now, (1) x10 becomes

$$30v_2 - 10v_3 - 4200 = 0 \quad \dots\dots\dots (3)$$


and, (2) x3 gives

$$-30v_2 + 51v_3 - 900 = 0 \quad \dots\dots\dots (4)$$


$$(3)+(4) \text{ becomes } 41v_3 - 5100 = 0 \Rightarrow v_3 = 124.39 \text{ V}$$

Substitution of v_3 in (2) gives $v_2 = 181.46 \text{ V}$

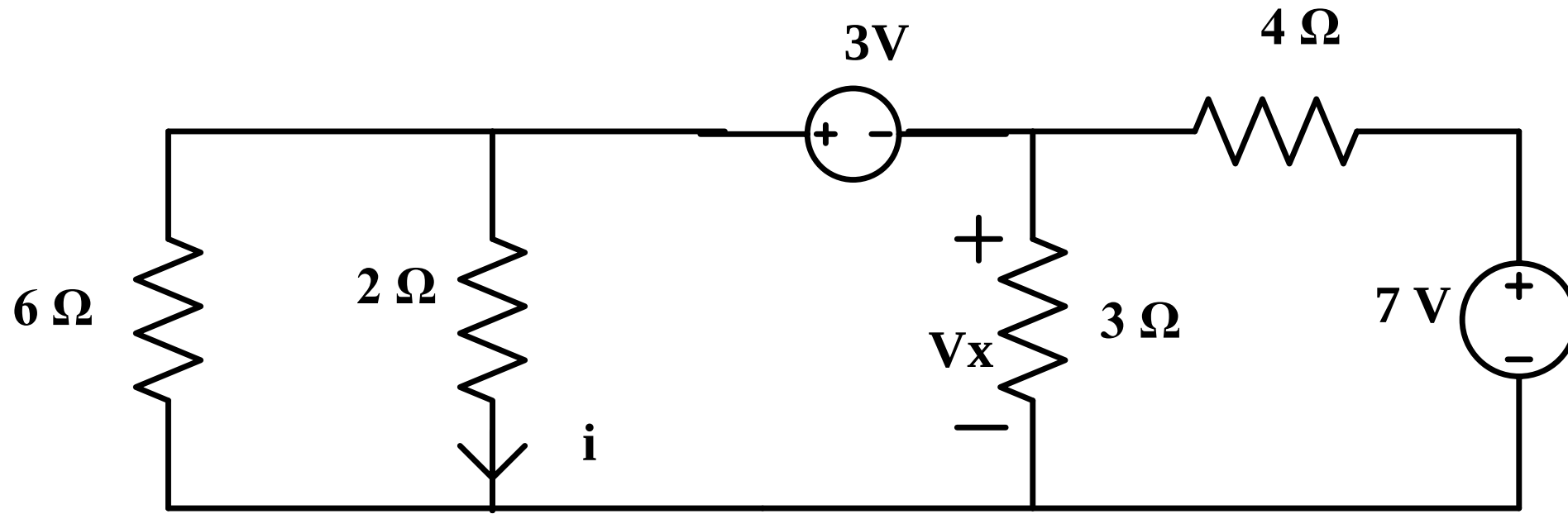Voltage across the 6Ω resistor is $v_2 - v_3 = 181.46 - 124.39 = 57.07 \text{ V}$ (Ans)



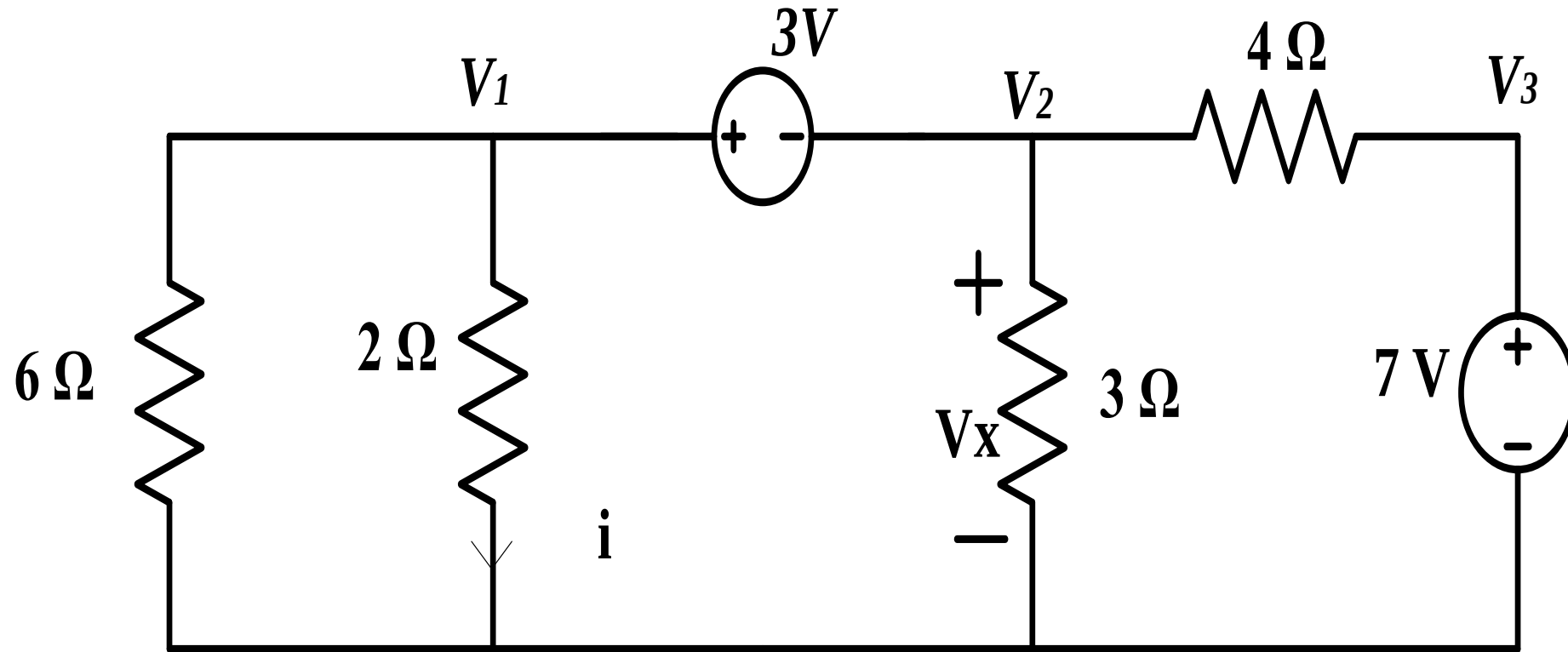Q4. Using nodal analysis and supernode, find V_x and i in the circuit



V_1 , V_2 , V_3 are the three nodes apart from the reference node. As a source is connected in between V_1 and V_2 it forms a **super node**.

Due to the super node $V_1 - V_2$: $v_1 - v_2 = 3$
.....(1)

Applying KCL at supernode overlapping V_1 and V_2 :

$$\frac{V_2 - 7}{4} + \frac{V_2}{3} + \frac{V_1}{2} + \frac{V_1}{6} = 0$$

OR

$3(v_2 - 7) + 4v_2 + 6v_1 + 2v_1 = 0$ resulting in

$$8v_1 + 7v_2 = 21 \quad \text{.....(2)}$$

Substitution of (1) in (2) gives

$$24 + 8v_2 + 7v_2 = 21$$


$$\Rightarrow v_2 = -0.2 \text{ V}$$

Now, (1) gives $v_1 = 2.8$


Therefore, $i = v_1/2 = (3 + v_2) / 2 = (3 - 0.2) / 2 = \mathbf{1.4 \text{ A}}$ (Ans)


Lastly, $\mathbf{V_x = v_2 = -0.2 \text{ V}}$ (Ans)

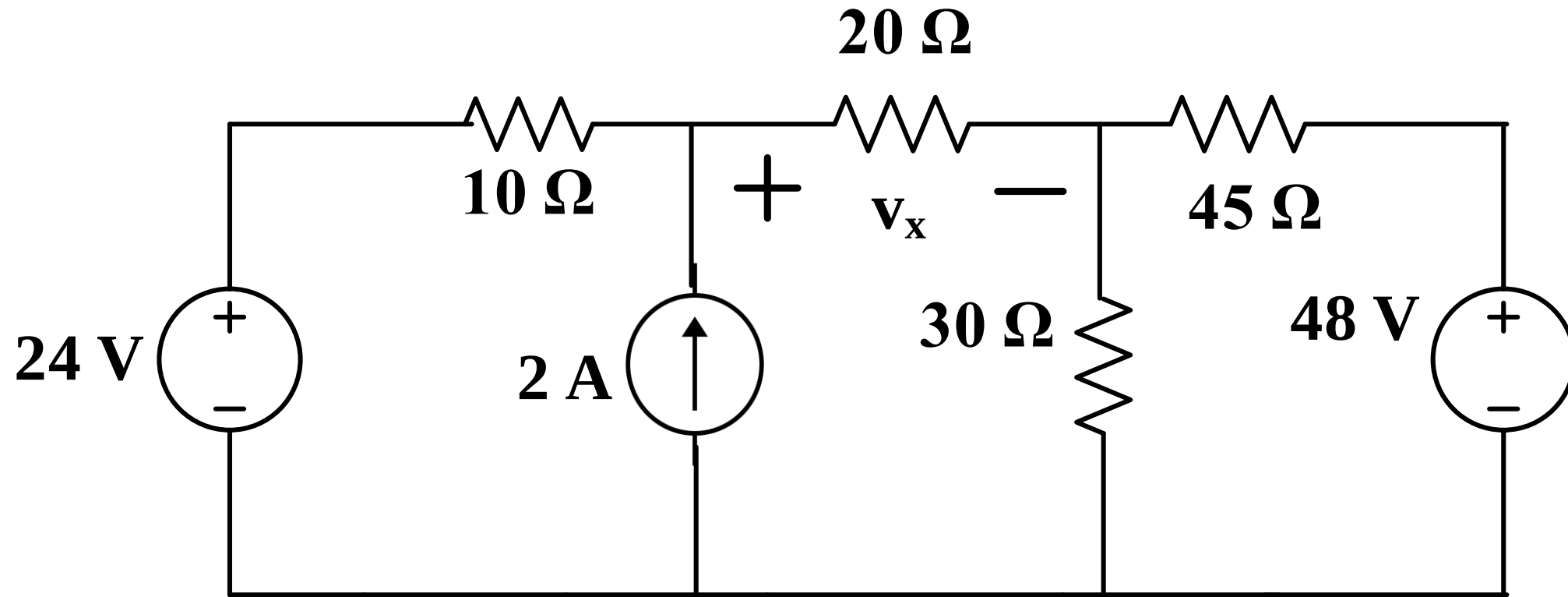Q5. Use superposition and source transformation to find the value of v_x for the circuit shown below.



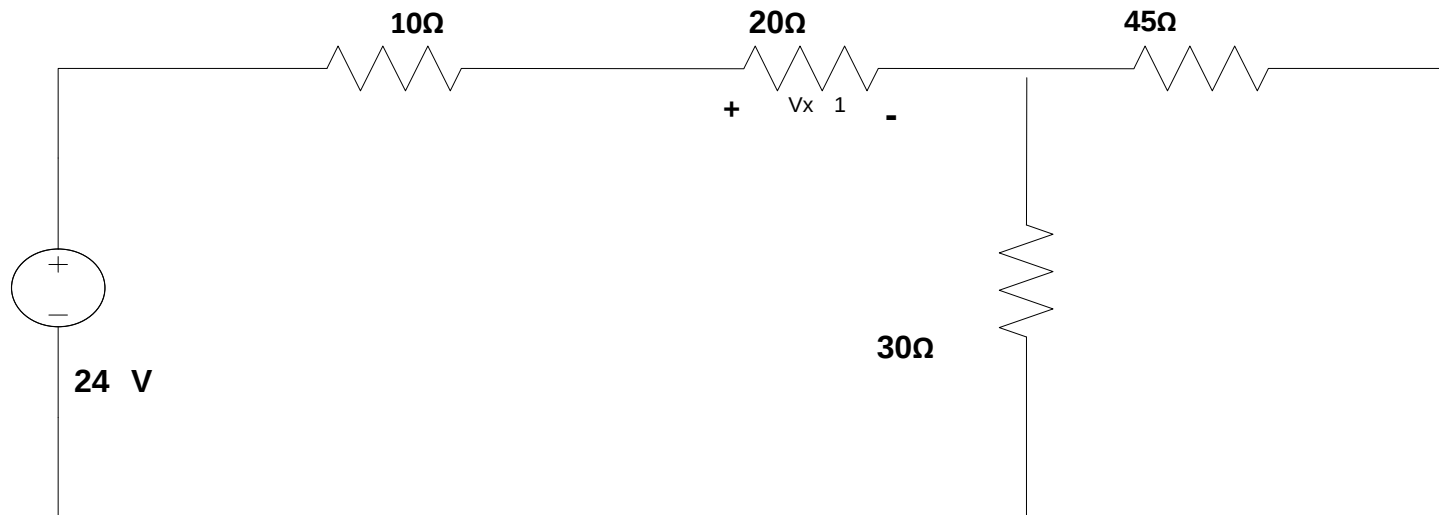Considering only 24 V source and setting 2A and 48V sources to ZERO the circuit becomes:




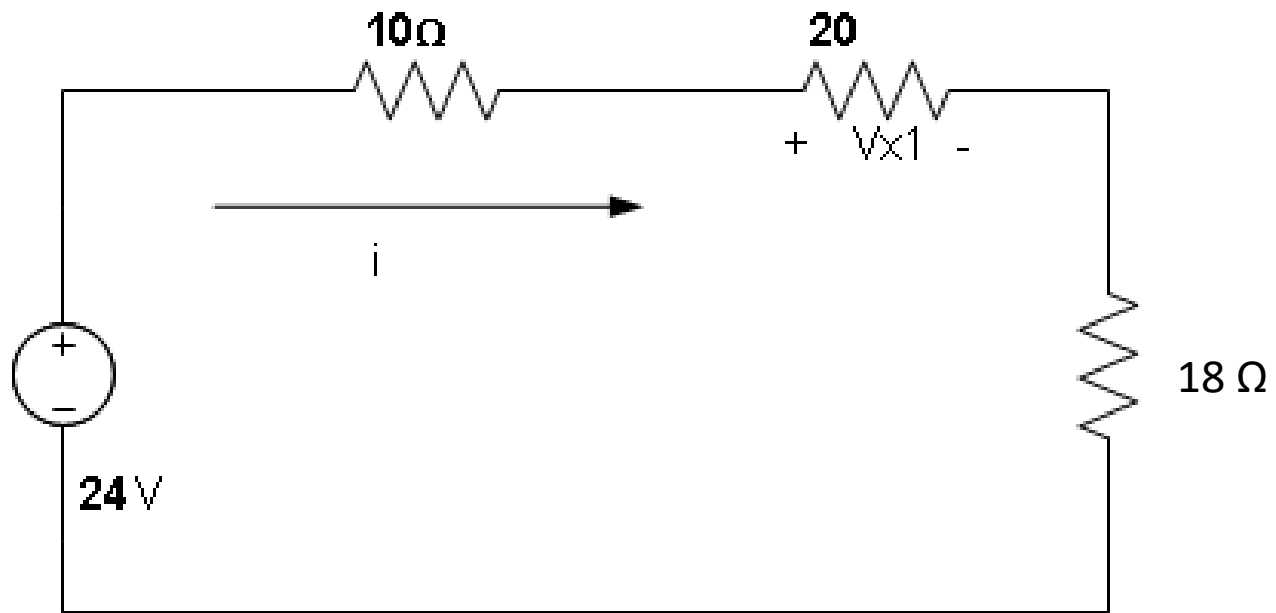

$$i = \frac{24}{10 + 20 + 18} = 0.5 \text{ A}$$

$$V_{X1} = 0.5 \times 20 = 10 \text{ V}$$

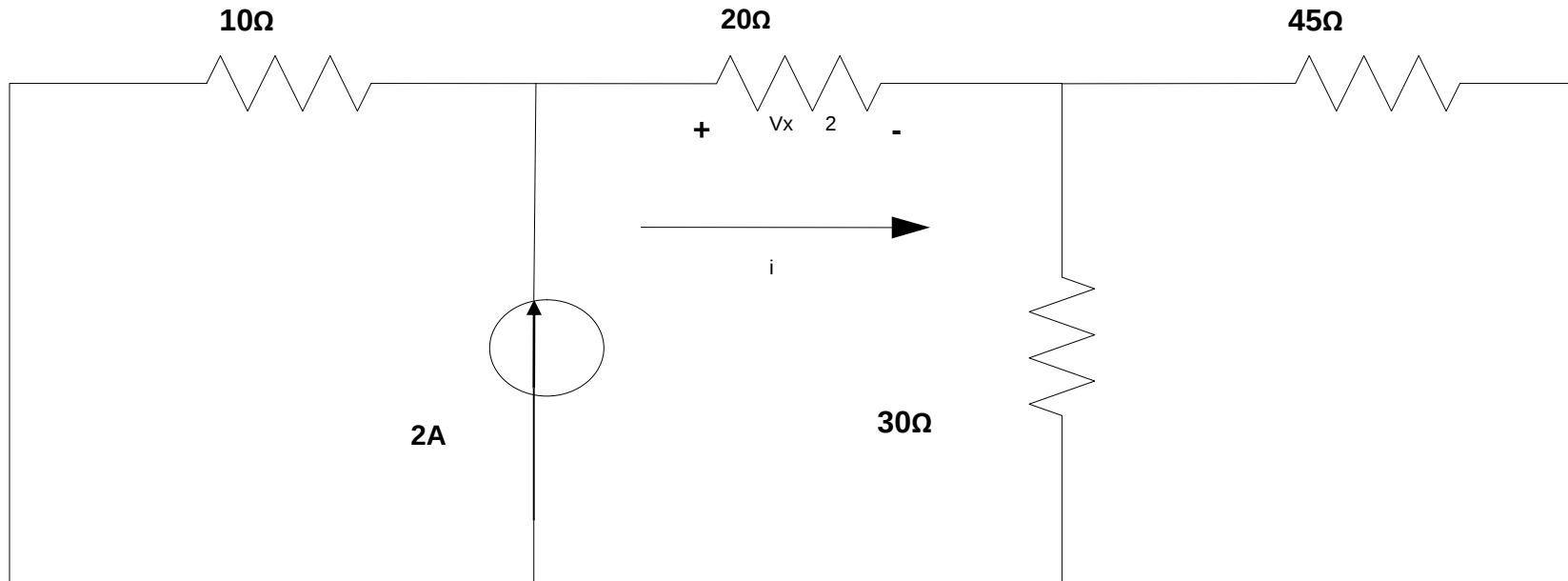
Similarly, considering only the 2 A current source, the circuit is:




Current through 20 Ω is $2 \times 10 / (10 + 20 + 18) = 0.41666 \text{ A}$


Then, $V_{x2} = i \times 20 = 0.416 \times 20 = 8.33 \text{ V}$

Considering only the 48 V source,

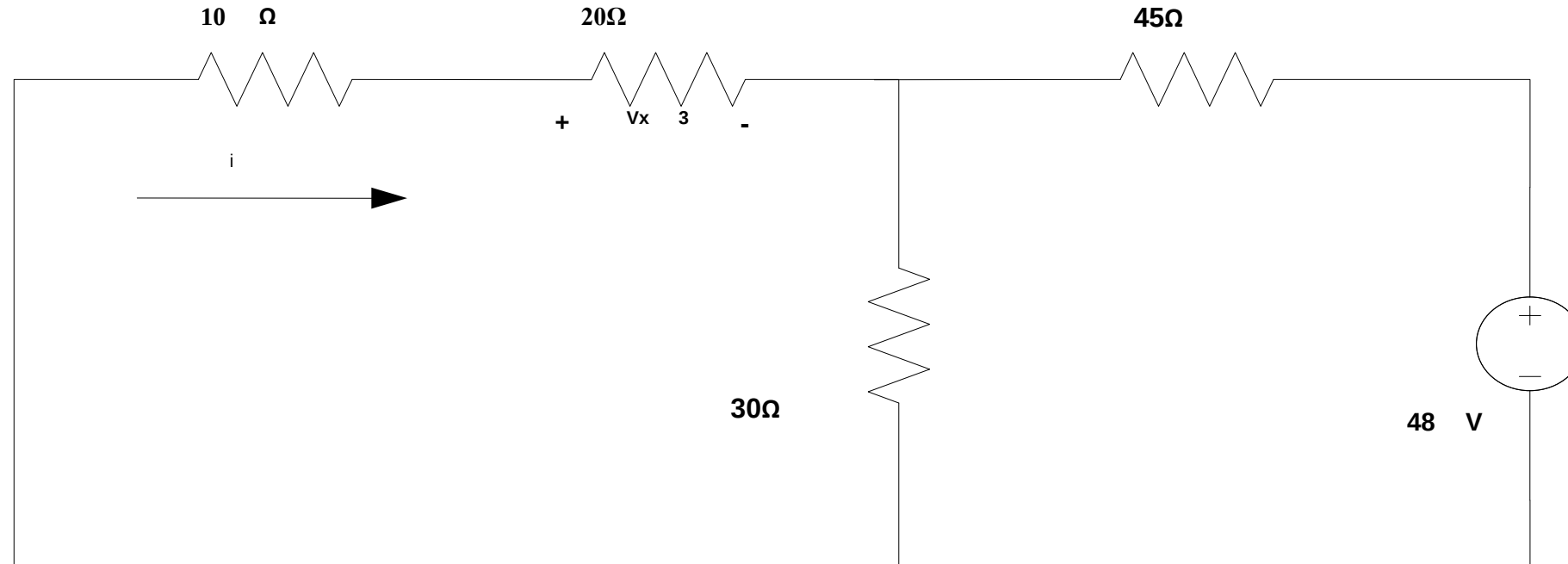

Using source transformation,

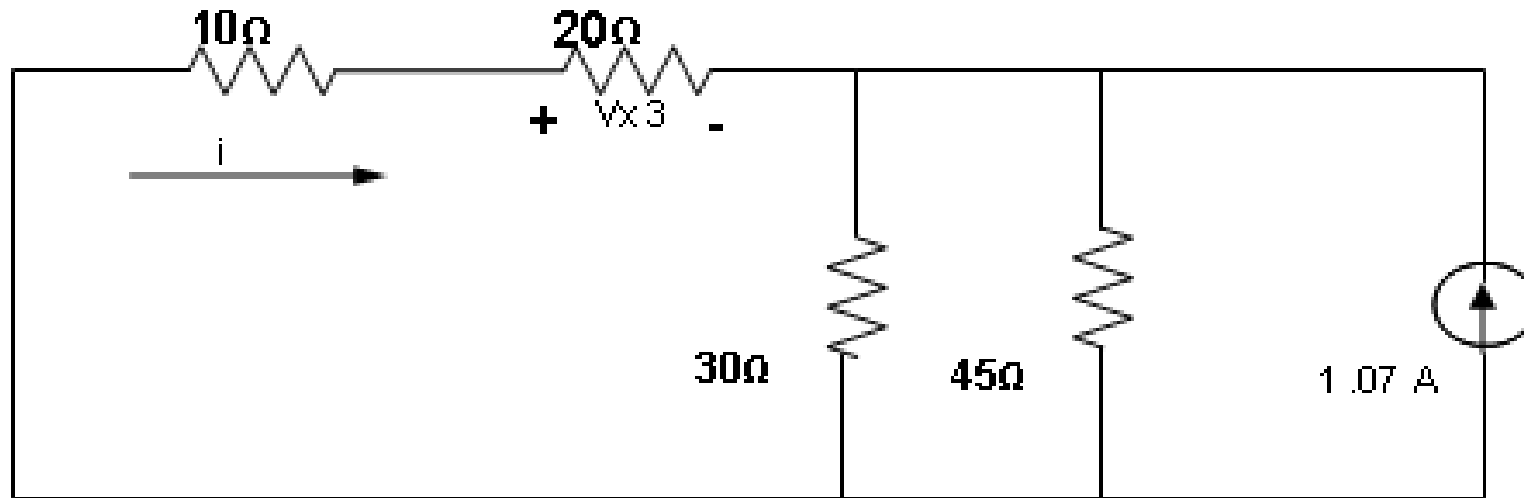

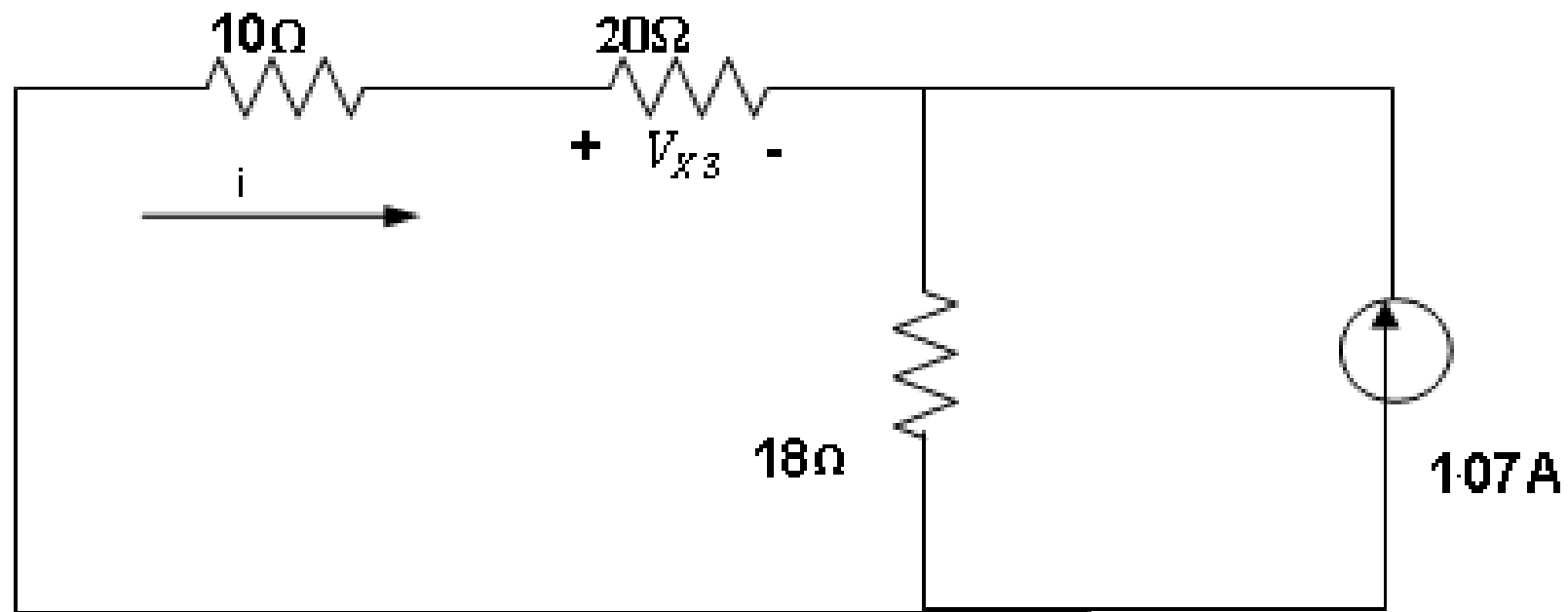

$$i = -1.07 \times \frac{18}{18 + (10 + 20)} = -0.4 \text{ A}$$


$$V_{X3} = i \times 20 = -8 \text{ V}$$

Using superposition,


$$V_x = V_{X1} + V_{X2} + V_{X3} = 10 + 8.33 - 8 = 10.33 \text{ V.}$$

ANOTHER METHOD

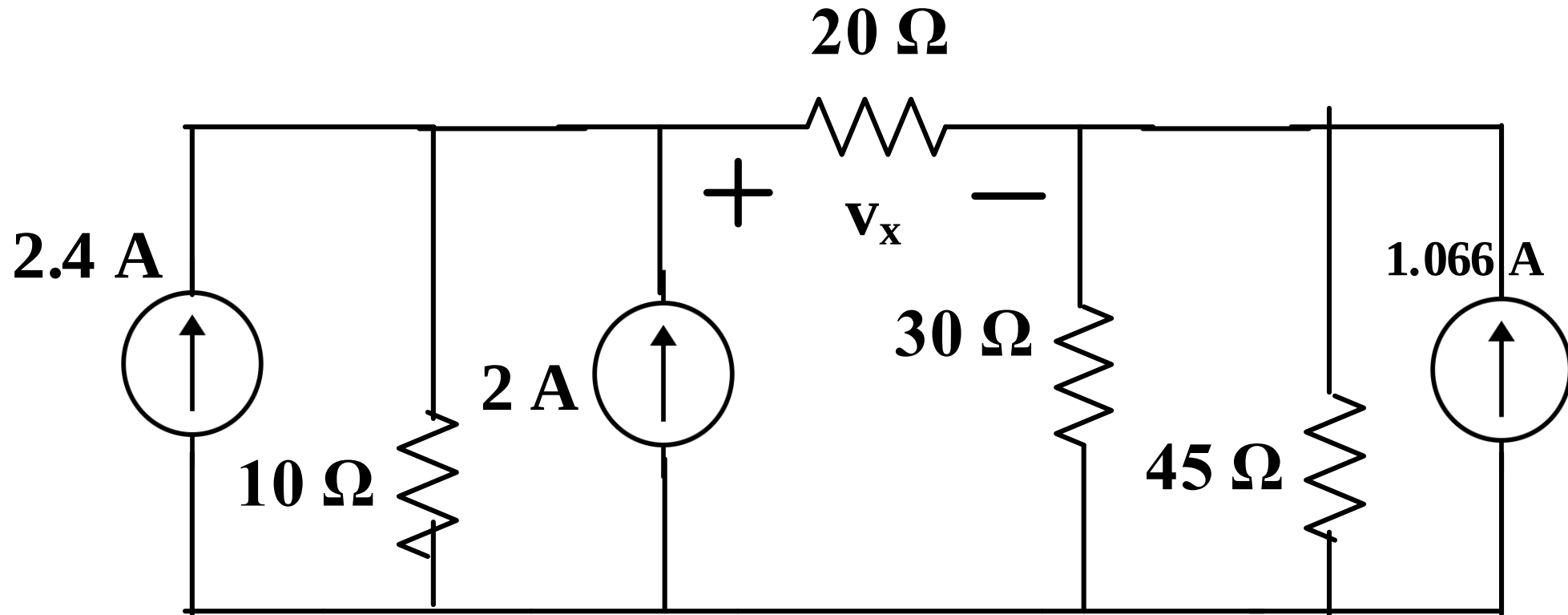Converting both the VOLTAGE SOURCES (24V and 48V) into current sources:



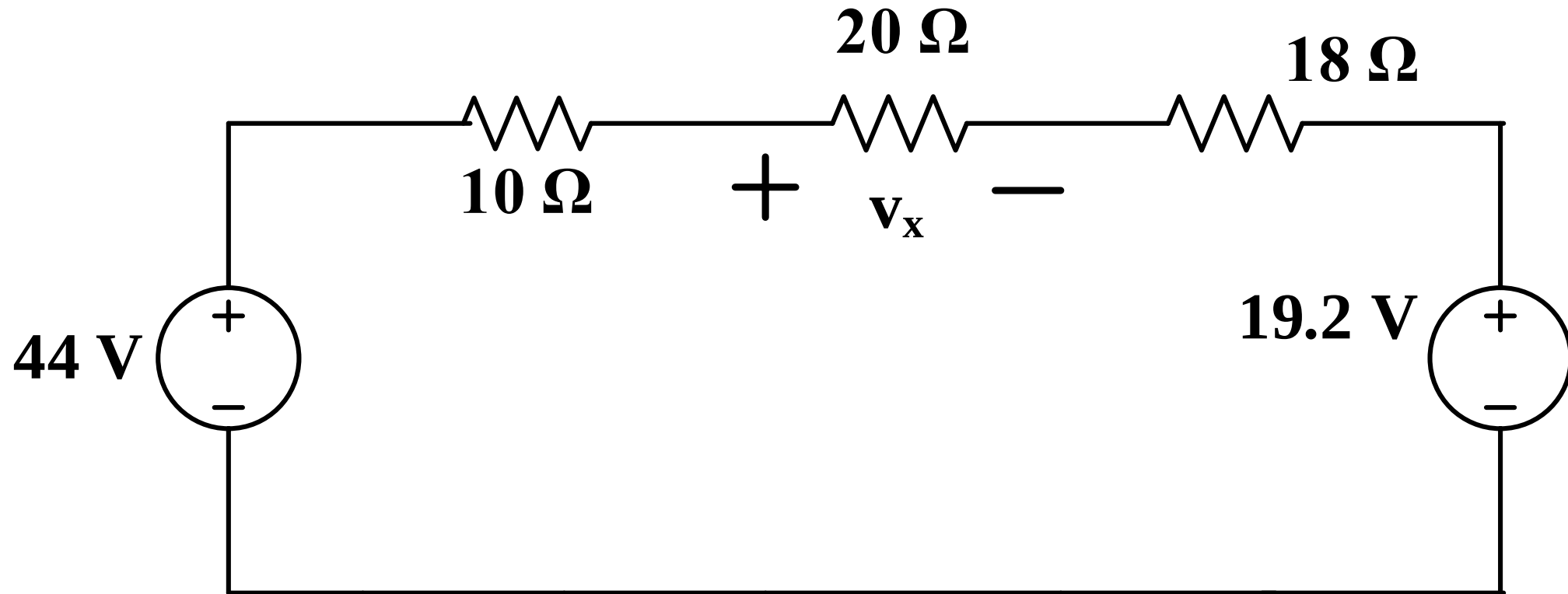Converting all the CURRENT SOURCES into Voltage sources:



$$\text{Loop current } i = \frac{44-19.2}{10+20+18} = 0.516\text{A}$$

$$V_X = 0.516 \times 20 = 10.33 \text{ V}$$

END