


# EE101ME – Electric Circuits


# Thevenin's Theorem
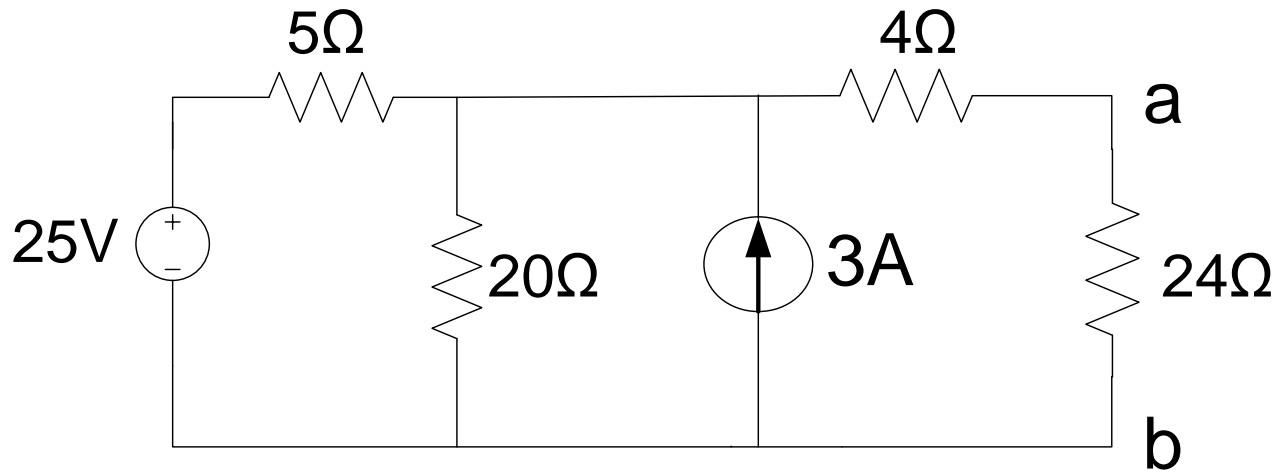
# Thevenin's Theorem


**Theorem** : Any two-node linear network (circuit) may be replaced by a voltage source equal to the open circuit voltage between the nodes in series with the resistance as seen by a load at this port

Find voltage  $V_{ab}$  across a-b ( $24\Omega$  resistor or load) using Thevenin's theorem.



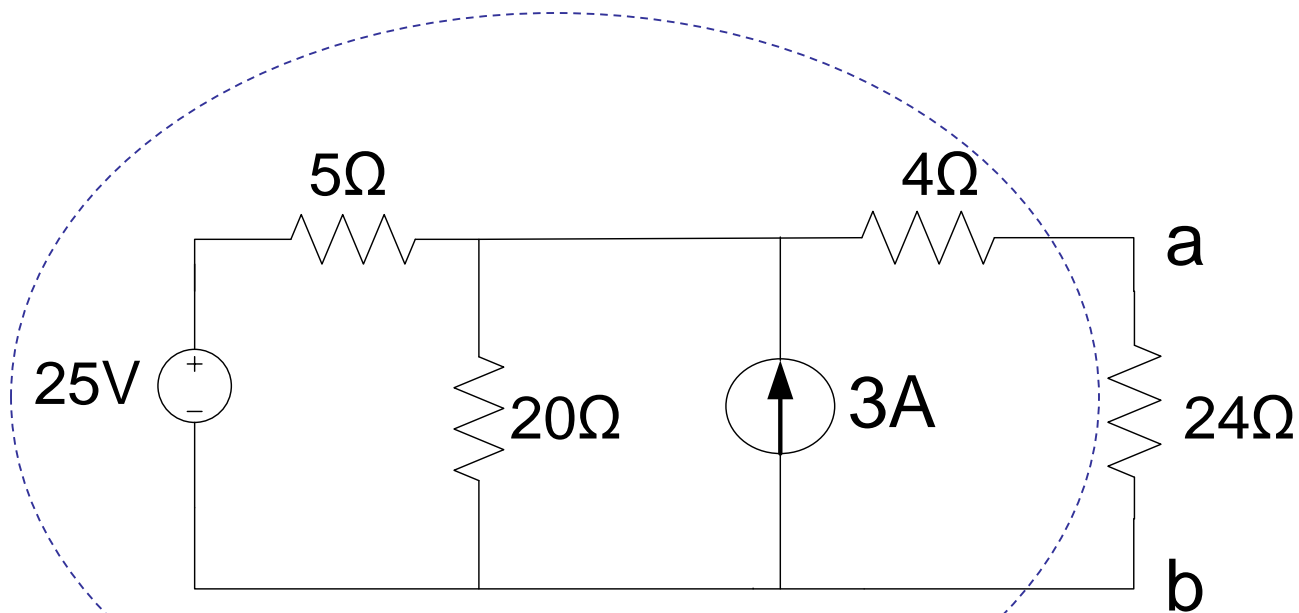

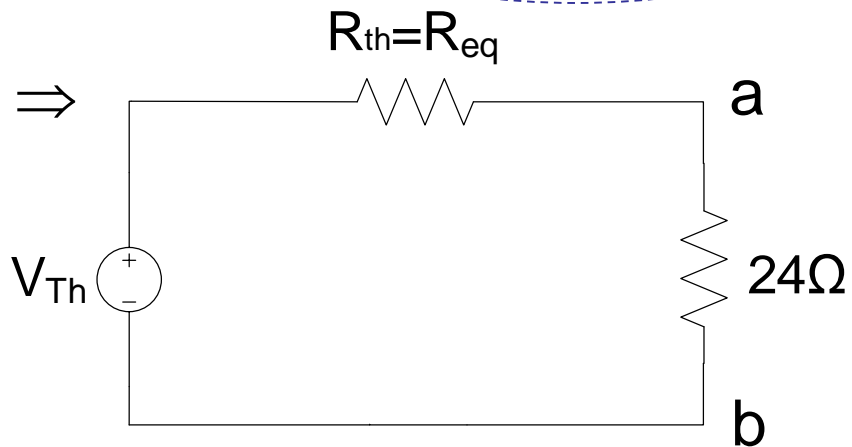Replace by  
Thevenin's Equivalent Circuit




Thevenin's Equivalent Circuit

$V_{Th}$  – Open circuit voltage across a-b


$R_{th} = R_{eq}$  - Equivalent Resistance as seen by the load after deactivating all independent sources (setting to 0)

1. Open Circuit at nodes (terminals) a-b

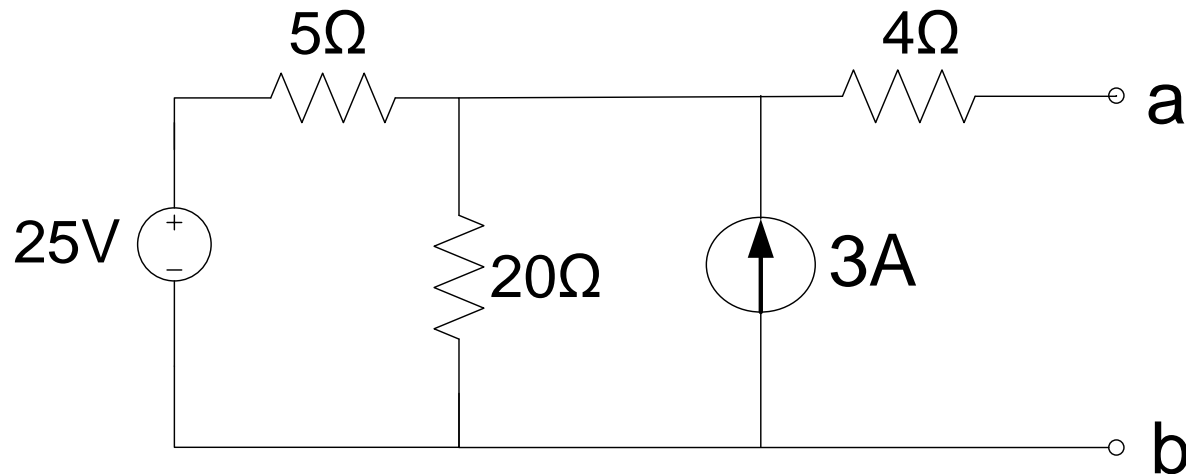

$$V_{Th}$$

$$V_{Th} = v_1$$

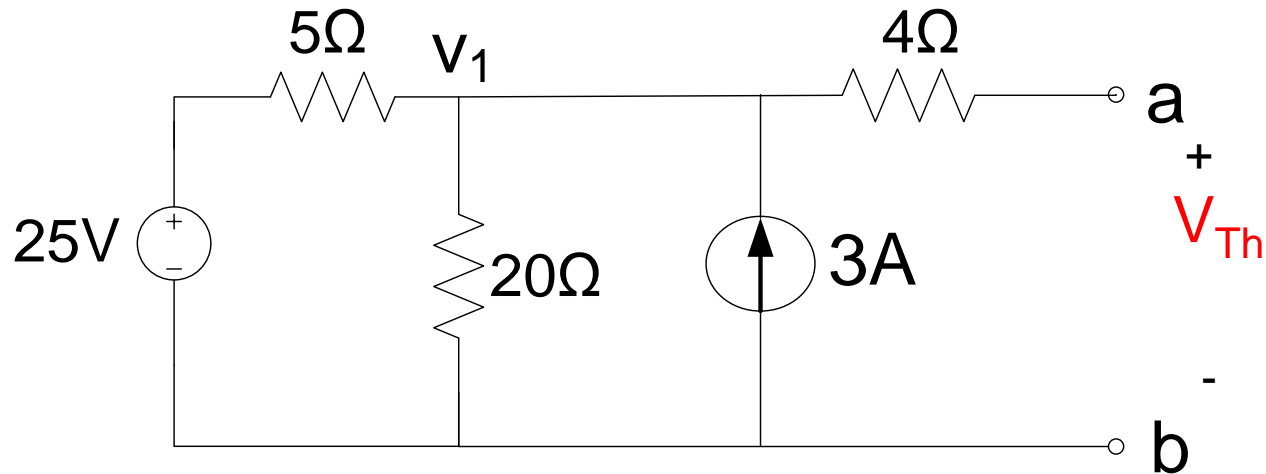

Applying nodal analysis,

$$\frac{v_1 - 25}{5} + \frac{v_1}{20} = 3$$

$$V_{Th} = 32V$$


$$v_1 = 32V$$

$$R_{eq} = R_{th}$$


➤ Deactivate all independent sources (SET to 0)

✓ Voltage sources – short circuit

✓ Current sources – Open circuit

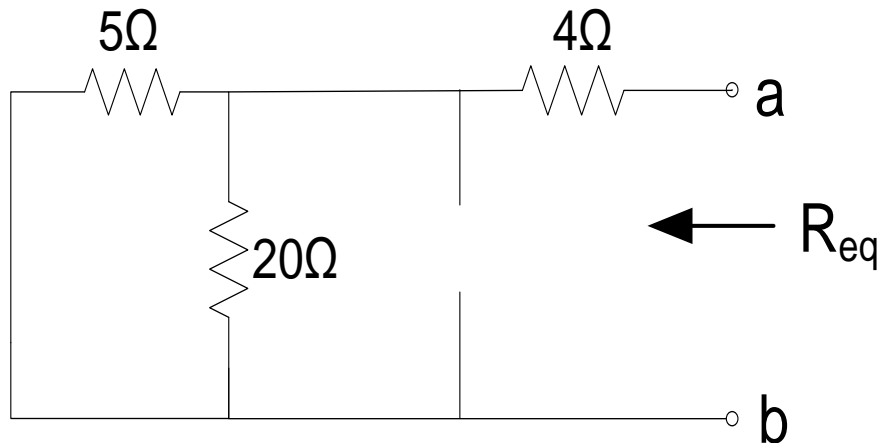

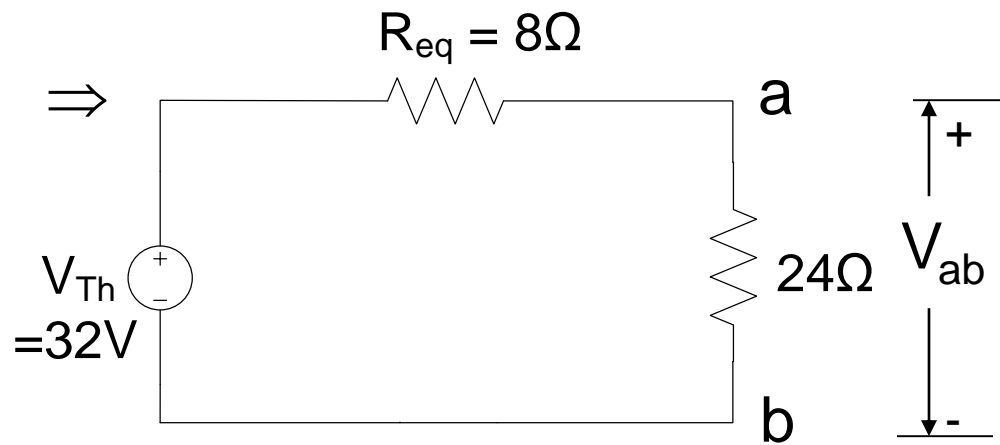
$$R_{eq} = 4 + 20 \parallel 5 = 4 + 4 = 8\Omega$$



$$V_{ab} = 32 \times \frac{24}{24 + 8} = 24V$$



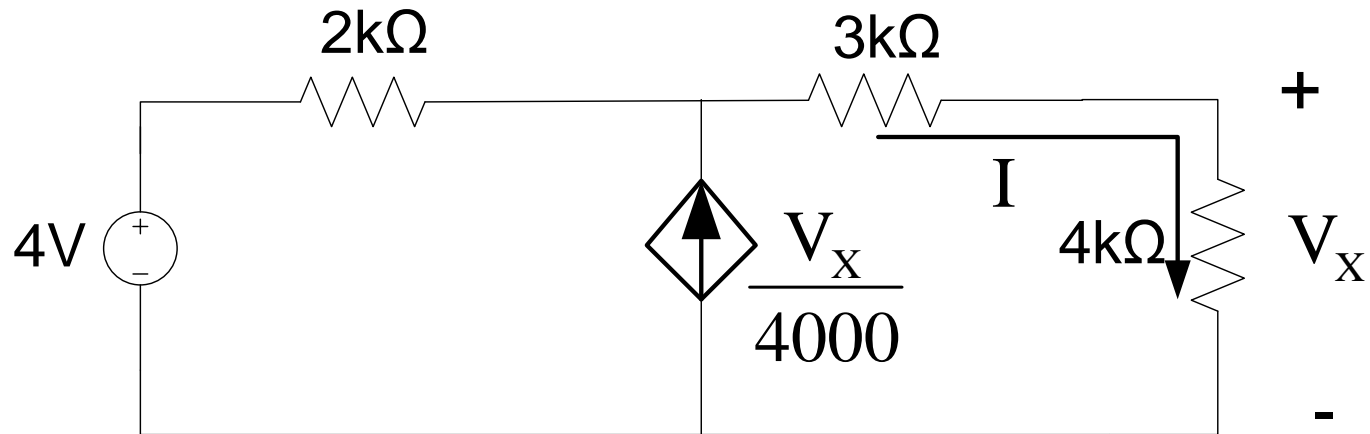
Find  $I$  (current through  $4\text{k}\Omega$ ) applying Thevenin's Theorem



## Solution

$$V_{Th}$$

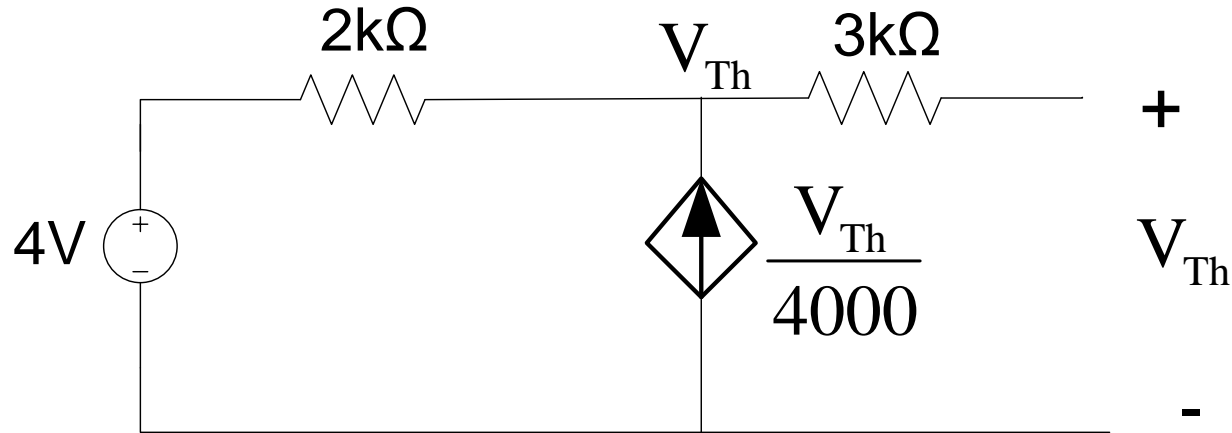1. Open Circuit the  $4k\Omega$  resistance



Applying nodal analysis,


$$\frac{V_{Th} - 4}{2000} = \frac{V_{Th}}{4000}$$

$$\text{or, } 2V_{Th} - 8 = V_{Th}$$

$$V_{Th} = 8V$$


$R_{eq}$

# 1. Deactivate the independent sources

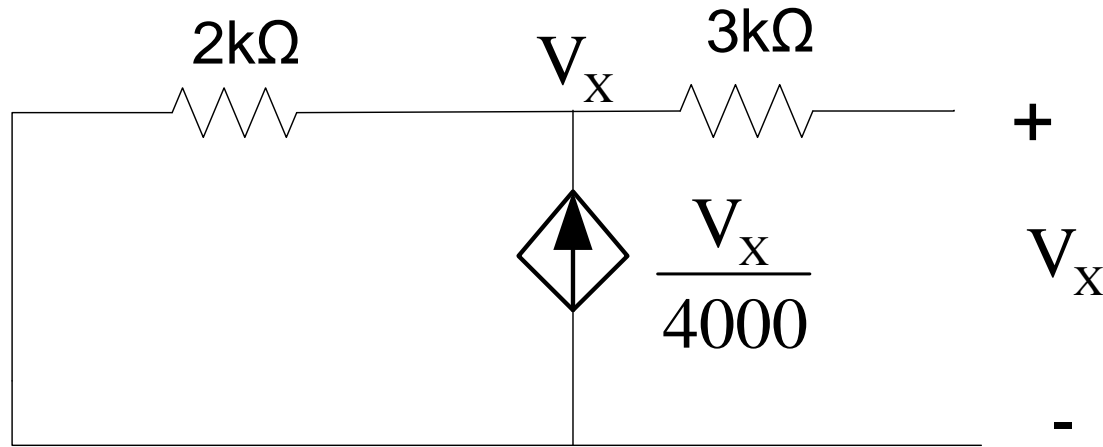

You must NOT deactivate DEPENDENT source(s)

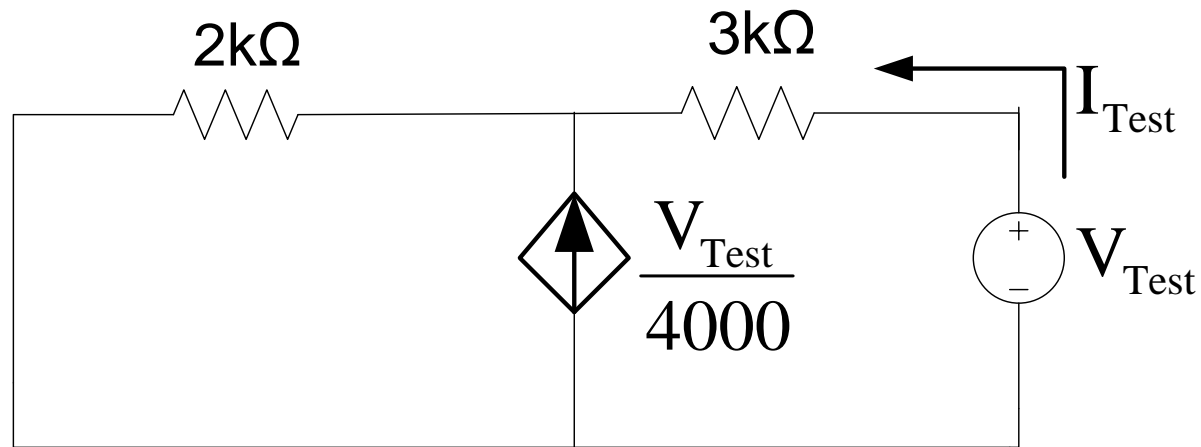1. Apply a test voltage  $V_{\text{Test}}$



Applying nodal analysis,

$$I_{\text{Test}} + \frac{V_{\text{Test}}}{4000} = \frac{(V_{\text{Test}} - I_{\text{Test}} \times 3000)}{2000}$$


$$4000I_{\text{Test}} + V_{\text{Test}} = 2V_{\text{Test}} - 6000I_{\text{Test}}$$

$$V_{\text{Test}} = 10000I_{\text{Test}}$$

$$\frac{V_{\text{Test}}}{I_{\text{Test}}} = 10000 = 10\text{k}\Omega$$

$$R_{\text{eq}} = 10\text{k}\Omega$$

## Thevenin's Equivalent Circuit

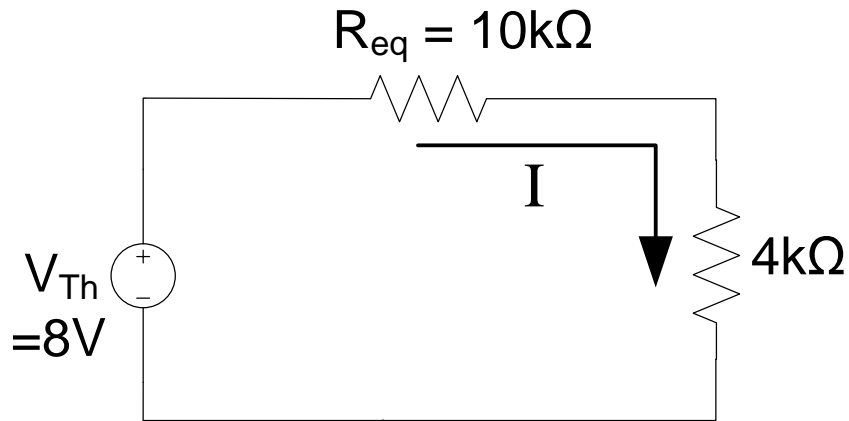

Current through the  $4\text{ k}\Omega$  resistor becomes

$$I = \frac{8}{10 + 4} = 0.571\text{mA}$$

END