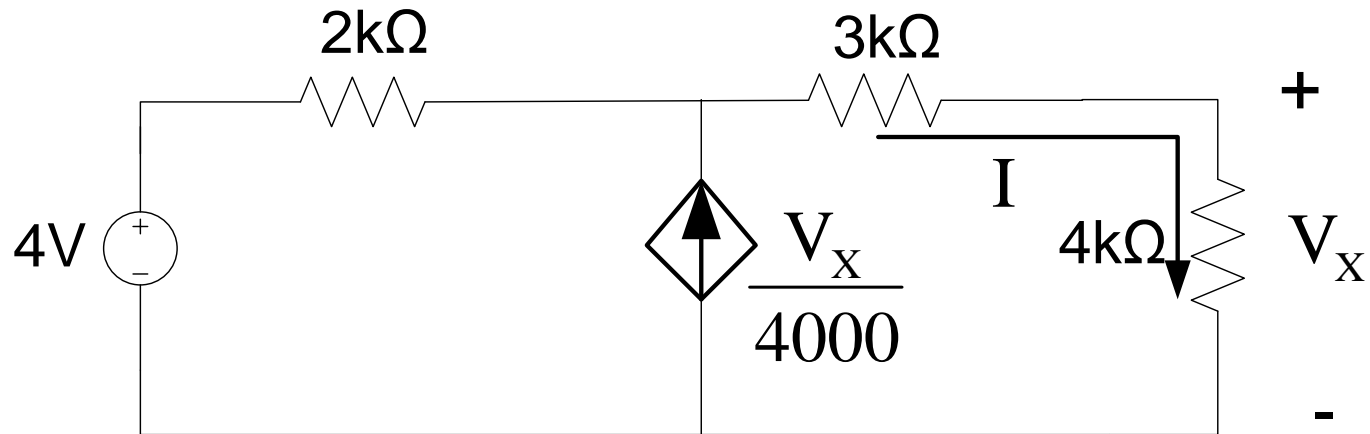


# EE 101ME – Electric Circuits

# **Revisiting Thevenin's Theorem**


Find  $I$  (current through  $4\text{k}\Omega$ ) applying Thevenin's Theorem



## Solution

$V_{Th}$

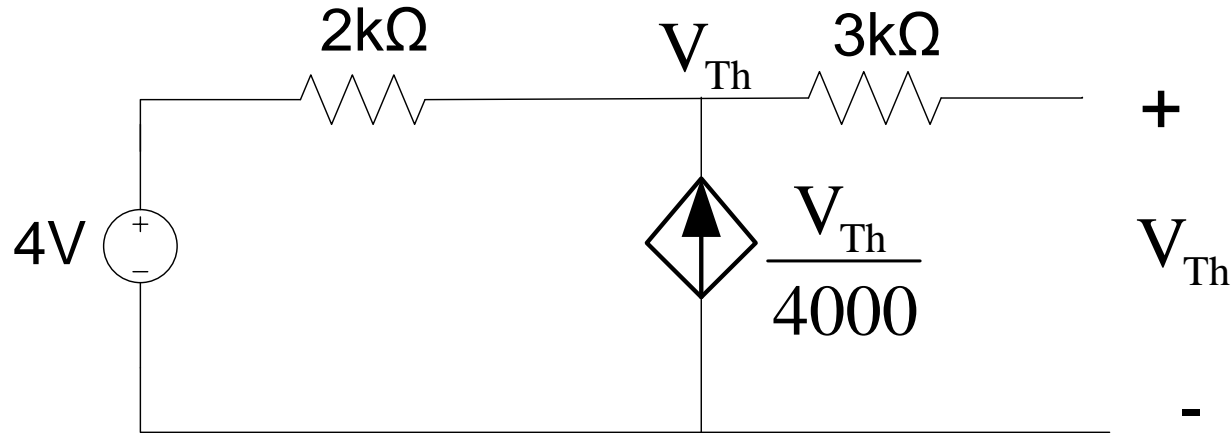1. Open Circuit the  $4k\Omega$  resistance



Applying nodal analysis,


$$\frac{V_{Th} - 4}{2000} = \frac{V_{Th}}{4000}$$

$$\text{or, } 2V_{Th} - 8 = V_{Th}$$

$$V_{Th} = 8V$$


$R_{eq}$

1. Deactivate the independent sources

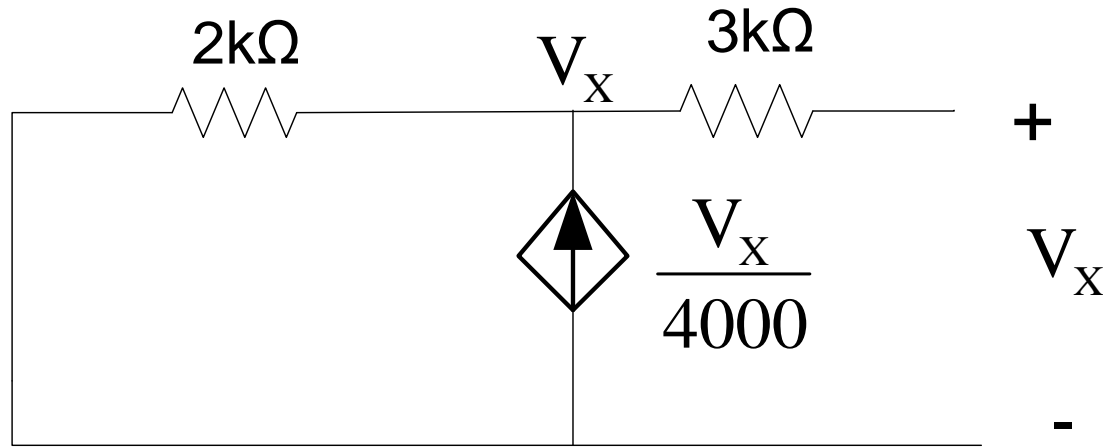

2. Do NOT deactivate dependent sources

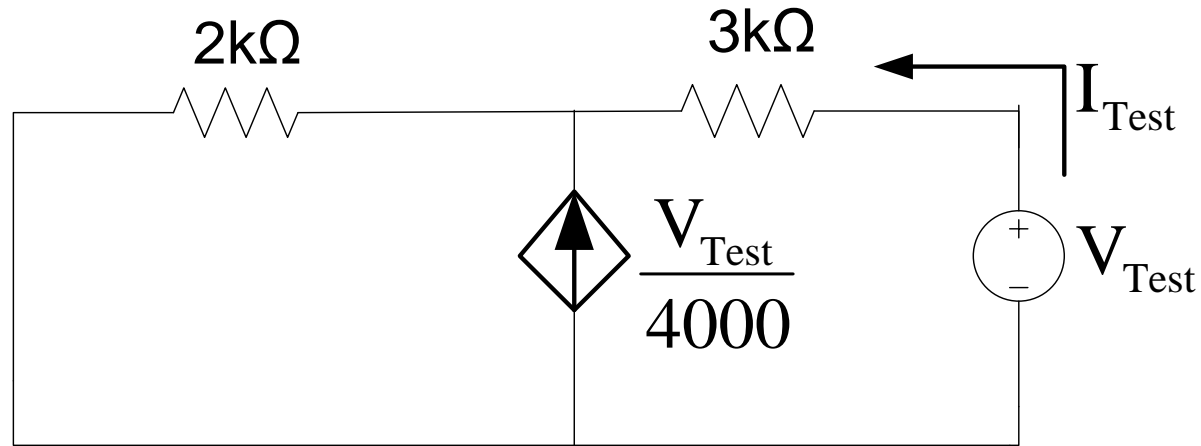1. Apply a test voltage  $V_{\text{Test}}$



Applying nodal analysis,

$$I_{\text{Test}} + \frac{V_{\text{Test}}}{4000} = \frac{(V_{\text{Test}} - I_{\text{Test}} \times 3000)}{2000}$$


$$4000I_{\text{Test}} + V_{\text{Test}} = 2V_{\text{Test}} - 6000I_{\text{Test}}$$

$$V_{\text{Test}} = 10000I_{\text{Test}}$$

$$\frac{V_{\text{Test}}}{I_{\text{Test}}} = 10000 = 10\text{k}\Omega$$

$$R_{\text{eq}} = 10\text{k}\Omega$$


## Thevenin's Equivalent Circuit

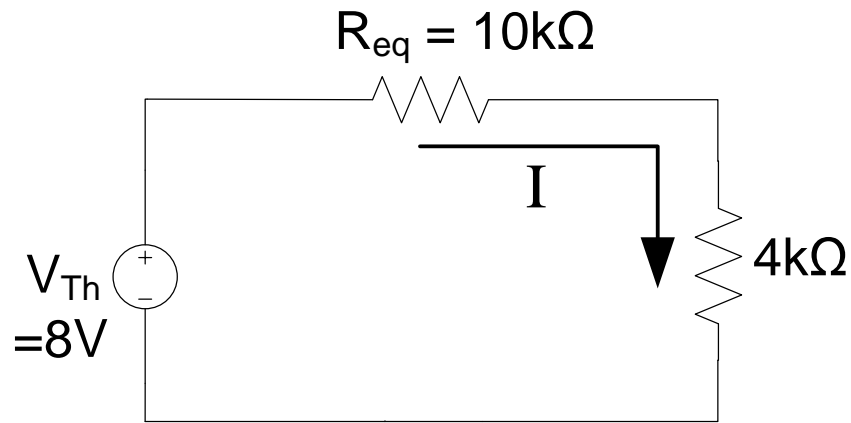

$$I = \frac{8}{10 + 4} = 0.571mA$$




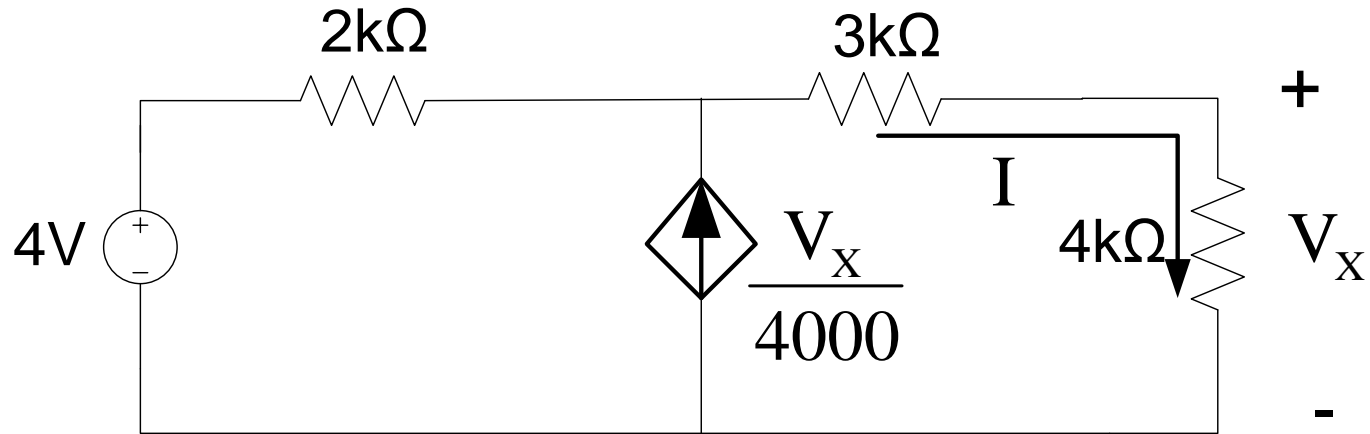
## Alternative Method to find $R_{eq} = R_{th}$



We know


$$V_{Th} = 8V$$

## Find Short Circuit Current $I_{sc}$

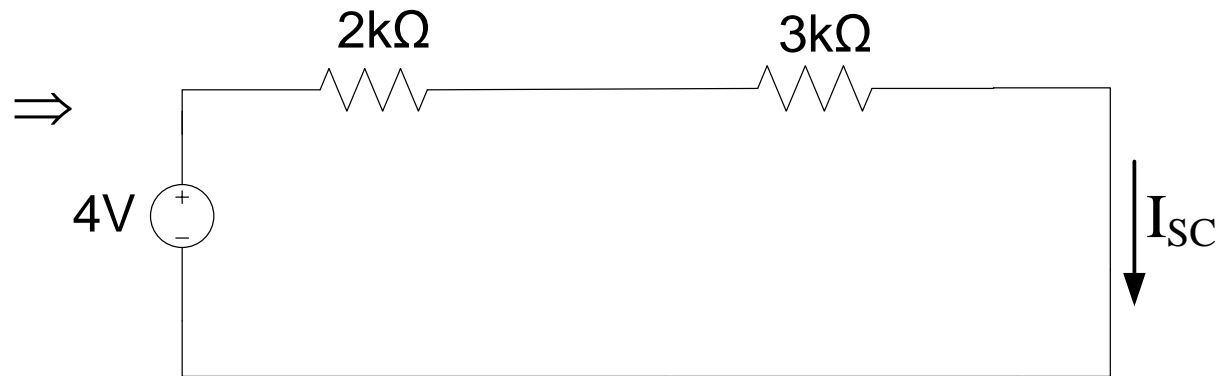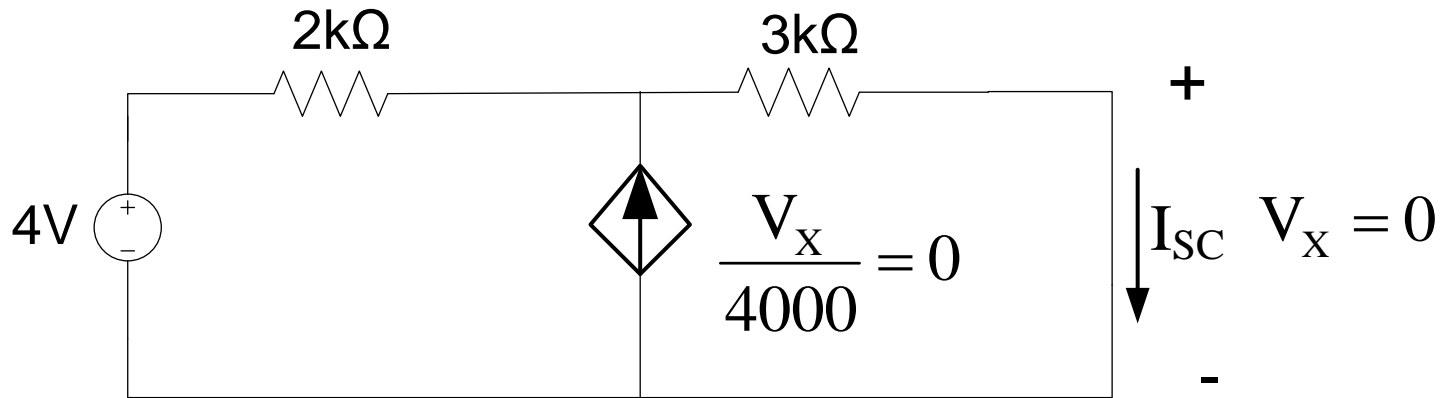

$$I_{sc} = \frac{4}{2k + 3k} = 0.8\text{mA}$$
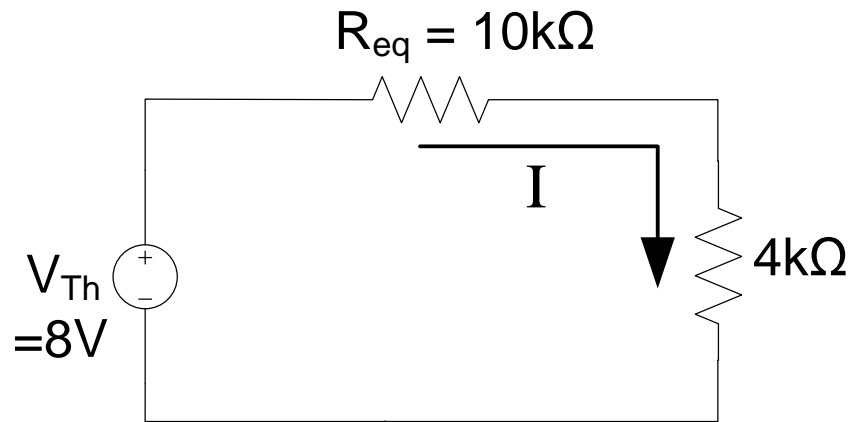
$$R_{eq} = \frac{V_{Th}}{I_{SC}} = \frac{8V}{0.8mA} = 10k\Omega$$



$$I = \frac{8}{10 + 4} = 0.571mA$$


Thevenin's Equivalent Circuit

# Norton's Theorem
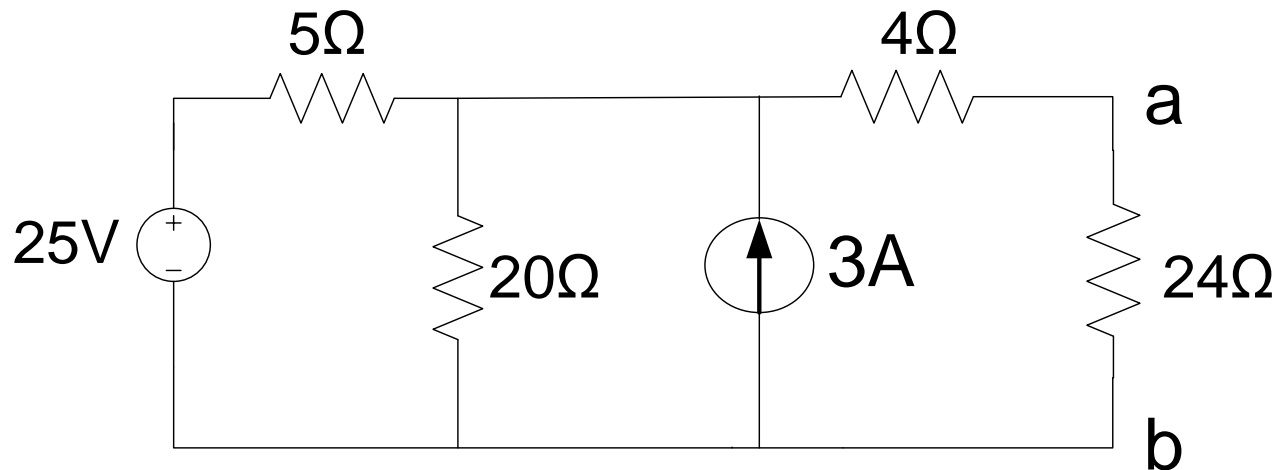
# Norton's Theorem


**Theorem** : Any two -node linear network may be replaced by a current source equal to the short circuited current between the nodes in parallel with the resistance as seen by a load at this port (terminal/node pair)

Q. Find voltage  $V_{ab}$  across terminal a-b (across  $24\Omega$  load) using Norton's theorem.





## Norton's Equivalent Circuit

$\Rightarrow$

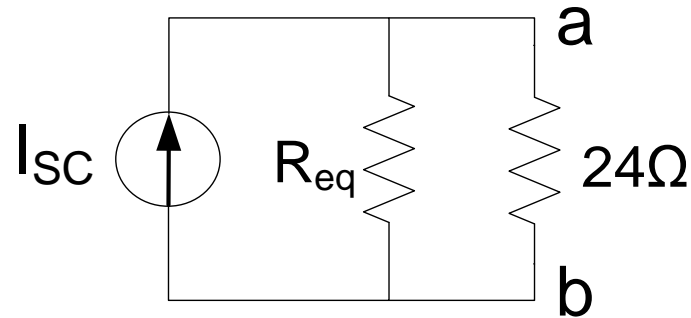

1. Short Circuit a-b and find  $I_{sc}$

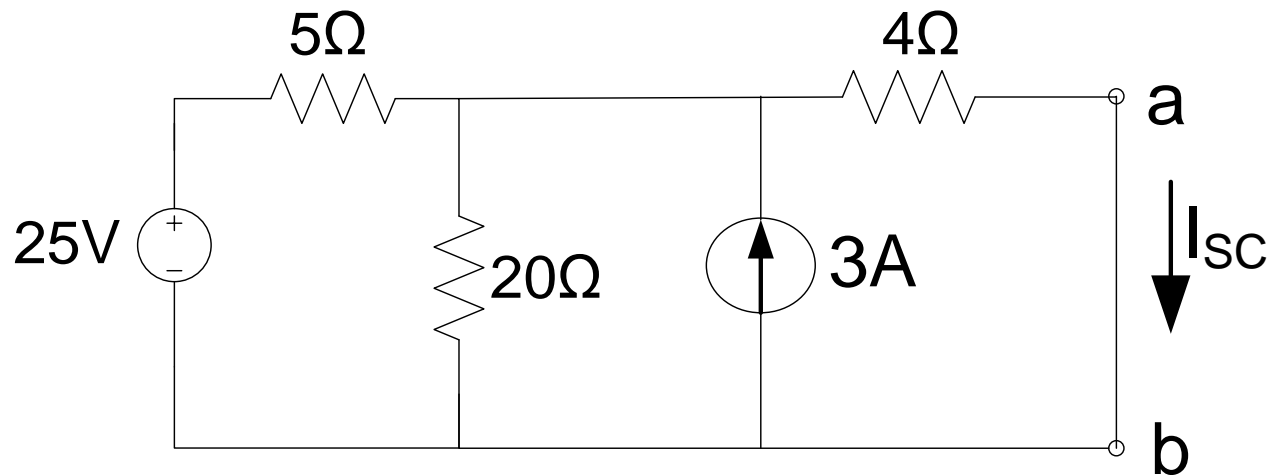

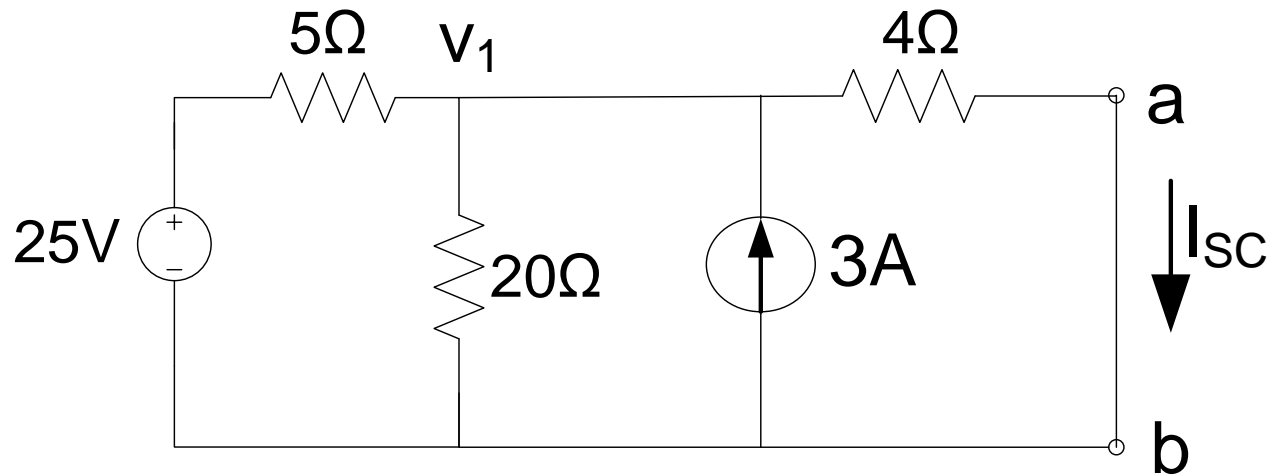

Applying nodal analysis,

$$\frac{v_1 - 25}{5} + \frac{v_1}{20} + \frac{v_1}{4} = 3$$

$$v_1 = 16V$$


$$I_{sc} = \frac{v_1}{4} = \frac{16}{4} = 4A$$

$$R_{eq}$$

➤ Deactivate all independent sources

✓ Voltage sources – short circuit


✓ Current sources – Open circuit

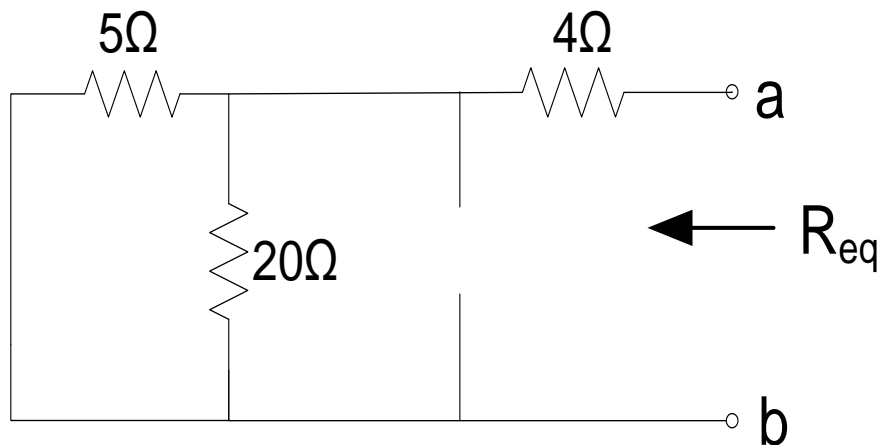

$$R_{eq} = 4 + 20 \parallel 5 = 4 + 4 = 8\Omega$$



$\Rightarrow$

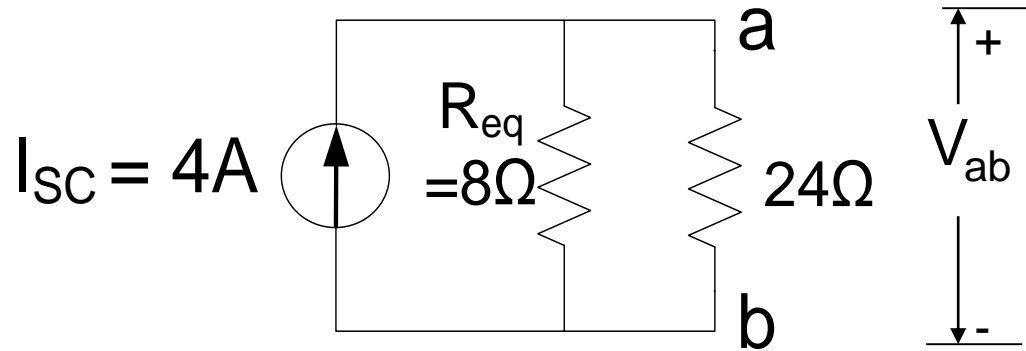

Norton' s Equivalent Circuit


Voltage  $V_{ab}$  across terminal a-b (across  $24\Omega$  load) is

$$V_{ab} = 4 \times \frac{8}{8 + 24} \times 24 = 24V$$

Thevenin's Equivalent Circuit

By Source Transformation

Norton's Equivalent Circuit

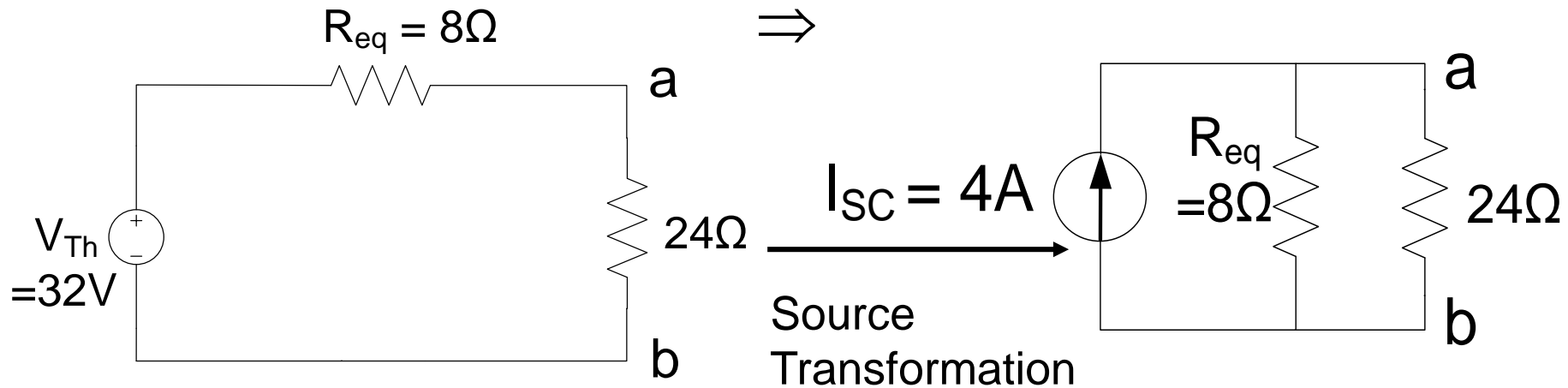

Thevenin's Equivalent Circuit


Norton's Equivalent Circuit

$$I_{SC} = \frac{V_{Th}}{R_{eq}}$$

$$R_{eq} = \frac{V_{Th}}{I_{SC}}$$

# Maximum Power Transfer


# Maximum Power Transfer

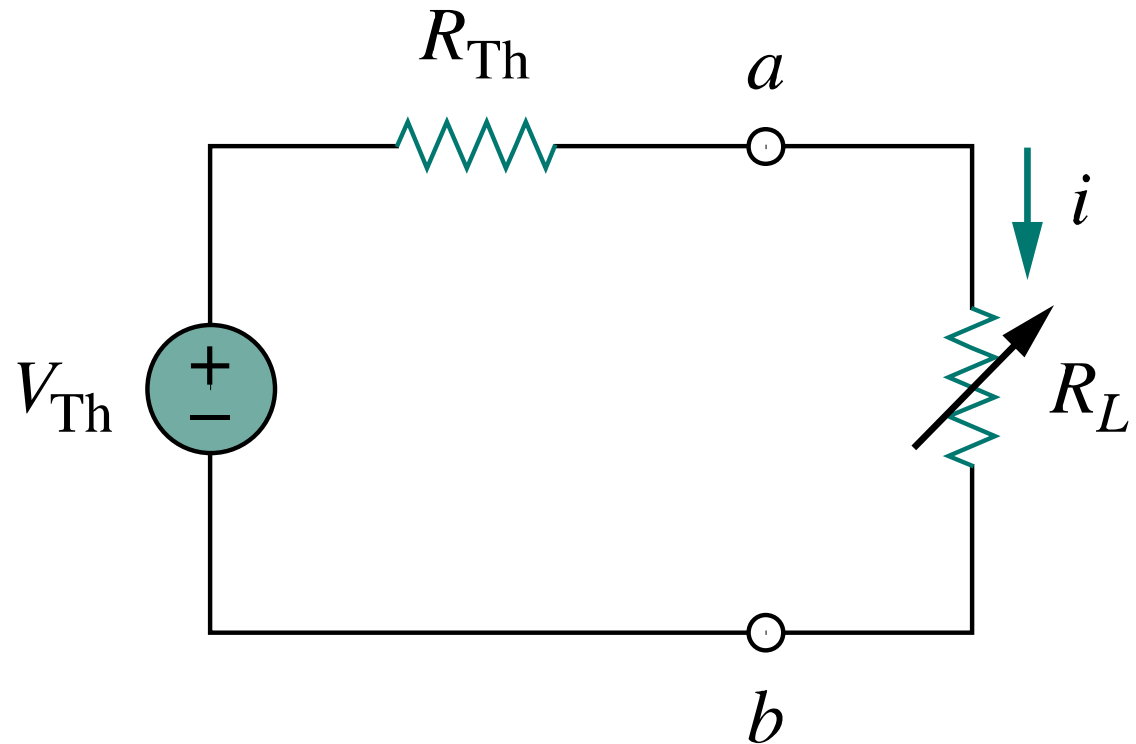

# Power delivered to load

$$p = i^2 R_L = \left( \frac{V_{\text{Th}}}{R_{\text{Th}} + R_L} \right)^2 R_L$$

# Plot between $p$ and $R_L$

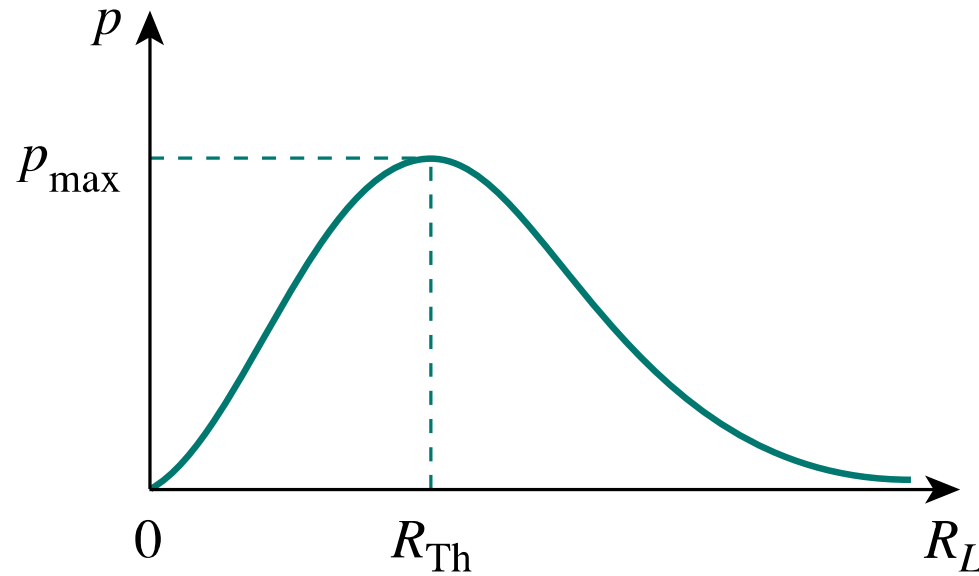

# Expression for $P_{max}$

$$\begin{aligned}\frac{dp}{dR_L} &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] \\ &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0\end{aligned}$$

which gives

$$R_L = R_{Th}$$

for delivering maximum power to the load resistor.


- Then, expression for maximum power

$$p_{\max} = \frac{V_{\text{Th}}^2}{4R_{\text{Th}}}$$


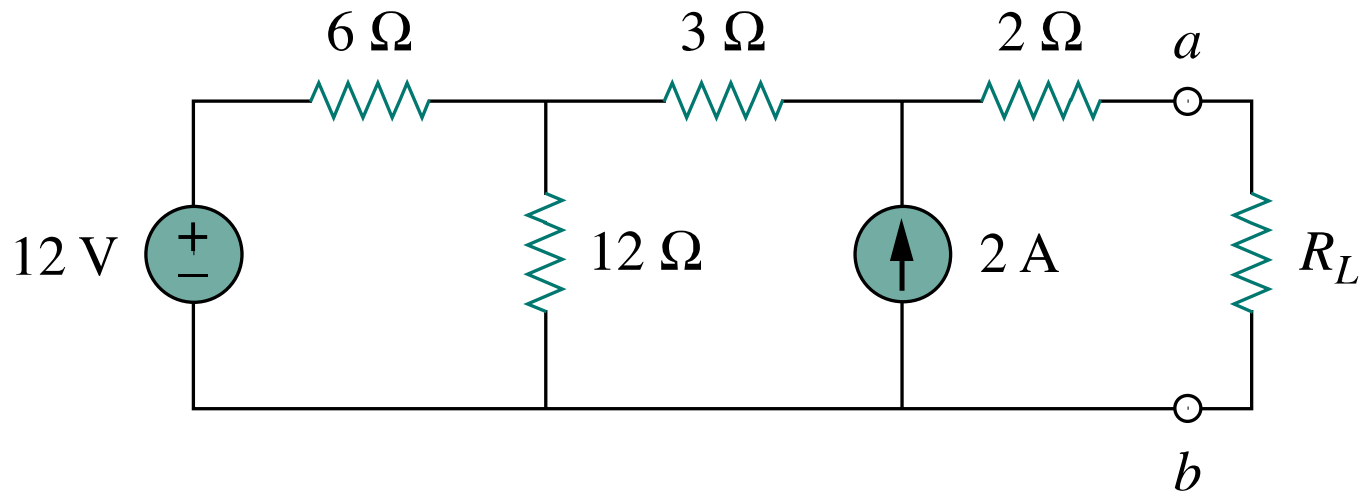
# Example

- Find maximum power that can be transferred to the load resistor  $R_L$ .



# Find $R_{TH}$ and $V_{TH}$

- Circuits to find the equivalent quantities

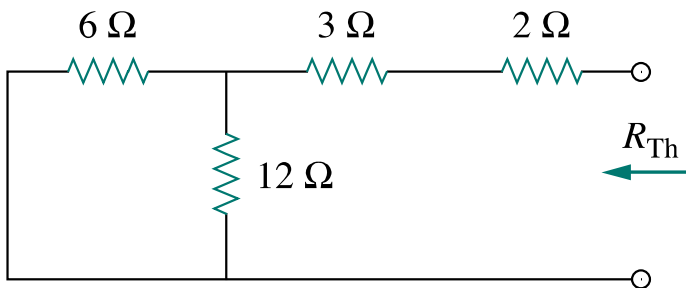


Fig.1

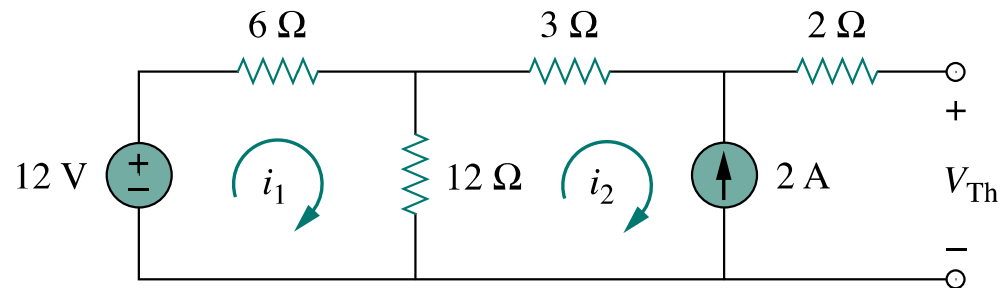


Fig.2

From Fig.1 it is easy to find  $R_{th} = 9\ \Omega$

Let's use mesh analysis of Fig.2. Loop current  $i_2 = -2\text{ A}$

Applying KVL to the leftmost loop of Fig.2, we get  $-12 + 6i_1 + 12(i_1 + 2) = 0$

Solving the above equation we get  $i_1 = -2/3\text{ A}$

KVL of the outer loop enables us to write

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0 \quad \Longrightarrow \quad V_{Th} = 22 \text{ V}$$

For maximum power transfer,

$$R_L = R_{Th} = 9 \Omega$$

and the maximum power is

$$p_{\max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$

END