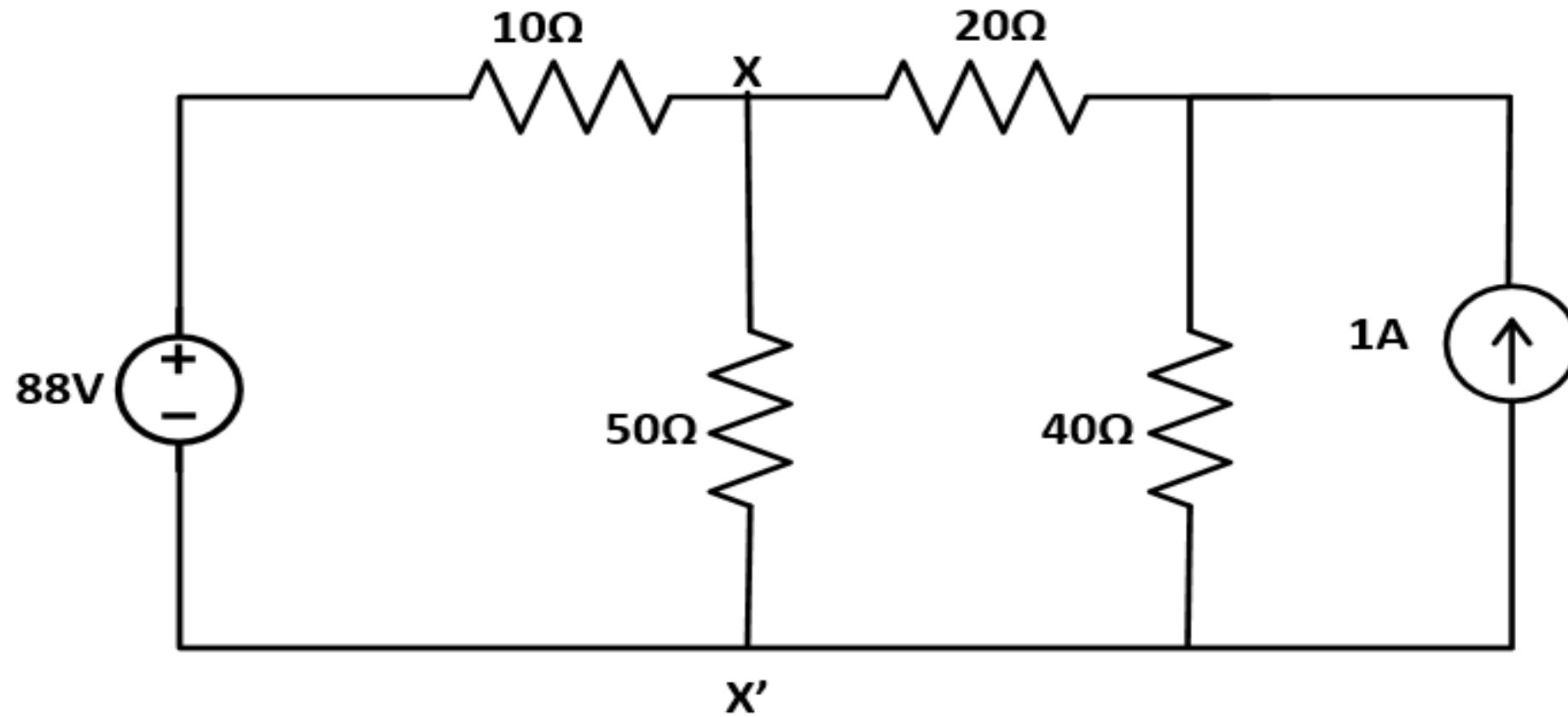


# EE 101ME – Electric Circuits


# Practice Problems

Q1. Find voltage across the terminal pair x-x' for the network shown below using

(a) Thevenin's equivalent circuit and (b) Norton's equivalent circuit



By Source transformation of 1A source,

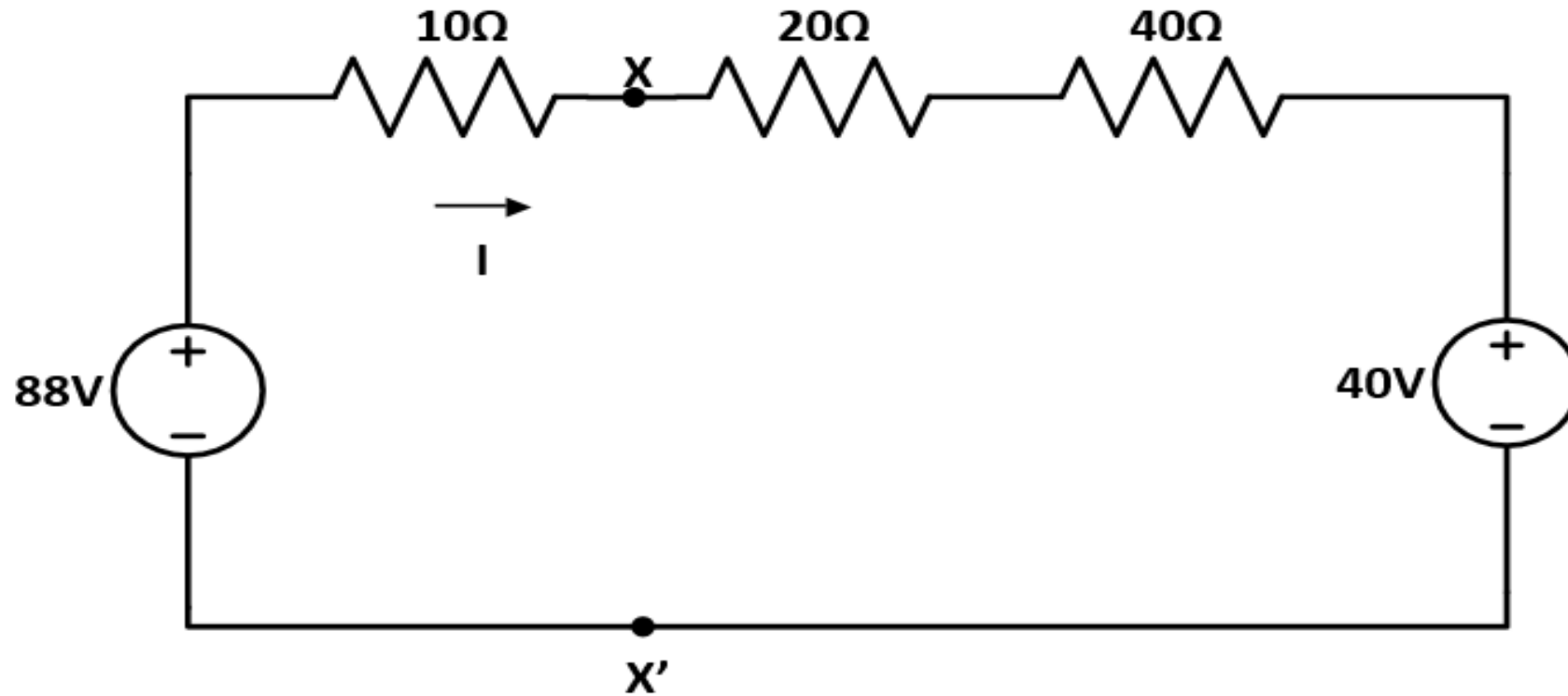


Voltage across X X' =  $V_{XX'} = 88 - 10 I$


$$= 88 - 10 \times 0.6857 = 81.143 \text{ V} \Rightarrow V_{\text{TH}} = V_{\text{THEVENIN}} = V_{XX'} = \mathbf{81.143}$$

Deactivating the independent sources,
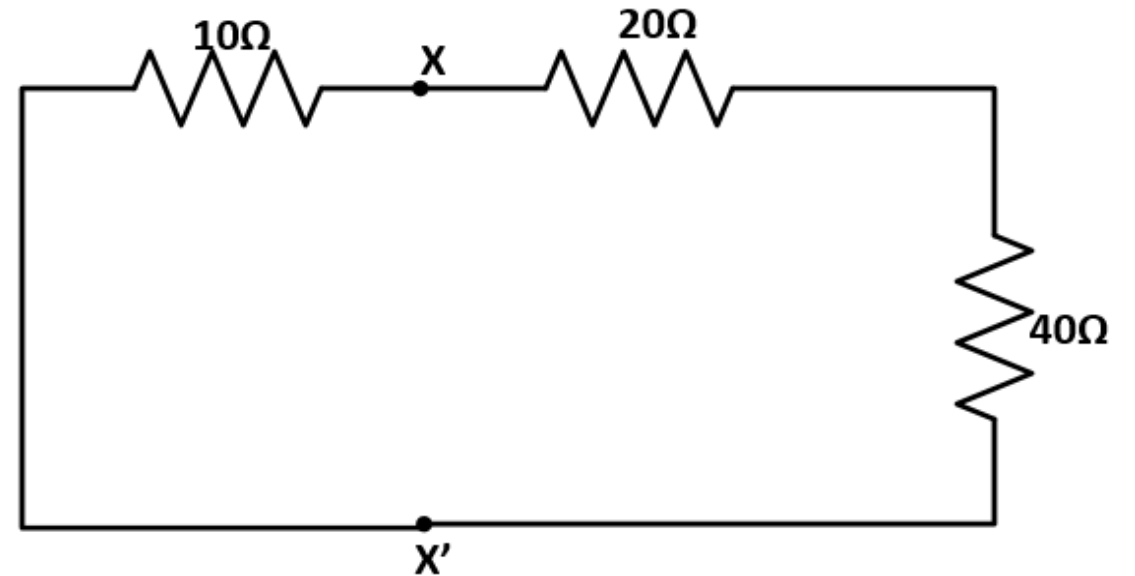
$$R_{TH} = 10 \parallel 60 = 8.57 \Omega$$




**Thevenin Equivalent Circuit:**

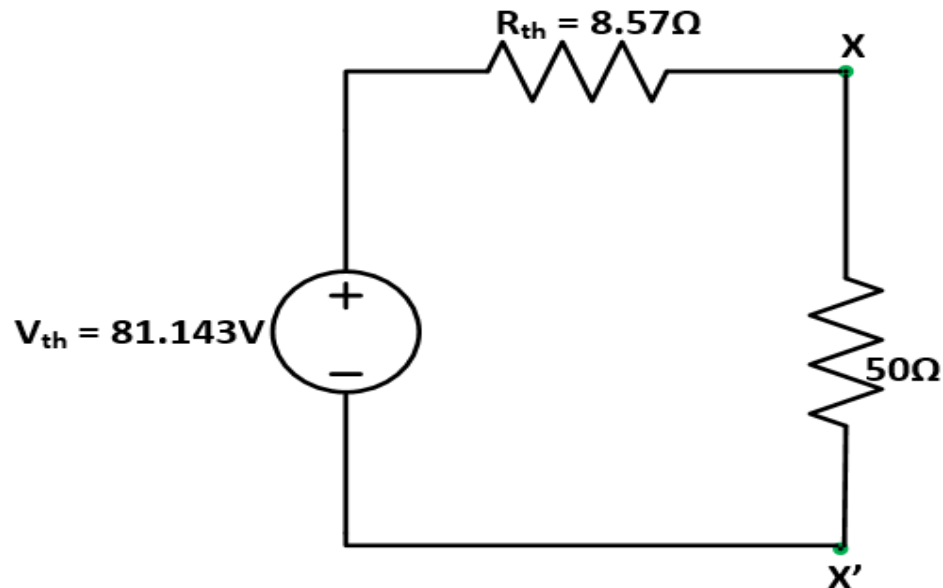

$$\begin{aligned} \text{Voltage across } xx' &= V_{TH} \frac{50}{50+8.57} \\ &= 81.143 \frac{50}{50+8.57} = \mathbf{69.27 \text{ V.}} \end{aligned}$$

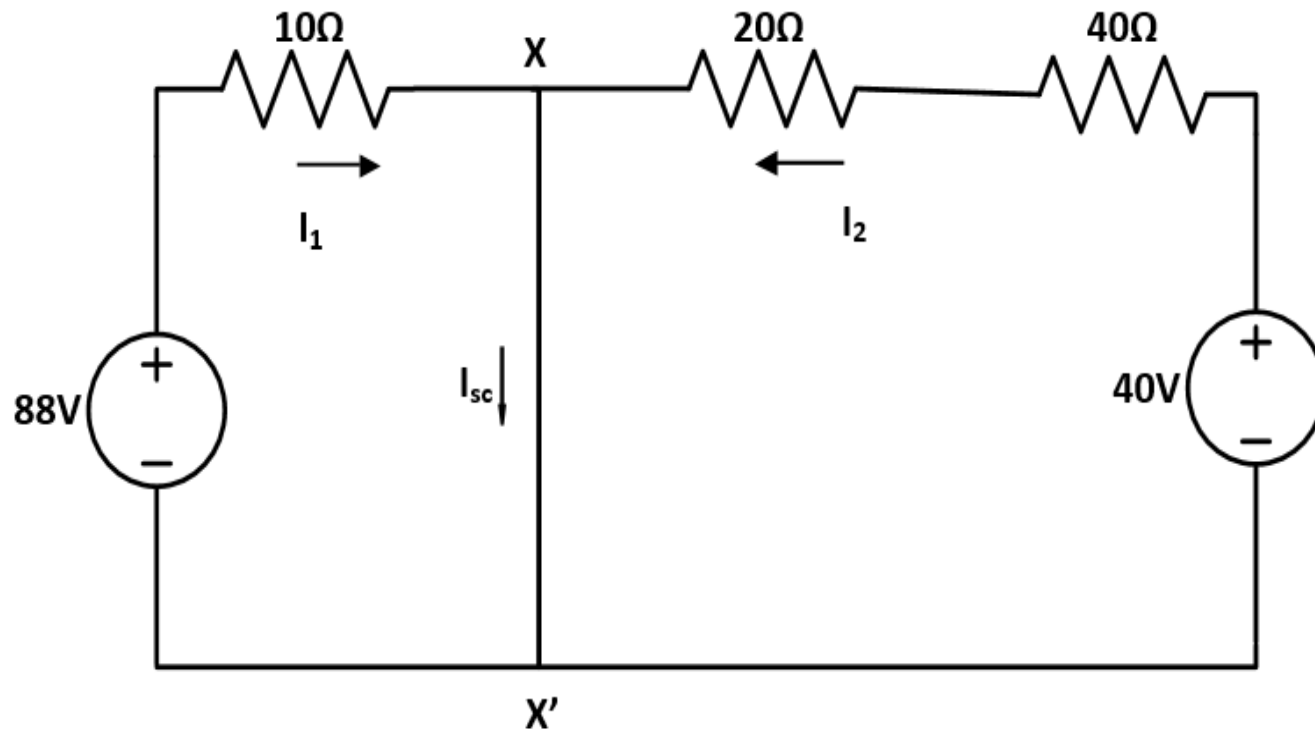Using Source transformation of 1A source,



Now, Loop I  $\Rightarrow$   $88 - 10 I_1 = 0$


or,  $I_1 = 8.8 \text{ A.}$

Loop II  $\Rightarrow$   $40 - I_2 \times 60 = 0$

or,  $I_2 = 0.67 \text{ A}$


Now  $I_{sc} = I_1 + I_2 = 9.47 \text{ A}$

∴ Norton equivalent circuit is

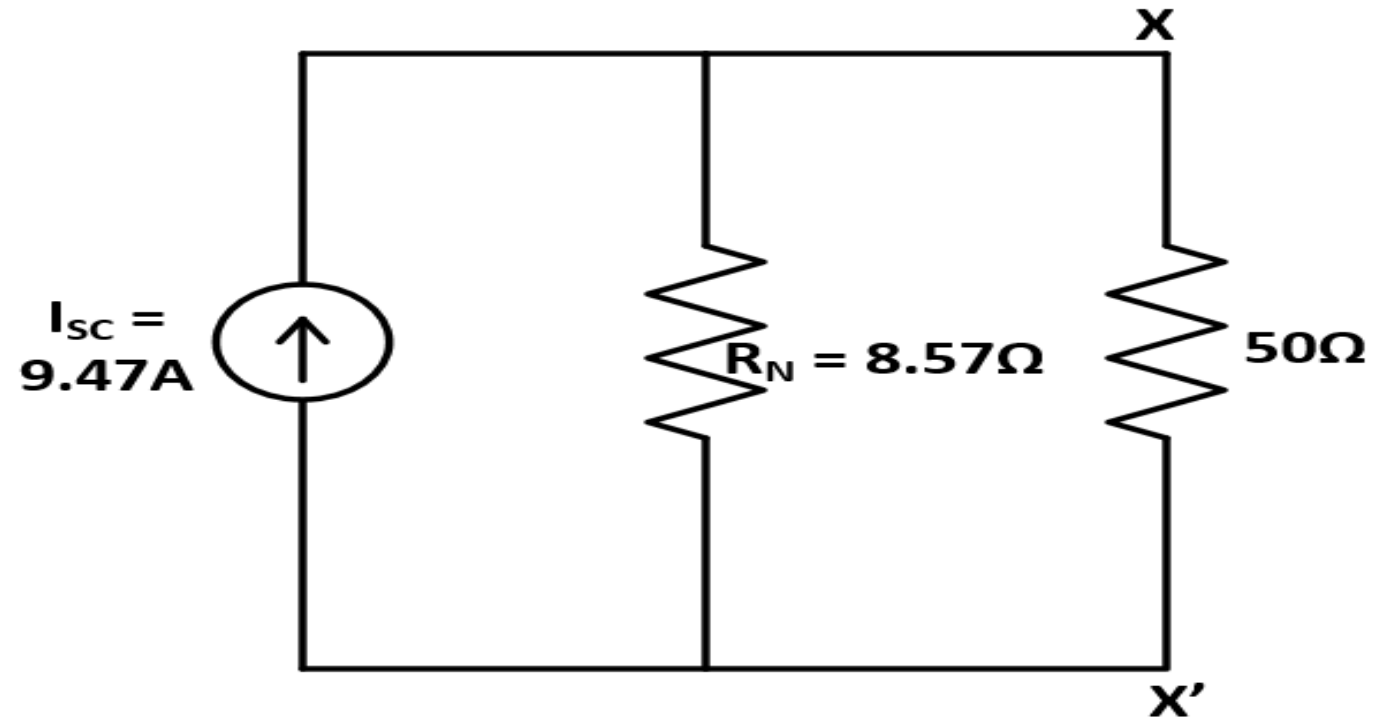


$$\text{Voltage across } xx' = I_{sc} \frac{8.57}{(8.57+50)} \times 50 = \mathbf{69.27 \text{ V.}}$$

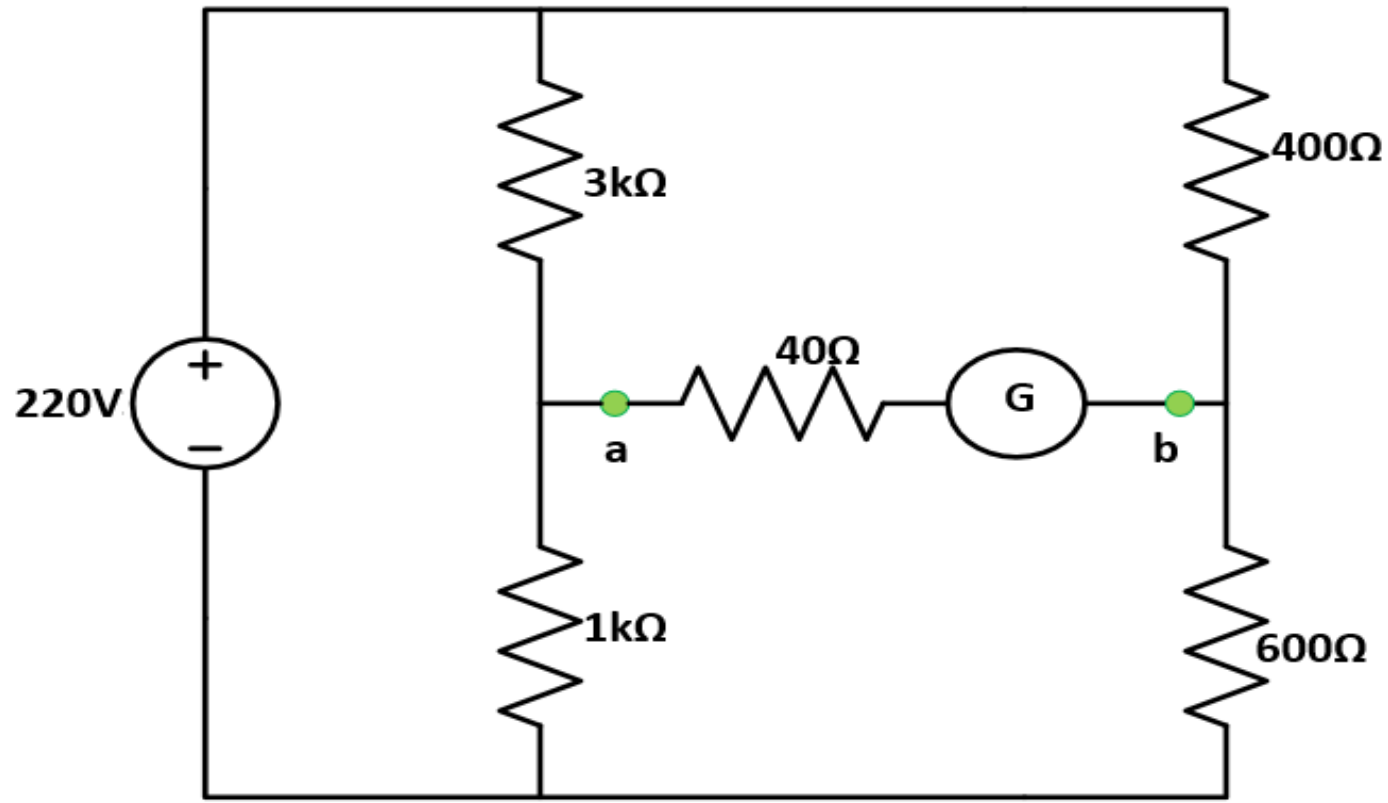Q2. Find current through the Galvanometer (G, from terminal a to terminal b) which has an internal resistance of  $40\ \Omega$ .





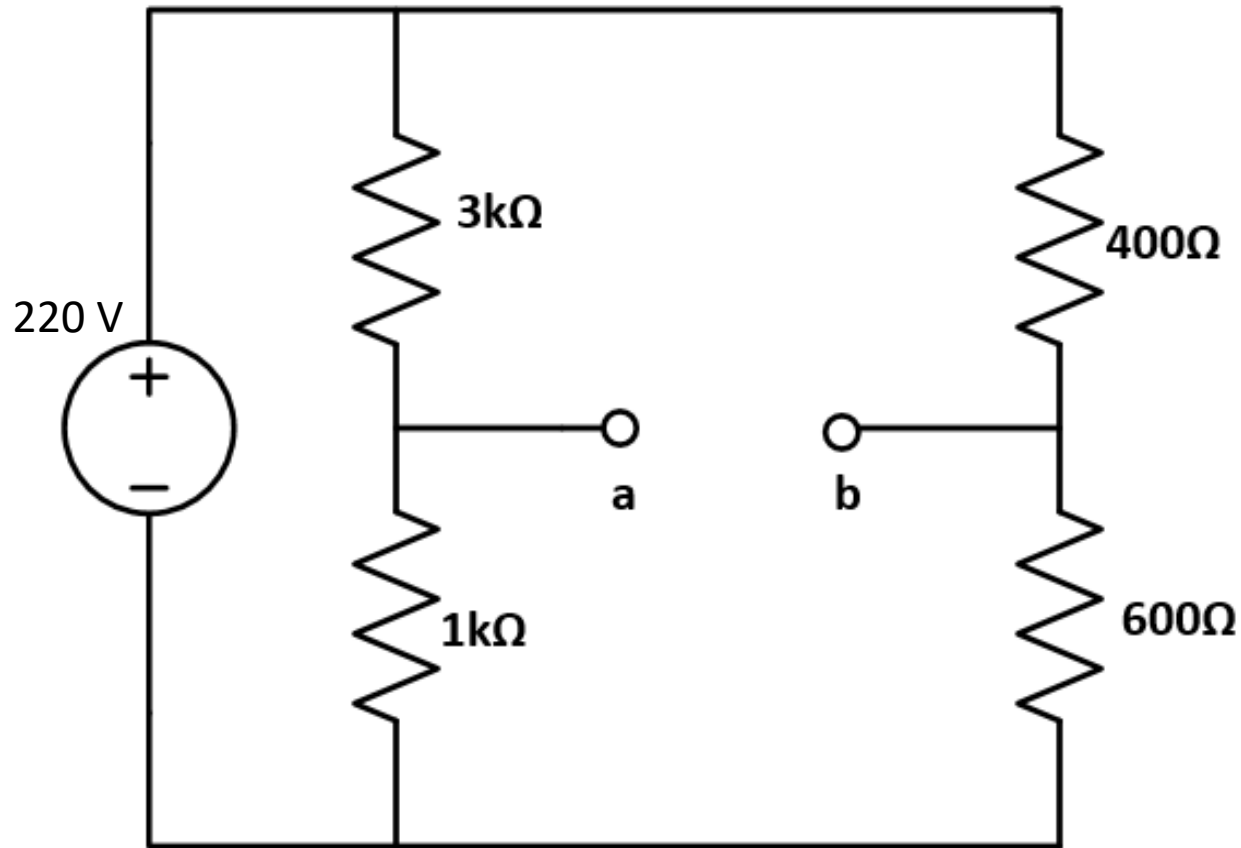

Thevenin equivalent across a-b are to be estimated.

$$V_a = \frac{1000}{1000 + 3000} \times 220 = 55 \text{ V}$$


$$V_b = \frac{600}{600 + 400} \times 220 = 132 \text{ V}$$

Applying KVL around loop **ab** gives

$$-V_a + V_{th} + V_b = 0$$

$$\Rightarrow V_{th} = V_a - V_b = 55 - 132$$


$$= -77 \text{ V}$$

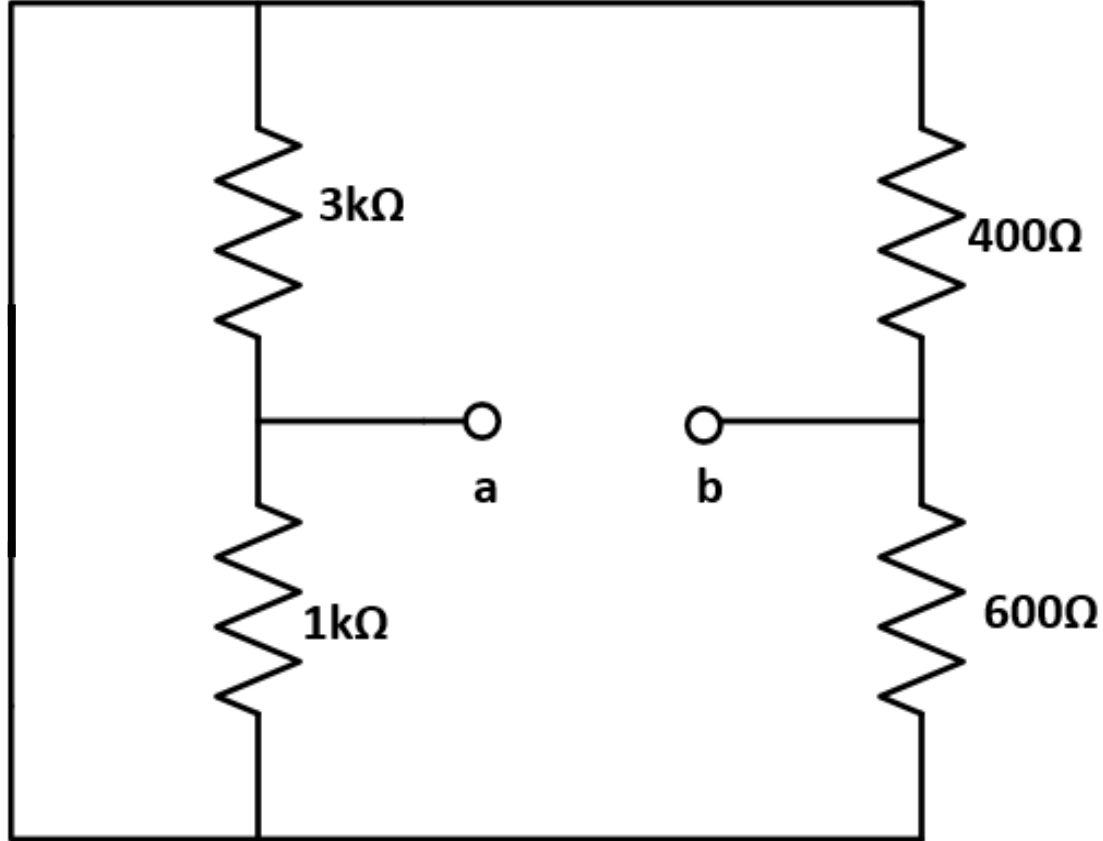

Notice that 3 kΩ and 1 kΩ resistors are in parallel and so are the 400 Ω and 600 Ω resistors. The two parallel combinations form a series combination with respect to terminals **a** and **b**.


$$\begin{aligned} R_{th} &= 3000 || 1000 + 400 || 600 \\ &= 990 \Omega \end{aligned}$$

The equivalent circuit is:

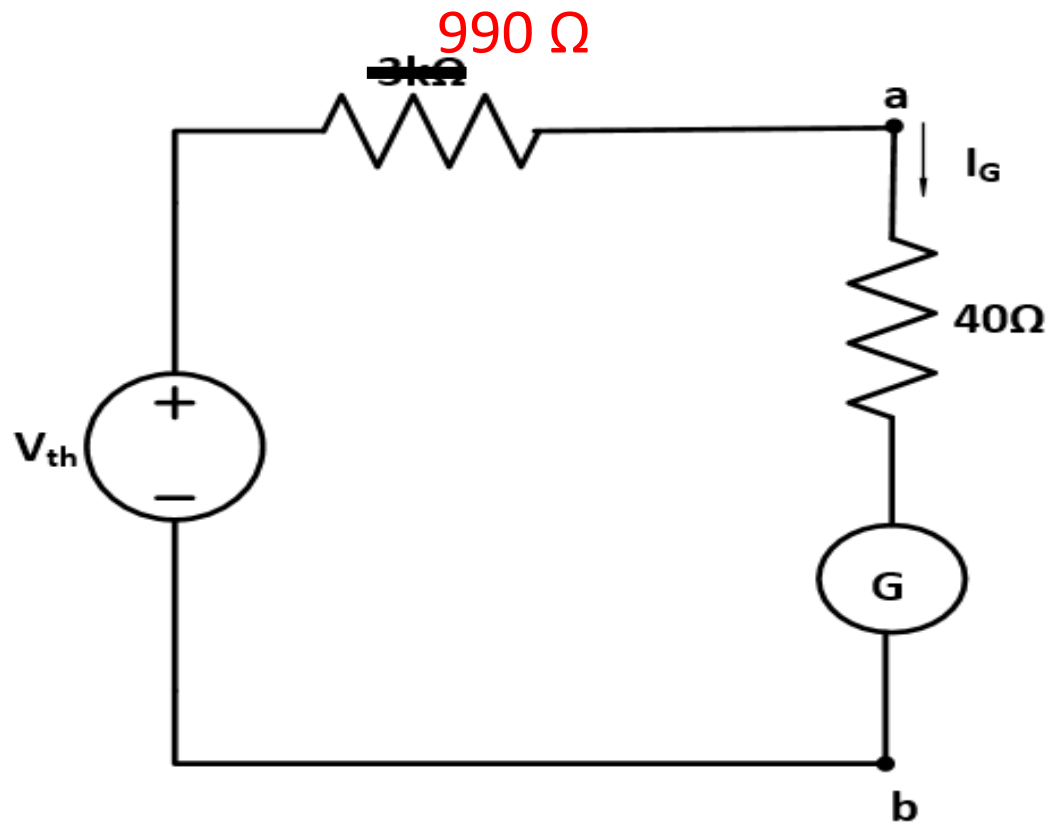

$$I_G = \frac{V_{Th}}{R_{Th} + R_m} = \frac{-77}{990 + 40} = -74.76mA$$

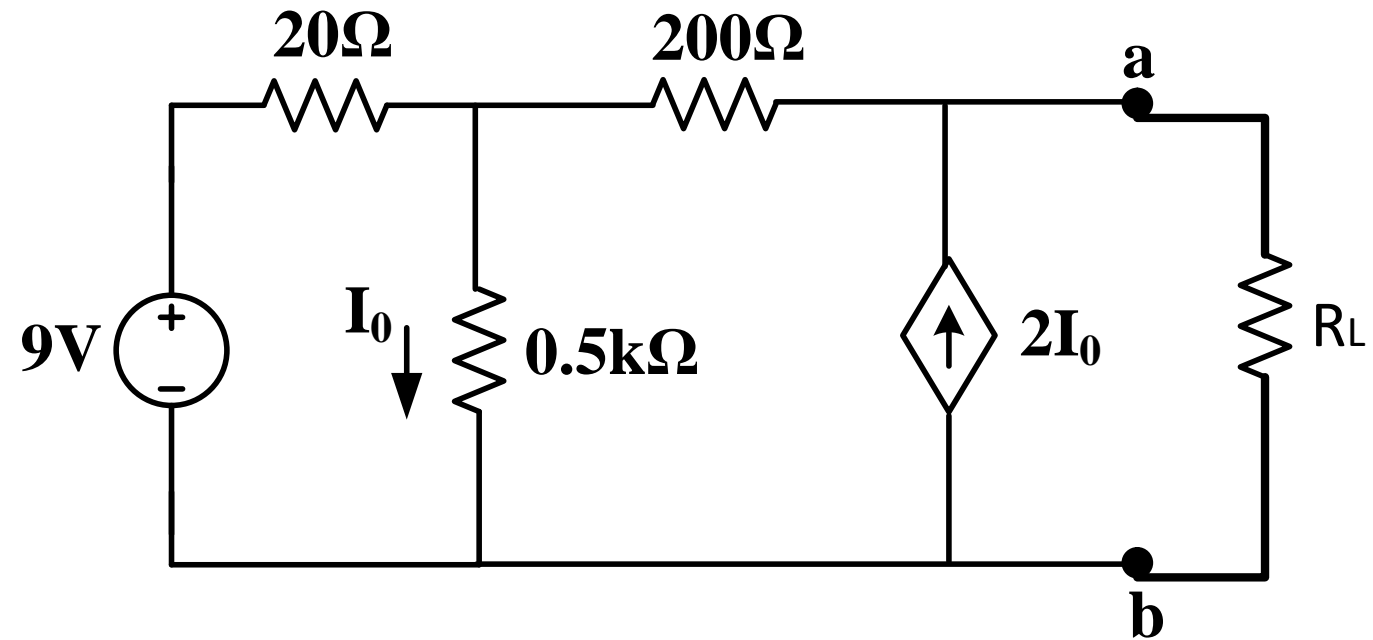Q3. Find maximum power delivered to the load resistor  $R_L$  of the following circuit.



After disconnecting  $R_L$ , let the voltage across  $0.5\text{ k}\Omega$  be  $V_x$  and the open circuit voltage across **a-b** be the Thevenin's voltage  $V_{th}$ .

Current through  $20\ \Omega$  is  $I_0$ . Then,  $9 + 20 I_0 = 500 I_0 \Rightarrow I_0 = 9/480$  giving  $V_{th} = 9 + 20 I_0 + 400 I_0 = 16.875\text{ V}$ .

Next, when a-b is short-circuited, let the current flowing from terminal a to terminal b be  $I_{sc}$ . Let the node voltage between the resistors  $20\ \Omega$  and  $200\ \Omega$  be  $V_x$ .

Then,  $(V_x - 9)/20 + V_x/500 + V_x/200 = 0 \Rightarrow V_x = 7.895\text{ V}$

$$I_{sc} = 2I_0 + V_x/200 = 2V_x/500 + V_x/200 = 0.071 \text{ A}$$

Now,  $R_{th}$  = Equivalent resistance across a-b

$$= V_{th}/I_{sc} = 237.676 \Omega$$

Maximum power delivered to the load  $R_L = 0.25 V_{th}^2 / R_{th} = 0.3$   
W (approx.)

END